

EXERCISE 1

Using the components, materials and equipment provided:

- (a) Connect the circuit as shown in figure 1. (3 marks)

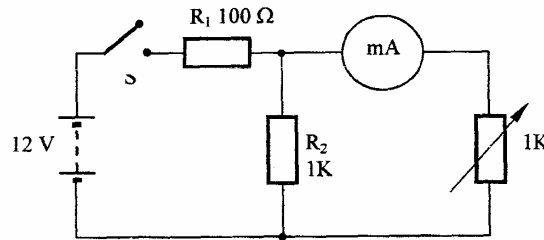


Figure 1

- (b) With the switch S open, adjust the power supply to 12v. Let the examiner check your work. (1 mark)
- (c) Adjust the variable resistor to obtain the current values shown in table 1. For each of the current values, measure and record the corresponding voltages.

Table 1

I (mA)	10	20	30	40	50	60
V_R (V)						

(6 marks)


- (d) Adjust the potentiometer to $1K\Omega$. Measure and record the current through:

(5 marks)

- (i) R1 _____
- (ii) R2 _____

(e) Plot the graph of voltage against current.

(3 marks)

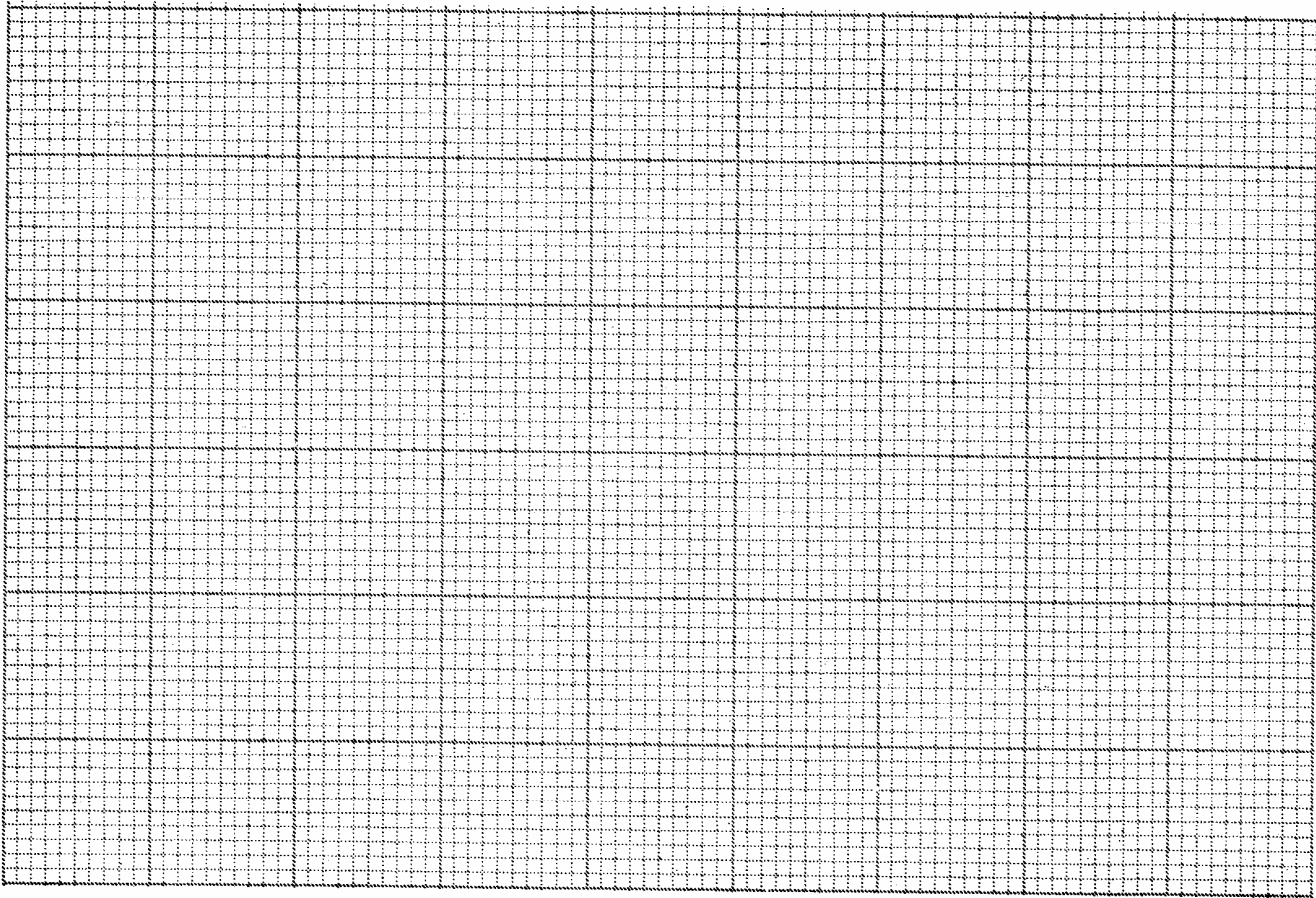

(f) From the graph, determine the voltage when the current is 35mA.

(2 marks)

EXERCISE 2

Using the tools, materials and equipment provided, fabricate the stand as shown in figure 2.
(20 marks)

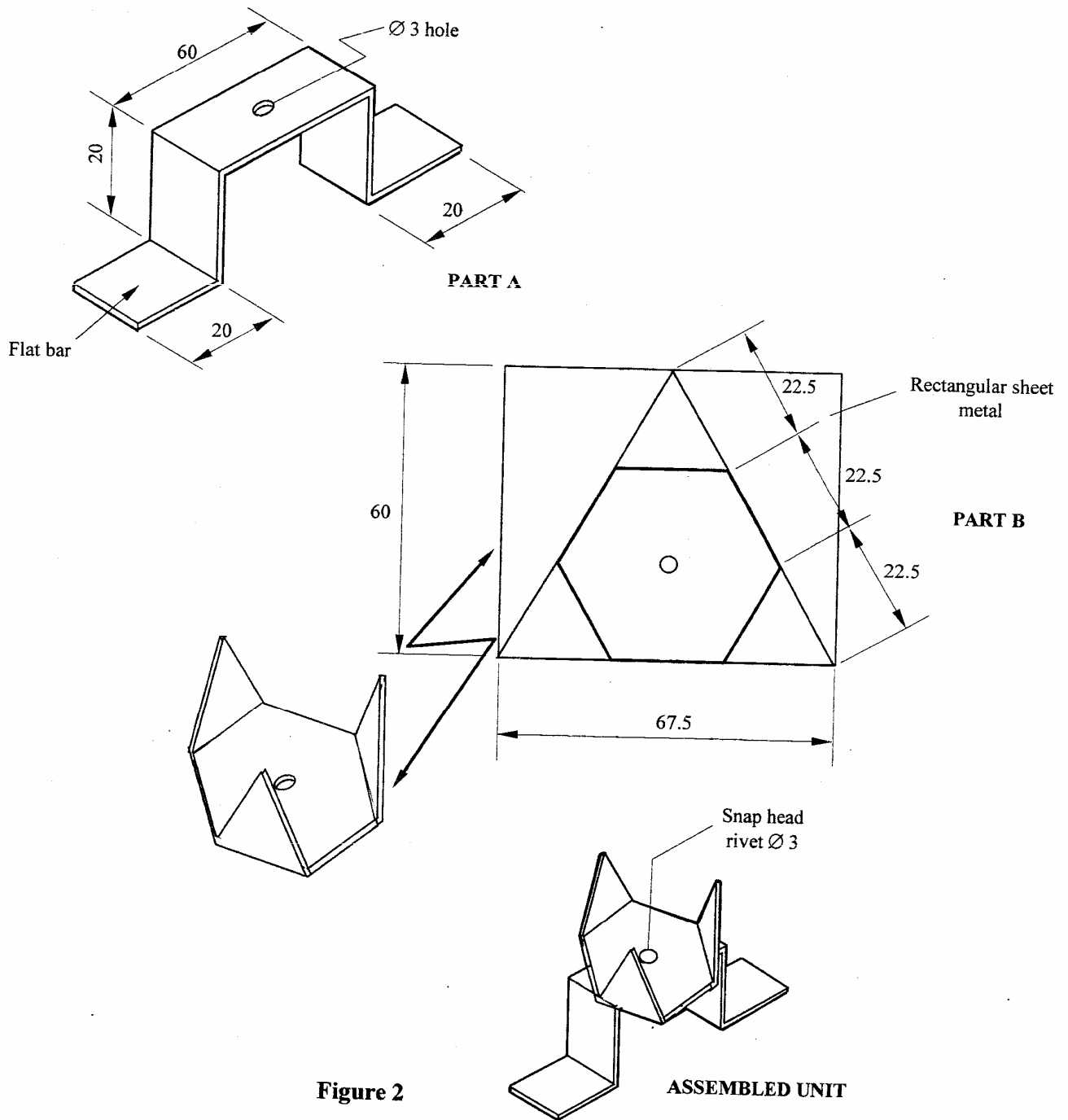


Figure 2

EXERCISE 3

Using the components, materials and equipment provided, carry out the following tasks:

- (a) Connect the circuit as shown in figure 3.

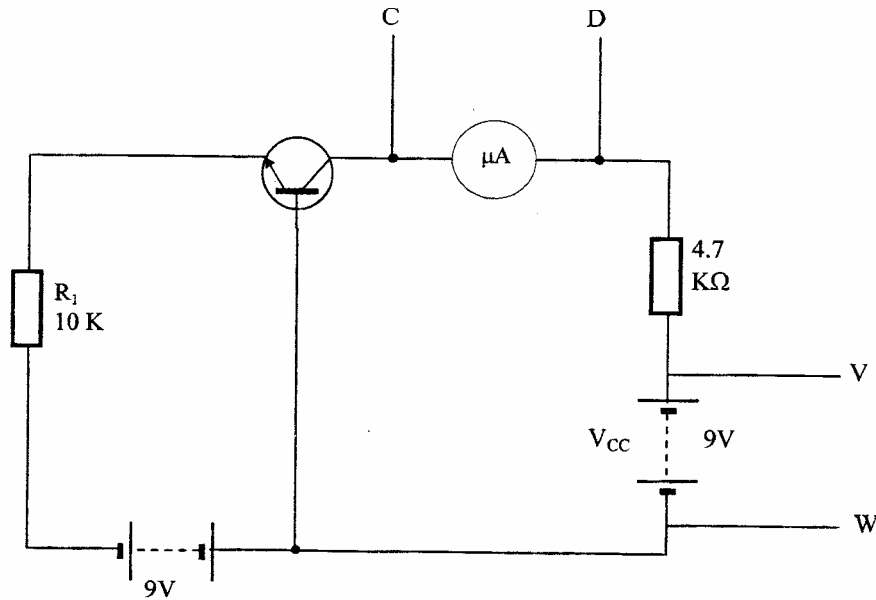


Figure 3

(5 marks)

Let the examiner check your work.

- (b) Adjust V_{cc} to the values shown in table 2 and for each voltage value measure and record the corresponding value of the collector current, I_c

(6 marks)

Table 2

V_{cc} (v)	9	7	5	3	1	0.5
I_c (mA)						

- (c) Repeat step in (b) above for the V_{cc} values shown in table 3 and complete the table.

(3 marks)

Table 3

V_{cc} (v)	10	8	6	4	2	0.5
I_c (mA)						

- (d) From the results obtained in (b) and (c) above, make two comments about the collector current I_c . (4 marks)
- (e) State **two** factors that determine the value of collector current. (2 marks)

EXERCISE 4

Figure 4 shows a block diagram of a prefabricated circuit provided.

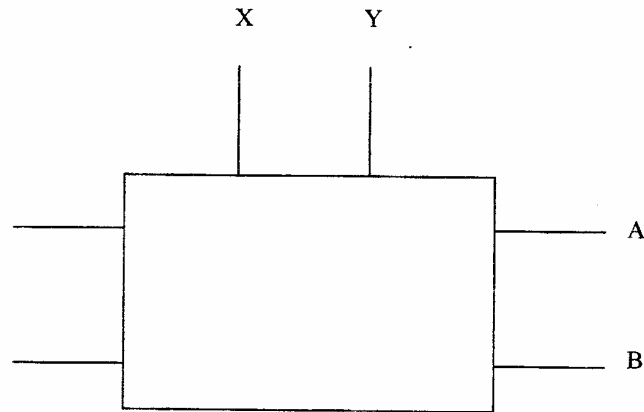


Figure 4

Perform the following tasks:

- (a) Adjust the power supply to 10V. (1 mark)
- (b) Connect the millimeter between points X and Y then connect the circuit to the power supply.
Let the examiner check your work. (1 mark)
- (c) Turn on the power supply.
- (d) Measure and record the following:
- (i) Potential drop across A – B
V =
 - (ii) Voltage across R_s
V =
 - (iii) the circuit current
I =
- (6 marks)

- (e) Increase the power supply to 12v and repeat steps (d) (i) (ii) and (iii) above.
- (i)
- (ii)
- (iii) (6 marks)
- (f) When voltage was increased from 10 to 12 volts, comment on the:
- (i) voltage across R_L ;
- (ii) voltage across R_S ;
- (iii) current through R_S (3 marks)
- (g) State the function of component Q in the circuit. (2 marks)
- (h) Disconnect the circuit and let the examiner check your work. (1 mark)

EXERCISE 5

Figure 5 shows a layout of a final sub-circuit. Using PVC conduit wiring system, install the circuit such that the lamp is controlled from the two switching positions. (15 marks)

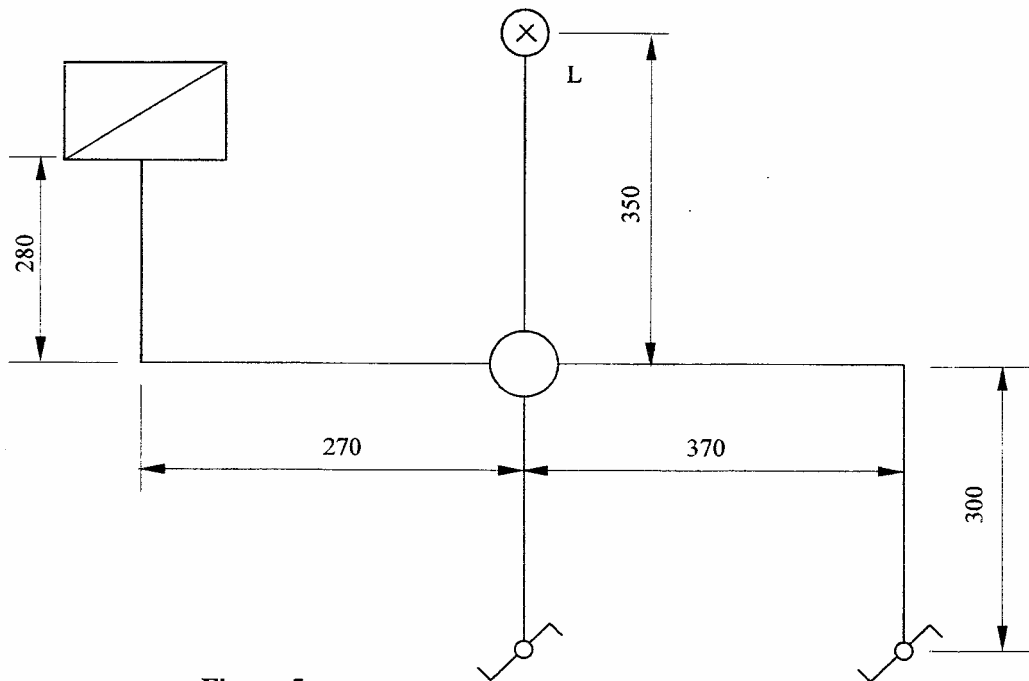


Figure 5

