



KABARAK

UNIVERSITY

UNIVERSITY EXAMINATIONS

2010/2011 ACADEMIC YEAR

FOR THE DEGREE OF BACHELOR OF COMPUTER

SCIENCE

COURSE CODE: PHYS 120

COURSE TITLE: BASIC ELECTRONICS

STREAM: Y1S2

DAY: TUESDAY

TIME: 9.00 – 11.00 A.M

DATE: 14/12/2010

INSTRUCTIONS:

- ❖ Answer question **ONE** and any **THREE** of the remaining
- ❖ Question **ONE** carries **28MARKS** and the remaining carry **14 MARKS** each.
- ❖ Symbols used bear usual meaning.

YOU MAY USE THE FOLLOWING CONSTANTS

Avogadro's number is $N = 6.025 \times 10^{23}$

Electronic charge $q = 1.6 \times 10^{-19} C$

Mass of an electron $m_e = 9.1 \times 10^{-31} Kg$

Boltzmann constant $k = 1.38 \times 10^{-23} J/K$

PLEASE TURNOVER

QUESTION ONE

- a) Write a sentence to define each of the following terms;
- Intrinsic semiconductor
 - Dopant
 - Donor
 - Fermi level (4marks)
- b) Find the mobility of electrons in copper assuming that each atom contributes one free electron for conduction. Resistivity of copper is $1.76 \times 10^{-16} \text{ cm}$ atomic mass of copper is 63.54 density is 8.96 g/cm^3 , (4marks)
- c) For a certain p-n junction, with contact potential $0.065V$, the junction capacitance is $4.5pF$ for $V_s = -10V$ and C_j is $6.5pF$ for $V_s = -2.0V$ find the constant m and zero-biased capacitance (4marks)
- d) Bipolar junction transistors are commonly referred to as “minority carrier” device explain. (2marks)
- e) An important parameter of every amplifier is gain. Explain what ‘gain’ is, and write a simple equation defining gain in terms of signal voltage. (2marks)
- f) List and explain two doping profile junctions. (2marks)
- g) Show that the ripple factor for half-wave rectification and full-wave rectification is 1.21 and 0.48 respectively (4marks)
- h) Cutoff voltage is not the same thing as pinch-off voltage, although the names seem quite similar. Give a concise definition for each of these field-effect transistor parameters, referencing them to a graph of characteristic curves. (2marks)
- i) A very important parameter of operational amplifier performance is slew rate. Describe what ‘slew rate’ is, and why it is important for us to consider in choosing an op-amp for a particular application. (2marks)
- j) What is a decibel? (2marks)

QUESTION TWO

- a) Explain the difference between depletion capacitance and diffusion capacitance in a P-N junction. (2marks)
- b) Briefly discuss critical electric field in relation to the breakdown processes at a P-N junction. (2marks)
- c) An abrupt silicon ($n_i = 10^{10} \text{ cm}^{-3}$) p-n junction at 300K consists of a p-type region containing 10^{16} cm^{-3} acceptors and an n-type region containing $5.0 \times 10^{16} \text{ cm}^{-3}$ donors.
- Calculate the built-in potential of this p-n junction. (2marks)
 - Calculate the total width of the depletion region if the applied voltage is 0.5V . (4marks)
 - Calculate maximum electric field in the depletion region in the n-type semiconductor at 0.5V . (2marks)
 - Calculate the depletion width in the n type region (2marks)

QUESTION THREE

- a) What is quiescent point of a transistor? (2marks)
- b) A bipolar transistor with an emitter current of 1mA has an emitter efficiency of 0.99 , a base transport factor of 0.995 and a depletion layer recombination factor of 0.998 . Calculate;
- The transport factor
 - The current gain of the transistor.
 - The base current, the collector current. (3marks)
- c) Determine the Q point of the transistor circuit shown in Fig.1 also draw the d.c load line. Given $\beta = 200$ and $V_{BE} = 0.7\text{V}$, $V_{BB} = 10\text{V}$, $R_B = 47\text{k}\Omega$, $R_C = 330\Omega$ and $V_{CC} = 20\text{V}$
- What is the operating point if $V_{CC} = 10\text{V}$?
 - What will be the operating point if $R_C = 5\text{k}\Omega$? (6marks)

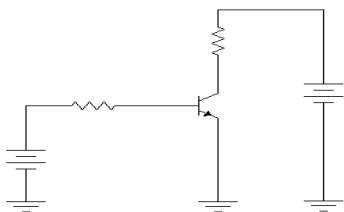


Fig. 1

- d) Discuss the following regions of a bipolar junction transistor.
- Cut off region
 - Active region
 - Saturation region. (3marks)

QUESTION FOUR

- a) Briefly explain the overall operations of the junction field effect transistor. (2marks)
- b) Determine the range of Q-point values for the circuit shown in Fig. 2

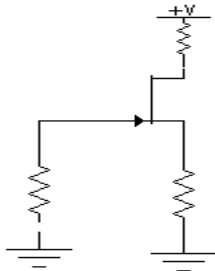


Fig. 2

Given that ;

$$V_{DD} = 10V, R_D = 500\Omega, R_S = 500\Omega, R_G = 1M\Omega$$

$$V_{GS(off)} = -2.0V \text{ to } V_{GS(off)} = -8.0V \text{ and } I_{DSS} = 4.0mA \text{ to } I_{DSS} = 16.0mA$$

(4marks)

- c) What does the term transconductance mean, with reference to a field-effect transistor?
Is the transconductance function for an FET a linear or a nonlinear relationship? Explain why, making reference to an equation if at all possible to explain your answer.

(3marks)

QUESTION FIVE

- a) Define the following terms as used in oscillators;
- Positive feedback
 - Barkhausen criterion
 - Damping
- (3marks)
- b) List the three requirements for proper oscillator operation. (3marks)
- c) Calculate the operating frequency of the following oscillator circuit, if C_2 and $C_3 = 0.005\mu F$ and $L_1 = 80mH$:

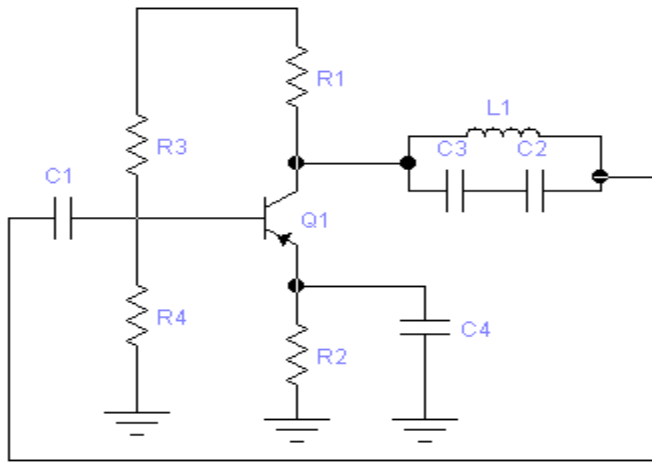


Fig. 4 (5marks)

- d) Write short notes on MOSFET transistors. (3marks)

QUESTION SIX

- a) State the difference between Inverting Amplifiers and Non-Inverting amplifiers. (4marks)
b) Perform the complete analysis of the Non-inverting amplifier shown in Fig. 3

Given the Op-amp parameters

$$A_{CM} = 0.001, A_{OL} = 180000, Z_{in} = 1M\Omega, Z_{out} = 80\Omega(\text{max}), \text{slew rate} = 0.5V/\mu s$$

$$R_{in} = 10K\Omega, R_f = 100K\Omega, R_L = 10K\Omega, \text{the voltage supply is } 1V_{PP}$$

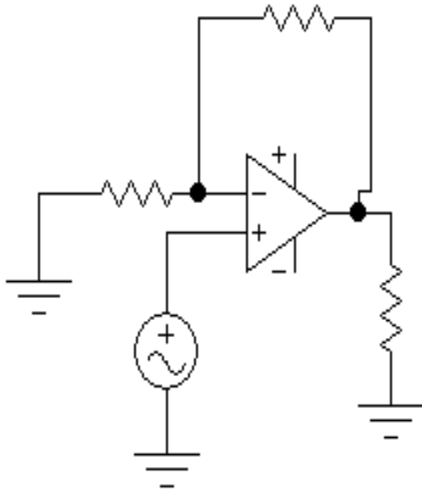


Fig. 3

(8marks)

- c) Discuss the differences between class A and class B amplifiers.

(4marks)