

KABARAK



UNIVERSITY

UNIVERSITY EXAMINATIONS

2009/2010 ACADEMIC YEAR

**FOR THE DEGREE OF BACHELOR OF COMPUTER
SCIENCE**

COURSE CODE: PHYS 120

COURSE TITLE: BASIC ELECTRONICS

STREAM: Y1S2

DAY: THURSDAY

TIME: 9.00 – 11.00 A.M.

DATE: 03/12/2009

INSTRUCTIONS:

Answer **QUESTION 1** and **ANY OTHER TWO**

PLEASE TURN OVER

Question 1 (30 marks)


- (a) Explain the difference in conductivity between metals, conductors and insulators. (3 marks)
- (b) Explain the term band gap as applied in semiconductors. (1 mark)
- (c) Starting with pure silicon material, describe how a n-type semiconductor can be achieved. (4 marks)
- (d) Define the following amplifier terms
- I. Closed loop gain
 - II. Open loop gain
 - III. Loop gain
- (e) Give any THREE differences between a JFET and a BJT. (3 marks)
- (f) I. Sketch the typical drain curves for an n-type JFET for varying V_{gs} . On the curves, mark and explain the Pinch – off voltage (V_p) and the I_{DSS} (7 marks)
- II. Given that $V_p = 5V$ and $I_{DSS} = 10mA$, find the drain – source resistance of the JFET. (2 marks)
- (g) Compare the I/V characteristic curves of a Si and Germanium diodes (4 marks)
- (h) Explain the three main operating regions of a transistor (6 marks)

Question 2 (20 marks)

- (a) Describe the operation of a full-wave rectifier (5 marks)
- (b) Draw and explain the principle operation of a zener diode voltage regulator. (5 marks)
- (c) (i) Explain the formation of the depletion layer in a simple pn junction (2 marks)
- (ii) Give the normal bias conditions of a transistor (2 marks)
- (d) Explain the following methods of making pn junctions
- I. Grown junction
 - II. Alloying

Question 3 (20 marks)

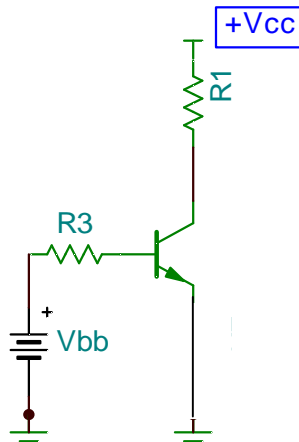- (a) (i) Draw a circuit indicating the normal biasing of an n-type JFET.. (2 marks)
- (ii) Explain how the V_{gs} bias regulates the drain current. (3 marks)
- (b) (i) State THREE factors that the DC transistor gain β_{dc} depends on. (3 marks)
- ((ii) For the circuit shown below, $R_1= 3k$, $R_3= 200k$, $\beta =100$, $V_{BE} = 0.7 V$, $V_{bb}= 5V$ and $V_{CC} = 10 V$.



- (i) Find the transistor currents I_B , I_C and I_E . (7 marks)
- (ii) Determine V_{CB} (2 marks)
- (iii) Draw the load-line and estimate the Q point (3 marks)

Question 4 (20 marks)

- (a) (i) List 5 advantages of negative feedback in amplifiers. (5 marks)
- (ii) Draw a black box representation of an amplifier with feedback, and use the diagram to show that the closed loop gain of an amplifier employing negative feedback is of the form

$$A_0 = \frac{A}{1 + A\beta} \quad \text{where } A \text{ is the open loop gain and } \beta, \text{ the feedback factor.}$$

- (7 marks)
- (b) (i) Draw a labeled block diagram of a shunt - series feedback amplifier. (4 marks)
- (ii) The input to the shunt – series feedback amplifier is 5 mA and the output is 4.5 mA when the feedback network is 10. Find the open loop gain of the amplifier. (4 marks)