

KABARAK



UNIVERSITY

EXAMINATIONS

2008/2009 ACADEMIC YEAR

**FOR THE DEGREE OF BACHELOR OF SCIENCE IN
COMPUTER SCIENCE**

COURSE CODE: PHYS 120

COURSE TITLE: BASIC ELECTRONICS

STREAM: Y1S2

DAY: FRIDAY

TIME: 9.00 – 11.00 A.M

DATE: 27/03/2009

INSTRUCTIONS

Answer QUESTION 1 and ANY OTHER TWO

You may need the following constants:

Electronic charge $e = 1.6 \times 10^{-19} \text{C}$.

$\pi = 3.14$

Boltzmann constant $k = 1.38 \times 10^{-23} \text{ J/K}$

Constant of material for Germanium $\eta_{\text{Ge}} = 1$

1 electron volt $= 1.6 \times 10^{-19} \text{ Joules}$

PLEASE TURN OVER

Question 1 (30 marks)

- (a) Give any FOUR advantages of associated with the use of semiconductor devices over their vacuum based counterparts in electronics industry. (2 marks)
- (b) Explain why increase in temperature leads to increase in conductivity in semiconductors while the opposite happens in metals. (2 marks)
- (c) Explain the term ENERGY GAP as applied in semiconductors. (1 mark)
- (d) Starting with pure silicon material, describe how a p-type semiconductor can be achieved. (3 marks)
- (e) A diode whose threshold voltage is 0.7 V is connected in a circuit with a voltage source of 3 V. Estimate the barrier potential when the diode is
- (I) Reverse biased (1 mark)
- (II) Forward biased (1 mark)
- (f) Determine current I in the circuit below (Fig. 1) if
- (I) the diode is ideal (2 marks)
- (II) $V_{th} = 0.4$ V, diode forward resistance = 20Ω . (2 marks)

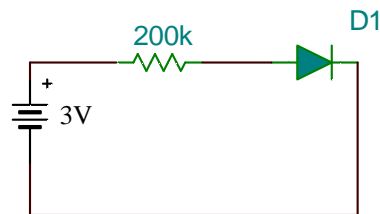


Fig. 1


- (g) State THREE factors that the β_{dc} depends on. (3 marks)
- (h) Draw transistor circuits to illustrate the following bias modes:
- (I) voltage divider bias (2 marks)
- (II) collector feedback bias (2 marks)
- (i) Give any THREE differences between a JFET and a BJT. (3 mks)
- (j) Give FOUR advantages of employing negative feedback schemes in amplifiers. (4 marks)
- (k) Sketch the drain curves for a small signal E-MOSFET. (2 Marks)

Question 2 (20 marks)

- (a) Compare the I/V characteristic curves of a Si and Germanium diodes (5 marks)
- (b) (i) Describe the operation of a bridge rectifier (5 marks)
- (ii) A bridge rectifier uses four identical diodes of forward resistance of 5Ω each. It is supplied from a transformer with an output of 20 V(rms) and secondary winding of 10Ω . Calculate,
- I. the dc load current I_{dc} (2 marks)
- II. Dc output voltage V_{dc} (2 marks)
- (iii) Sketch and explain the output of the rectifier when a filter capacitor is connected across the load. (2, 2 marks)

Question 3 (20 marks)

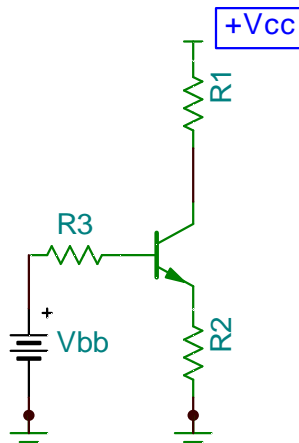- (a) (i) Draw a circuit of an n type E-MOSFET with positive V_{gs} bias. (2 marks)
- (ii) Explain how the V_{gs} bias regulates charge motion in the E-MOSFET. (3 marks)
- (b) (i) State THREE factors that the DC transistor gain β_{dc} depends on. (3 marks)
- ((ii) For the circuit shown below, $R_1= 3k$, $R_2= 500$ Ohms, $R_3= 200k$, $\beta =100$, $V_{BE} = 0.7$ V, $V_{bb}= 5V$ and $V_{CC} = 10$ V.



- (i) Find the transistor currents I_B , I_C and I_E . (7 marks)

- (ii) Determine V_{CB} (2 marks)
- (iii) Draw the load-line and estimate the Q point (3 marks)

Question 4 (20 marks)

- (a) (i) State TWO golden rules which idealize the op-amp behavior. (2 marks)
- (ii) Show that the gain for an inverting amplifier is of the form

$$Gain = \frac{-R_2}{R_1} \quad \text{where } R_1 \text{ and } R_2 \text{ are input and feedback resistors respectively.} \quad (4 \text{ marks})$$

- (iii) Draw a circuit of an op-amp integrator and deduce the voltage output expression in integral form. (6 marks)
- (b) Show that the gain of an amplifier with negative feedback depends only on the intrinsic gain A and the feedback factor β , hence calculate the closed loop gain if $A=100$ and $\beta = 0.1$ (6, 2 marks)