

KABARAK



UNIVERSITY

UNIVERSITY EXAMINATIONS

2010/2011 ACADEMIC YEAR

**FOR THE DEGREE OF BACHELOR OF EDUCATION
SCIENCE**

COURSE CODE: PHYS 120

COURSE TITLE: BASIC ELECTRONICS

STREAM: SESSION III

DAY: MONDAY

TIME: 9.00 – 11.00 A.M.

DATE: 11/04/2011

INSTRUCTIONS:

- *Answer Question ONE and any other TWO Questions. Question One carries 30marks while each of the other Two Questions carry 20marks.*

PLEASE TURN OVER

QUESTION 1 (30 marks)

- a) Define the following terms (4mks)
- Electron shells
 - Valence electrons
 - Ionization
 - Energy gap
- b) Compare the conductivity of semiconductor atom and conductor atom (2mks)
- c) i) Define what is meant by covalent bond. (1mk)
ii) Explain how an n-type semiconductor can be achieved. (3mks)
- d) Explain what is meant by the following. (2mks)
- Barrier potential
 - Depletion layer
- e) i) Explain what is meant by biasing an electronic device. (1mk)
ii) State and explain two biasing techniques used with semiconductor diodes. (3mks)
- f) Differentiate between elemental semiconductors and compound semiconductors. State two examples of each. (4mks)
- g) Differentiate between the following and state one example of each. (3mks)
- Acceptor and donor atoms
 - Extrinsic and intrinsic semiconductors
- h) A potential of 5V is applied across a diode whose barrier potential is 0.7V. If a current of $150\mu\text{A}$ flows through the diode when a $8k\Omega$ limit resistor is used, find the forward dynamic resistance of the diode. (3mks)
- i) Sketch a basic circuit of an operational amplifier differentiator and derive its transfer function. (4mks)

QUESTION 2 (20 marks)

- a) i) Differentiate between half wave and full wave rectification. (2mks)
ii) Draw a circuit diagram of a full wave rectifier and describe how it operates. (5mks)
- b) I) Define the following transistor parameters. (2mks)
- Alpha DC
 - Hybrid (h_{FE})
- II) State and explain the three main operating regions of a transistor. (6mks)
- c) i) Sketch a schematic diagram of an operational amplifier integrator circuit (2mks)


ii) Derive the transfer function of an operational amplifier integrator circuit (3mks)

QUESTION 3 (20 marks)


- a) i) What are field effect transistors. (1mk)
ii) Sketch a circuit diagram showing how junction field effect transistors are biased. (3mks)
iii) The data sheet of a certain JFET indicates that $I_{DSS} = 4mA$ and $V_p = -6V$. Find the drain current for $V_{GS} = -2V$. (4mks)
- b) i) State two special characteristics of operational amplifiers. (2mks)
ii) Sketch a schematic diagram of an inverting operational amplifier and derive its closed-loop gain (A_{vf}). (5mks)
- c) i) What is an oscillator? (1mk)
ii) Sketch a labeled clock pulse output of astable multivibrator. (2mks)
- d) A transistor has the following $V_{CC} = 12V$, $I_B = 50\mu A$, and $\beta = 100$. Sketch its load line. (2mks)

QUESTION 4 (20 marks)

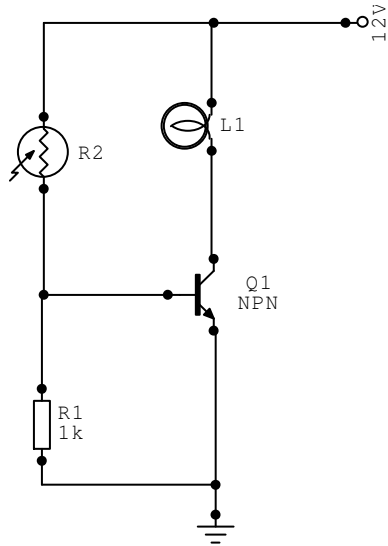- a) Explain why for good conductors, increase in temperature leads to decrease in conductivity while for semiconductors, the opposite is true (2mks)
- b) What is the major difference between?
i). bipolar and unipolar device (2mks)
ii). minority and majority charge carriers (2mks)
- c) Draw a circuit symbol for a semiconductor diode and explain why it acts as a rectifier. (2mks)
- d) Consider the given circuit




- i). Explain how the circuit works (2mks)
 - ii). State one practical use of this circuit (1mk)
- e) i) State and explain two configurations of operational amplifiers. (2mks)
 - ii) Sketch a basic circuit of operational amplifier comparator and explain how it operates. (3mks)
- f) Determine the operating region of the transistor in the given circuit. Given that for this transistor $V_{CE(sat)} = 0.2V$ and $\beta_{DC} = 50$ (4mks)

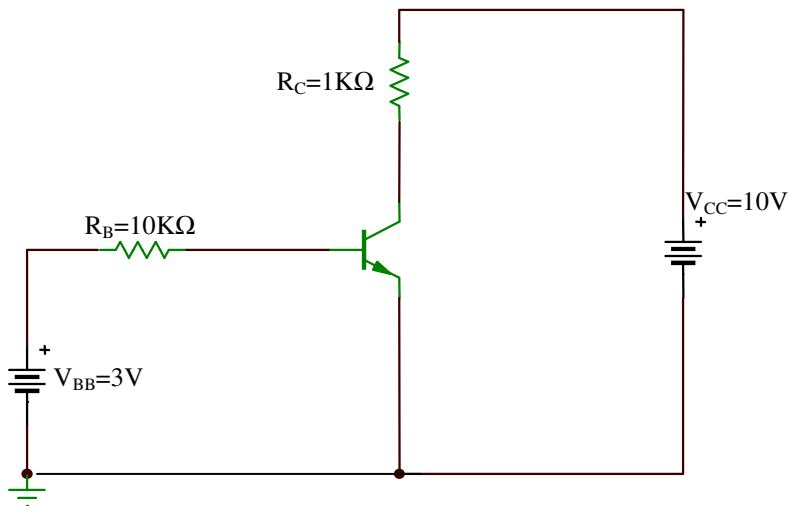

QUESTION 5 (20 marks)

a) Consider the given transistor circuit

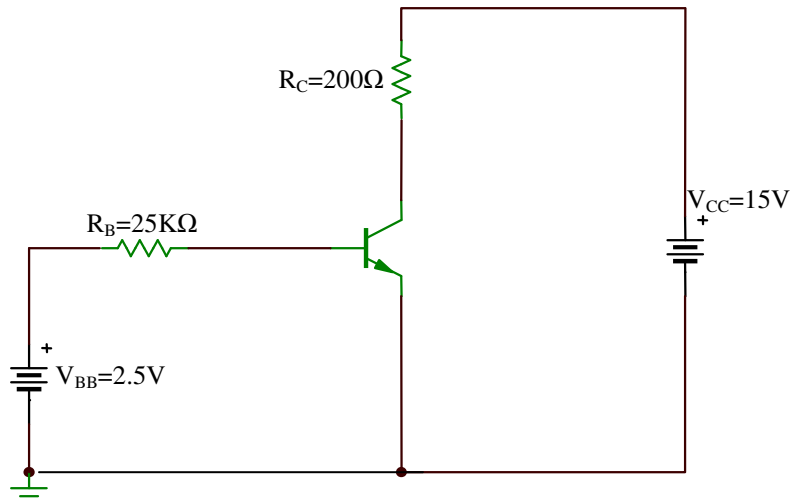

Given that for this transistor, $V_{BE} = 0.7V$ and $\beta_{DC} = 250$, determine for the circuit;

- i). Base current I_B (3mks)
- ii). Collector current (I_C) (3mks)
- iii). Collector-emitter voltage (V_{CE}) (3mks)
- iv). Collector-base voltage (V_{CB}) (2mks)

b) A certain clock oscillator produces an output square wave with $t_{high} = 4\mu s$ and $t_{low} = 6\mu s$. Calculate the clock frequency duty cycle. (4mks)

c) A differentiator has a feedback resistor $R = 25k\Omega$ and input capacitance $C = 0.02\mu F$. Calculate;

- i). It's cut off frequency. (3mks)
- ii). It's maximum linear operating frequency. (2mks)