

**KABARAK**



**UNIVERSITY**

**UNIVERSITY EXAMINATIONS**

**2010/2011 ACADEMIC YEAR**

**FOR THE DEGREE OF BACHELOR OF COMPUTER SCIENCE**

**COURSE CODE: COMP 223**

**COURSE TITLE: DIGITAL CIRCUIT DESIGN**

**STREAM: Y2S2**

**DAY: TUESDAY**

**TIME: 2.00 – 4.00 P.M.**

**DATE: 22/03/2011**

---

**INSTRUCTIONS:**

- *Answer Question **ONE** and any other **TWO** Questions. Question One carries **30marks** while each of the other Two Questions carry **20marks**.*

**PLEASE TURN OVER**

**QUESTION 1 (30 marks)**

- a) i) Perform the following arithmetic (2mks)  
 I)  $102FH + ABCH$  (2mks)  
 II)  $00001000_2 - 00000011_2$  (2mks)  
 ii) Convert  $(3.625)_{10}$  into binary (2mks)
- b) i) State De-Morgan's theorem of two variables (2mks)  
 ii) Write a simplified logic expression for the given logic K-maps (6mks)

AB					
		1	1		1
CD					
	1	1		1	
	1	1		1	
	1	1		1	

AB					
		1	1	1	1
C			1	1	

- c) i) Draw circuit symbol of NAND gate. (1mk)  
 ii) Show using diagrams how you can use a NAND gate to implement an AND function and an OR function (4mks)
- d) i) What is a truth table? (1mk)  
 ii) State two uses of truth tables (2mks)  
 iii) Negate the given logic function (2mks)

$$X \cdot \bar{Y} + \bar{X} \cdot Y$$

- e) In a chemical processing plant, a liquid chemical is used in a manufacturing process. The chemical is stored in three different tanks. A level sensor in each tank produces a HIGH voltage when the level of chemical in the tank drops below a specified fixed point. Design a circuit that monitors the chemical level in each tank and indicates when the level in any two of the tanks drops below the specified point (3mks)

f) Draw a combinational circuit to implement the given logic function (3mks)

$$W = XY(Z + Y) + X \oplus Z$$

**QUESTION 2 (20 marks)**

a) i) Draw a logic symbol of a NOR gate (1mk)

ii) Manipulate the given logic function into a form which can be implemented using NOR gates only (5mks)

$$Y = \bar{A}\bar{B}\bar{C} + AC + \bar{B}$$


iii) Draw the logic diagram of the resulting manipulated function in (ii) above (3mks)

b) Simplify the following logic expressions and draw the logic circuits for the simplified functions.

i)  $W = X.Y + \bar{X}.Y + \bar{X}.\bar{Y}$  (2mks)

ii)  $Y = \overline{(\bar{A} + C)} \cdot \overline{(B + \bar{D})}$  (2mks)

c) Consider the given circuit.

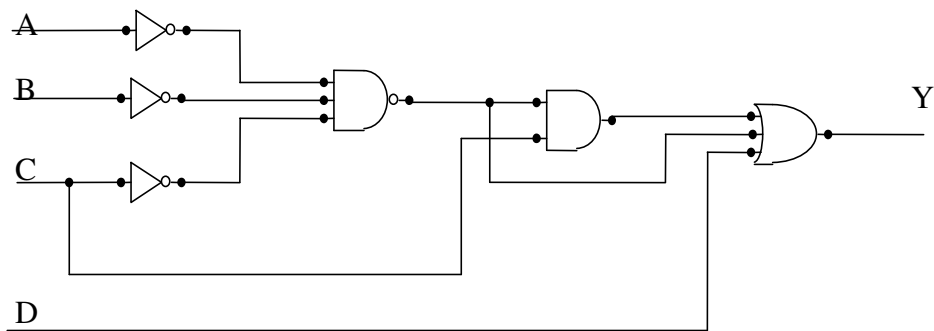

i). obtained the unsimplified output logic expression for the above circuit. (3mks)

ii). Using De-Morgan's and Boolean theorem's, simplify the output logic expression in (i). (3mks)

iii). Draw a logic circuit of the simplified function in (ii). (1mk)

**QUESTION 3 (20 marks)**

- a) i) Design and draw a two bit comparator circuit that will produce a logic 1 output when the two input signals are identical. (3mks)  
 ii) Manipulate the output logic expression of the two bits circuit in (i) into a form which can be implemented using NAND gates only. (2mks)  
 iii) Draw the circuit diagram of the manipulated function in (ii) (2mks)

- b) i) Prepare K-map for the given function (6mks)

$$I) W = \bar{A}\bar{B}CD + ABCD + A\bar{B}D + \bar{A}CD + \bar{A}C\bar{D}$$

$$II) Y = B + AC$$

- ii) Use the prepared K-map to simplify the function (I) and write down the simplified logic function (2mks)

- c) Explain the following logic circuits

- i) Sequential logic circuit (1mks)  
 ii) Combinational logic circuit (1mks)

- d) State and explain two classifications of sequential logic circuits (3mks)

**QUESTION 4 (20 marks)**


- a) Differentiate between the following (4mks)

- i). Programmable logic devices and fixed logic devices  
 ii). Finite state machines and algorithmic state machines.

- b) i) What is a counter? (1mk)  
 ii) State two uses of counters (2mks)  
 iii) Draw a 4-bit ripple digital counter. (4mks)  
 iv) State two advantages of synchronous counters (2mks)

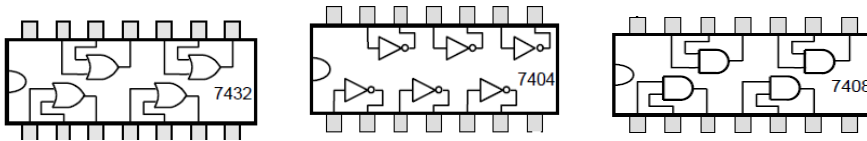- c) Connect the chips provided below to implement

$W = (\overline{X + Y})(Z + Y)$ , given that pin 7 and 14 on each IC represent GND and +V<sub>ss</sub> respectively. (5mks)




- d) State two uses of shift register (2mks)

**QUESTION 5 (20 marks)**

- a) Define the following terms as used with sequential circuits (4mks)
- Clock duty cycle
  - State diagrams
  - State tables
  - Clock width

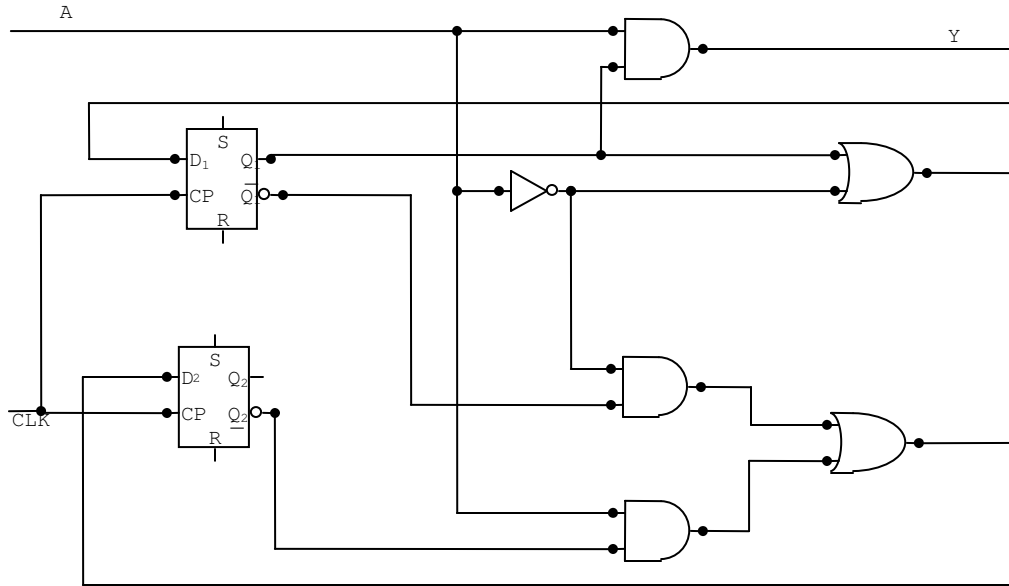b) Consider the following sequential circuit



The circuit has one input A, one output Y and two state variables  $Q_1$  and  $Q_2$

- Write the Boolean expressions which can be used to determine the behavior of the circuit (3mks)
  - From the Boolean expressions in (i), develop the state table for this circuit. (4mks)
  - Use the state table to develop the state diagram for this circuit. (4mks)
- c) i) What is a programmable array? (1mk)  
 ii) Draw a programmable array which can give (4mks)

$$W_1 = \bar{A} + B, W_2 = \bar{A} + \bar{B}, W_3 = A + \bar{B}, W_4 = A + B$$