

**KABARAK**



**UNIVERSITY**

**UNIVERSITY EXAMINATIONS**

**2009/2010 ACADEMIC YEAR**

**FOR THE DEGREE OF BACHELOR OF COMPUTER SCIENCE**

**COURSE CODE: COMP 223**

**COURSE TITLE: DIGITAL CIRCUIT DESIGN**

**STREAM: Y2S2**

**DAY: WEDNESDAY**

**TIME: 9.00 – 11.00 A.M.**

**DATE: 11/08/2010**

---

**INSTRUCTIONS:**


*Answer Question ONE and ANY other TWO*

**PLEASE TURNOVER**

**QUESTION 1 (30 MARKS)**

- a) Explain the following logics  
 i) Sequential logic (2 marks)  
 ii) Combinational logic (2 marks)

b) Consider a data latch below:

 


State the status of Q if

- i)  $Preset' = 0$  (1 mark)  
 ii)  $Clear' = 0$  (1 mark)
- c) State ANY two common uses of a register. (2 marks)
- d) i) Draw a diagram of a series-in series-out shift register employing four D latches. (3 marks)  
 ii) Complete the table below for a shift register. (3 marks)

	In	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>	Q <sub>4</sub>
t <sub>0</sub>	1				
t <sub>1</sub>	0	1			
t <sub>2</sub>	1		1		
t <sub>3</sub>	1	1		1	
t <sub>4</sub>	0	1	1		1
t <sub>5</sub>	0		1	1	

 - f) Simplify the following expressions and draw the simplified logic circuit.
- i)  $Y = \overline{A}BC\overline{D} + \overline{A}\overline{B}C\overline{D}$  (3 marks)  
 ii)  $Y = \overline{(\overline{A} + C)} \cdot (B + \overline{D})$  (3 marks)
- g) Determine the output of the following logic circuits:




(4 marks)

- h) i) State the function of a MUX. (1 mark)
- ii) Draw a functional diagram of a 2-input MUX and deduce its output expression. (3 marks)
- iii) List two applications of a MUX (2 marks)

**QUESTION 2 (20 MARKS)**

 
- a) List TWO problems encountered with asynchronous counters (2 marks)
- b) List THREE differences between the asynchronous and synchronous counters. (3 marks)
- c) Draw a synchronous (parallel) counter and explain its operation. (10 marks)
- d) Connect the chips provided below to implement  $f=ab+b'c$  given pin 7 and 14 on each IC represent GND and  $+V_{DD}$  respectively. (5 marks)



**QUESTION 3 (20 MARKS)**

- a) Given the numbers, decimal 227 and binary 1101101, convert both numbers to decimal, binary, hexadecimal and BCD equivalents where applicable. (8 marks)
- b) i) With the use of logic gates, draw a logic circuit of a JK flip flop. (3 marks)
- ii) Present the truth table of a JK flip flop. (5 marks)

 - iii) Complete the following timing diagram of a NGT JK latch (3 marks)



- iv) State one advantage of JK over SR latch (1 mark)

**QUESTION 4 (20 MARKS)**

- a) Design a counter that counts from 0 to 9 using JK flip-flops that respond to NGT of the clock. Use additional logic to generate an output Z which activates an LED when a count of 5 or 7 is attained. (8 marks)
- b) i) Draw a block diagram of a full adder. (2 marks)
- ii) Give the truth table of the full adder using three inputs A, B and Cin (Carry-in) and the outputs Sum and carry-out. (4 marks)
- iii) Derive the expressions for sum and carry-out based on the truth table; hence draw a logic diagram for the full adder. (6 marks)