

KABARAK



UNIVERSITY

UNIVERSITY EXAMINATIONS

2009/2010 ACADEMIC YEAR

**FOR THE DEGREE OF BACHELOR OF SCIENCE IN
EDUCATION SCIENCE**

COURSE CODE: PHYS 420

COURSE TITLE: DIGITAL ELECTRONICS

STREAM: SESSION VII & VIII

DAY: SATURDAY

TIME: 2.00 – 4.00 P.M.

DATE: 28/11/2009

INSTRUCTIONS:

ANSWER QUESTION ONE AND ANY OTHER TWO QUESTIONS.

PLEASE TURN OVER

QUESTION 1 (24 marks)

- (a) Using only two-input NOR gates, show how a NAND gate can be made. (2marks)
 (b) The circuits in fig. 1 are a D-latch and a D-flip-flop. Complete the timing diagram by drawing the waveforms of X and Y assuming that they are both low initially. (2marks)

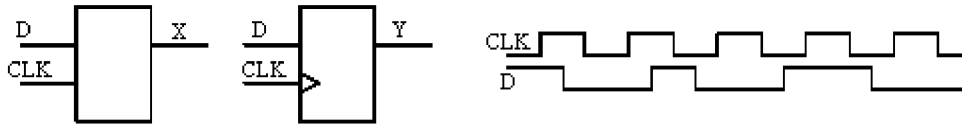


Fig. 1

- (c) Given a logic function

$$f = A \cdot B \cdot C \cdot D + A \cdot D + B \cdot C \cdot D + A \cdot B \cdot C \cdot D + A \cdot B \cdot D$$

- (i) Draw a Karnaugh map for f and write simplified function of f (3marks)
 (ii) Design a NAND-only circuit to implement f. (2marks)
 (iii) Design a NOR-only circuit to implement f. (2marks)
- (d)
- (i) Determine the maximum conversion time of an 8-bit ADC with a 2-MHz clock, if the ADC is of a staircase ramp type. (1mark)
 (ii) Determine the percentage resolution of a 12-bit BCD DAC. (1mark)
- (e)
- i. Represent the function as a sum of product form from the pattern in a Karnaugh map below. (1 mark)
 ii. Using Boolean algebra to simplify the logic expression in (i) and give the name of the gate. (1 mark)


A,B		0		1	
		0	1	0	1
C	0	0	1	0	1
	1	1	0	1	0

- (f) Differentiate between Combinational and sequential circuits (3 marks)
 (g) Describe how a 2-to-1 MUX functions (6 marks)

QUESTION 2 (12 marks)

- (a) If the 3-bit binary number A B C represents the digits 0 to 7:
 (i) Make a truth table for A, B, C and Q, where Q is true only when an odd number of bits are true in the number.
 (ii) Write a statement in Boolean algebra for Q.
 (iii) Convert this equation to one that can be mechanized using only two XOR gates. Draw the resulting circuit.

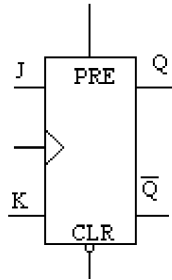- (b) Show how gated-SR flip-flop can be modified to operate as a D flip-flop and draw the truth table for D flip-flop. (2marks)
- (c) Design a modulo-7 asynchronous counter using JK flip-flops and sketch the counter circuit. The JK flip-flop is as shown below. (3marks)



- (d) Modify the counter circuit in (c) above, so that the counter can be used as an electronic dice, i.e. counting, 1, 2, 6 rather than 0, 1, 2....6. (2marks)

QUESTION 3 (12 marks)

- (a) With show of diagrams explain how adder-subtractor functions (10 marks)
- (b) Differentiate between asynchronous and synchronous systems. (2 marks)

QUESTION 4 (12 marks)

With show of diagrams explain how XOR-gates can be used as :

- i. A controlled inverter. (4 marks)
- ii. A parity generator and checker. (8 marks)

QUESTION 5 (12 marks)

- (a) Show how four D type flip-flops can be connected to form a shift register where data be rotated in, and explain how it functions. (6marks)
- (b) A 3-bit binary number is represented as $A_2 A_1 A_0$, where A_0 is the LSB. Design a logic circuit which will produce a HIGH output whenever the binary number is either 1, 2, 4 or 7. Implement the circuit using :
- (i) a 1 to 8 MUX . (3marks)
- (ii) a 1 to 4 MUX. (3marks)

QUESTION 06 (12 marks)

With show of diagrams explain how a full adder can be developed out of two half-adders.

(12 marks)

(a) Why is the above scheme impractical for implementing a 12-bit D/A converter circuit?

(1mark)

(b) Why is a sample-and-hold amplifier usually used with an A/D converter?

(3mark)