

**KABARAK**



**UNIVERSITY**

**UNIVERSITY EXAMINATIONS**

**2010/2011 ACADEMIC YEAR**

**FOR THE DEGREE OF BACHELOR OF TELECOMMUNICATION**

**COURSE CODE: PHYS 126**

**COURSE TITLE: ELECTRICITY AND ELECTRONIC  
SYSTEMS**

**STREAM: Y1S2**

**DAY: TUESDAY**

**TIME: 9.00 – 12.00 P.M.**

**DATE: 22/03/2011**

---


**INSTRUCTIONS:**

- *Answer Question **ONE** and any other **THREE** Questions. Question One carries **20marks** while each of the other Three Questions carry **10marks**.*
- *The following constants may be useful*
  - Permeability of free space  $\mu_0 = 4\pi \times 10^{-7} \text{ Wb / A}$
  - Permittivity of free space  $\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2 / \text{NM}^2$
  - Resistivity of Steel  $\rho = 1.6 \times 10^{-8} \Omega \text{m}$

**PLEASE TURN OVER**

**QUESTION 1 (20 marks)**

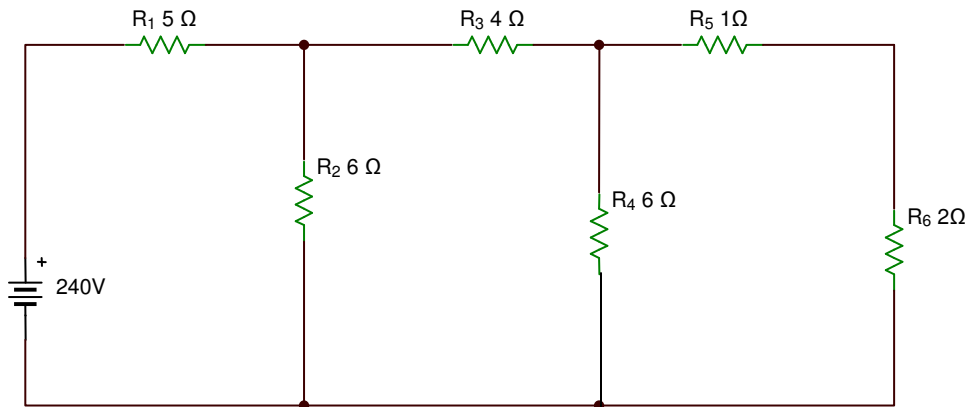- a) Define the following terms (2mks)
- i). Electric current
  - ii). Resistance
- b) i) State and explain any two factors that affect the resistance of a metallic conductor. (2mks)
- ii) A rectangular block of Steel has dimensions 2.5cm by 2.5cm by 40cm. Find the conductance of the block between the two square ends. (2mks)
- c) A charge of 240C is moved when energy of 45J is applied between two points. Find the voltage between the two points. (2mks)
- e) Sketch a circuit diagram showing how a.c. full wave rectification can be achieved using a bridge rectifier (2mks)
- f) Explain why for good conductors, increase in temperature leads to decrease in conductivity while for semiconductors, the opposite is true (1mk)
- g) i) State Kirchhoff's current law. (1mk)
- ii) Determine the voltage across  $R_6$  in the given circuit (3mks)




- e) Differentiate between extrinsic and intrinsic semiconductors (1mk)
- f) i) Differentiate between poles and zeros of a system. (1mk)
- ii) A linear system is described by

$$\frac{d^2 y}{dt^2} + 5 \frac{dy}{dt} + 6y = 2 \frac{du}{dt} + u$$

Find the system poles and zeros (3mks)

**QUESTION 2 (10 marks)**

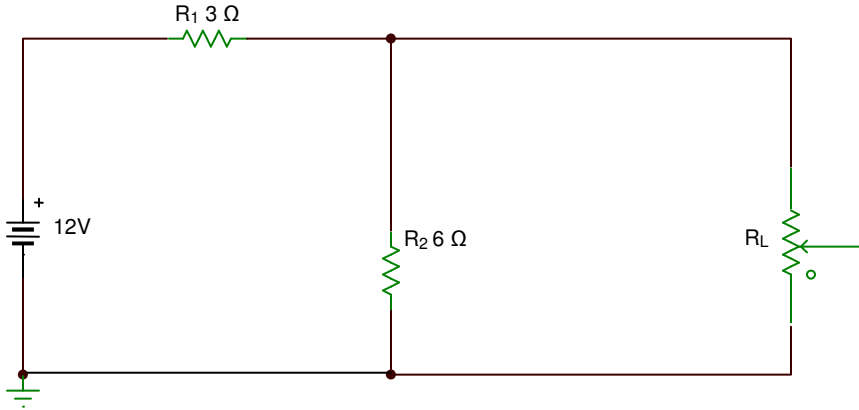- a) i) State Thevenin's theorem (1mk)  
ii) Find the Thevenin equivalent circuit for the given network, hence find the current through  $R_L$  for  $R_L = 10\Omega$  (4mks)




- b) State maximum power transfer theorem and hence show that  $P_{L_{max}} = \frac{E_{Th}^2}{4R_{Th}}$  (5mks)

**QUESTION 3 (10 marks)**

- a) i) What is capacitance? (1mk)  
ii) A potential difference of 4KV is applied across the plates of a capacitor of capacitance  $25\mu F$ . Calculate the charge in the capacitor. (2mks)
- b) i) Define transient period of an RC circuit (1mk)  
ii) Derive the expression of finding the current (I) at any time (t) of a capacitor during the transient growth, hence show that time constant ( $\tau$ ) during this phase is 63% of maximum value. (6mks)

**QUESTION 4 (10 marks)**

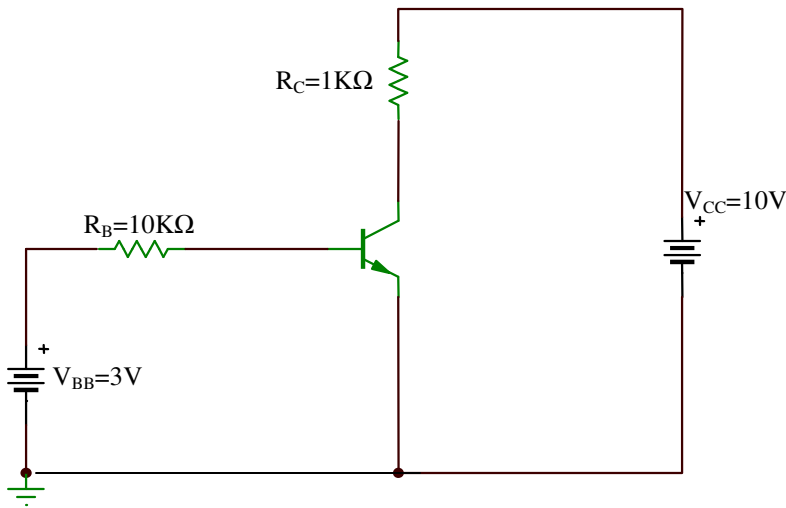- a) Determine the operating region of the transistor in the given circuit. Given that for this transistor  $V_{CE(sat)} = 0.2V$ ,  $V_{BE} = 0.7V$  and  $\beta_{DC} = 50$  (4mks)



- b) Sketch a schematic diagram of an inverting operational amplifier and derive its closed-loop gain (A). (3mks)
- c) Derive the transfer function of an operational amplifier integrator circuit (3mks)

**QUESTION 5 (10 marks)**

- a) A series RLC circuit is driven by an a.c of the form  $V = V_{\max} \sin \omega t$ . Given that  $R=250\Omega$ ,  $L= 0.8\text{mH}$ ,  $C= 2.5\mu\text{F}$ ,  $f= 50\text{Hz}$  and  $V_{\max}=200\text{V}$ . Find for this circuit
- i). The amplitude current (3mks)
  - ii). The phase angle (2mks)
- b) Define quality (Q) factor of a series RLC circuit and show that the Q-factor for series RLC circuit is given by

$$Q_s = \frac{1}{R} \sqrt{\frac{L}{C}} \quad (3\text{mks})$$

- c) Define resonance frequency of a series RLC circuit and show that this frequency is given by

$$\omega = \frac{1}{\sqrt{LC}} \quad (2\text{mks})$$