

**KABARAK**



**UNIVERSITY**

**UNIVERSITY EXAMINATIONS**

**2009/2010 ACADEMIC YEAR**

**FOR THE DEGREE OF BACHELOR OF SCIENCE IN  
EDUCATION SCIENCE**

**COURSE CODE: PHYS 422**

**COURSE TITLE: SEMICONDUCTOR DEVICES**

**STREAM: SESSION VIII**

**DAY: SATURDAY**

**TIME: 2.00 – 4.00 P.M.**

**DATE: 28/11/2009**

---

**INSTRUCTIONS:**

Answer **QUESTION 1** and **ANY OTHER TWO**

**PLEASE TURN OVER**

### QUESTION 1

- (a) Define the following terms:-
- (i) *Recombination* process. (1mark)
  - (ii) *Lifetime* of electron- hole-pair. (1mark)
- (b) Differentiate between extrinsic and intrinsic semiconductors. (2 marks)
- (c) Name the three modes of operation of the bipolar transistor and give the biasing conditions of each. (6 marks)
- (d) Explain the **four** important properties of the FETs. (8 marks)
- (e) Give three reasons why Si and Ge have advantage over other elements in the development of semiconductor devices. (4 marks)
- (f) Why is the ripple factor of a power supply an important specification? (2 marks)

### QUESTION 2

- (a) By show of diagrams describe positive and negative clipper circuits. (6marks)
- (b) A certain P-N junction has a leakage current of  $10^{-14}$  A at room temperature of  $27^\circ\text{C}$  and  $10^{-9}$  A at  $125^\circ\text{C}$ . The diode is forward biased with a constant-current source of 1 mA at room temperature. If the current is assumed to be constant, calculate the junction barrier voltage at room temperature and at  $125^\circ\text{C}$ . (6 marks)

### QUESTION 3

- (a) Determine the quiescent operating point for the circuit of fig. 2 and the sketch the loadline. (7marks)

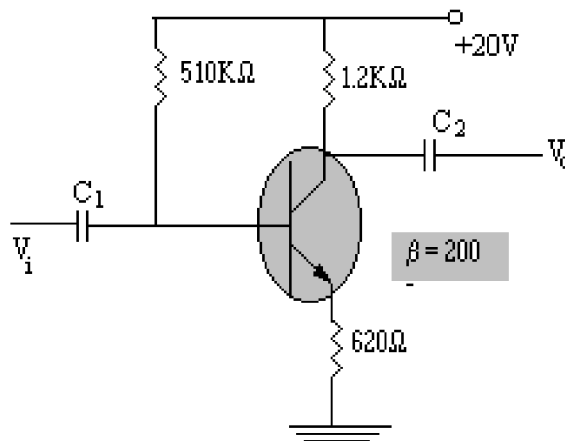


Fig. 2

- (b) Show that the stability factor is given by  $S = \frac{(1 + \beta)}{(1 - \beta) \frac{\Delta I_B}{\Delta I_C}}$  (5 marks)

**QUESTION 4**

- (a) Differentiate between the *enhancement mode* MOSFET and *depletion mode* MOSFET. (2marks)
- (b) Design a self-bias circuit such as to operate a JFET 2N5952. Use a 22-V supply and bias the device at  $I_D = 5\text{mA}$ ,  $V_{DS} = 15\text{V}$ .

The spec. sheet for the 2N5952 shows

$$I_{GSS} = 200\text{nA}$$

$$I_{DSS} = 4\text{mA to } 8\text{mA ( use } I_{DSS} = 6\text{mA)}$$

$$V_{GS(off)} = -1.3\text{V to } -3.5\text{V ( use } V_P = -2.5\text{V)}$$
 (8marks)

- (c) Calculate the stability factor of the circuit in fig. 3. (2 marks)

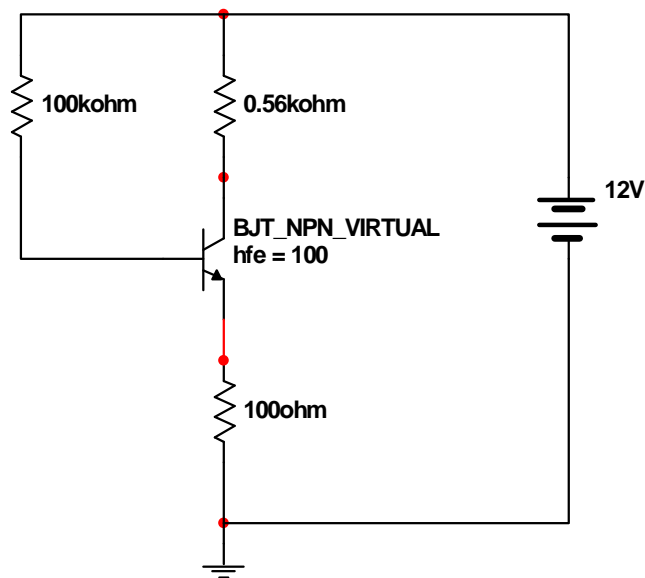


Fig. 3

**QUESTION 5**

- (a) Design a common emitter bias circuit that will conform to the following specifications:

Supply voltage =  $12V_{DC}$ ,  $\beta = 400$ ,  $I_{CQ} = 22\text{mA}$  (6 marks)

- (b) If the input voltage of the power supply shown in fig. 4 is  $20 V_{ac}$  and the load resistance is  $1 K\Omega$ . Calculate the size of the smoothing capacitor needed, in order for the load voltage to be  $25 V_{DC}$ . (6 marks)

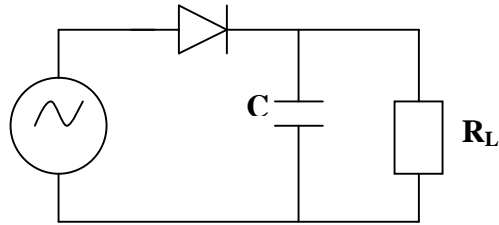


Fig. 4

**QUESTION 6**

- (a) Describe thermal runaway and how it is prevented. (12 marks)