



# UNIVERSITY OF NAIROBI

SECOND SEMESTER EXAMINATIONS 2007/2008

THIRD YEAR EXAMINATIONS FOR THE DEGREE OF BACHELOR OF SCIENCE IN  
ELECTRICAL & ELECTRONIC ENGINEERING

FEE 322: ELECTRICAL CIRCUIT THEORY II B

DATE: 22<sup>ND</sup> JULY, 2008

TIME: 11.15 A.M. – 01.15 P.M.


### INSTRUCTIONS

1. Attempt **ONE** question from **EACH** of the **THREE** sections
2. All questions carry equal marks
3. Smith Charts are provided

### SECTION A: TWO-PORT NETWORKS

#### QUESTION ONE: (20 MARKS)

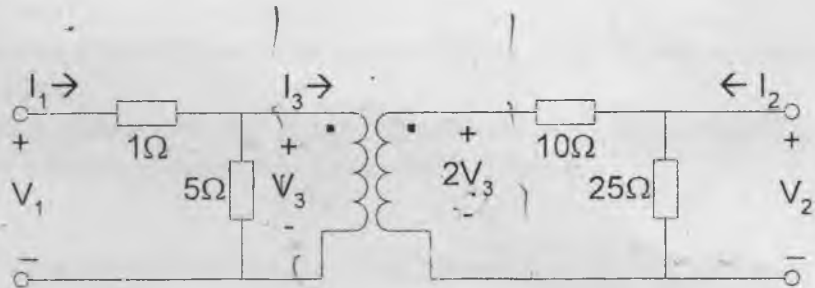- (i) Give the defining equations for the transmission (ABCD) parameters.
- (ii) For two networks connected in cascade, derive the expression for the overall ABCD parameters in terms of the ABCD parameters of the individual networks.
- (iii) Obtain the ABCD parameters for the circuit of Fig.Q1(a)
- (iv) Determine the open circuit voltage gain of the circuit



[8 marks]

Fig. Q1(a)

- (i) Explain what is meant by 'image impedance' as applies to two-port networks.
- (ii) Determine the values of the image impedances of the network in Fig.Q1(a).
- (iii) Determine the propagation function of the network in Fig.Q1(a)

$$Z_{i1} = \sqrt{\frac{AB}{CD}}, \quad Z_{i2} = \sqrt{\frac{BD}{AC}}$$

$$\Gamma_{\theta} = \frac{1}{2} \ln \left( \frac{\sqrt{AD} + \sqrt{BC}}{\sqrt{AD} - \sqrt{BC}} \right)$$

[6 marks]

- (c) (i) Give the defining equations for the *z-parameters* of a two port network.  
 (ii) Obtain the expressions for the *z-parameters* in terms of the ABCD parameters  
 (iii) Using the result in (ii) obtain the equivalent *T-network* for the network in Fig.Q1(a) [6 marks]

**QUESTION TWO: (20 MARKS)**

- (a) (i) Derive the expressions for the *z-parameters* in terms of the *h-parameters*.  
 (ii) Convert the network of Fig.Q2(a) into the equivalent *T-network*.  
 (iii) Determine the *z-parameters* of the network.  
 (iv) Determine the characteristic impedance of the network.  $Z_0 = \sqrt{Z_{11}^2 - Z_{12}^2}$  [8 marks]

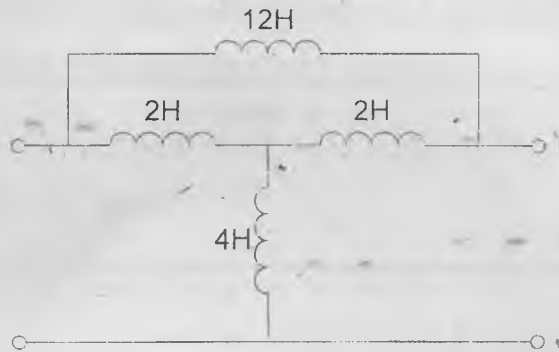


Fig. Q2(a)

- (b) (i) With the help of diagrams, show how termination on *image basis* differs from termination on *iterative basis* for a two-port network.  
 (ii) Show that the characteristic impedance of a symmetrical lattice network is given by  $\sqrt{Z_A Z_B}$ , where  $Z_A$  and  $Z_B$  are the series and diagonal arm impedances respectively  
 (iii) By converting the network of Fig. Q2(b) into a lattice network determine its characteristic impedance at  $\omega = 0.4$  radians. [8 marks]

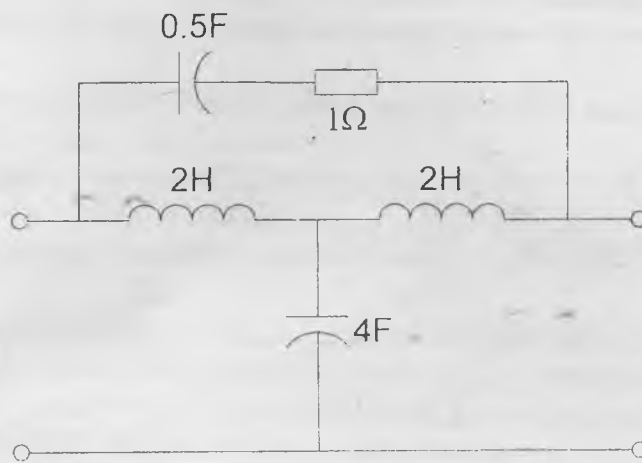


Fig. Q2(b)

- (c) Using a purely resistive symmetrical lattice network, design a *symmetrical π-type attenuator* having a characteristic impedance of  $100\Omega$  and an attenuation of 20 nepers. [4 marks]

SECTION B: ONE-PORT NETWORK SYNTHESIS

**QUESTION THREE: (20 MARKS)**

- (a) (i) Give the four properties that must be true for the driving point impedance functions for any non-dissipative network that is physically realizable.  
 (ii) Indicate which of the four are true for even dissipative networks.  
 (iii) State the separation property of reactive networks and explain its significance

[4 marks]

(b) For the circuit of Fig.Q3(b) determine

- (i) the driving point impedance of the network as a quotient of polynomials  
 (ii) a sketch of the reactance function  $X(j\omega)$   
 (iii) the second Cauey form of the equivalent network, indicating all the component values

[8 marks]

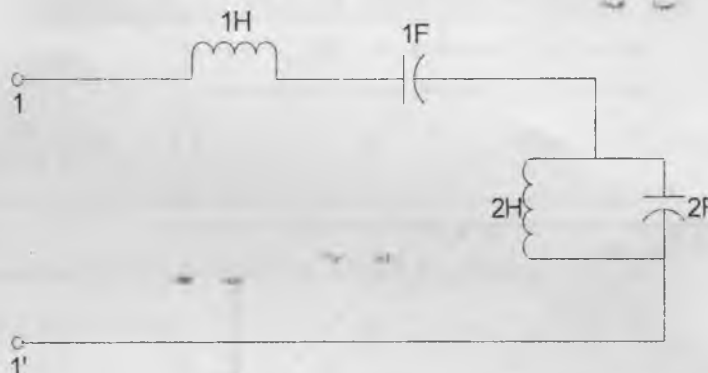


Fig. Q3(b)

- (c) A certain network's driving point admittance function has poles at  $s = -2$  and  $-6$  and zeros at  $s = 0, -4$  and  $-8$ . At  $s = -3$ , the admittance is  $1\text{mho}$ . Determine  
 (i) the quotient expression in  $s$  for the admittance function  
 (ii) the second Foster network, indicating all component values  
 (iii) the first Cauey network, indicating all the component values

[8 marks]

**QUESTION FOUR: (20 MARKS)**

- (a) (i) Give the factored form of the general driving point impedance expression in  $s$  for R-C networks.  
 (ii) Show a general pole-zero plot for the networks in (i), indicating any assumptions.  
 (iii) Give a sketch of a **complete** first Foster R-C network

[4 marks]

(b) For the driving point impedance function  $Z_D(s) = \frac{2s^2 + 8s + 6}{3s^2 + 18s + 24}$  determine

- (i) the first Foster network, indicating all component values  
 (ii) the second Cauey network, indicating all the component values

[8 marks]

(c) For the driving point impedance  $Z_D(s) = \frac{10s^4 + 12s^2 + 1}{2s^3 + 2s}$  determine

- (i) all the external and internal poles and zeros  
 (ii) the frequency pattern (pole-zero plot)  
 (iii) the second Foster form of the network, indicating all the component values

[8 marks]

SECTION C: TRANSMISSION LINES

QUESTION FIVE: (20 MARKS)

- (a) (i) Explain the advantage of double stub matching over single stub matching.
- (ii) Show that the impedance of a short circuit stub of a lossless line is pure reactance.
- (iii) Determine the range of the shortest lengths of an open circuit stub that result in inductive reactance.

[5 marks]

- (b) The layout for a double-stub tuner is shown in Figure Q4 below. Determine
  - (i) the required length  $l_1$  of the short circuit stub S1
  - (ii) the required length  $l_2$  of the open circuit stub S2
  - (iii) the VSWR on each of the three sections of the main line
  - (iv) the percentage of the power incident at the junction of stub S1 that gets transmitted
  - (v) the percentage of the power incident at the load that gets reflected

[15 marks]

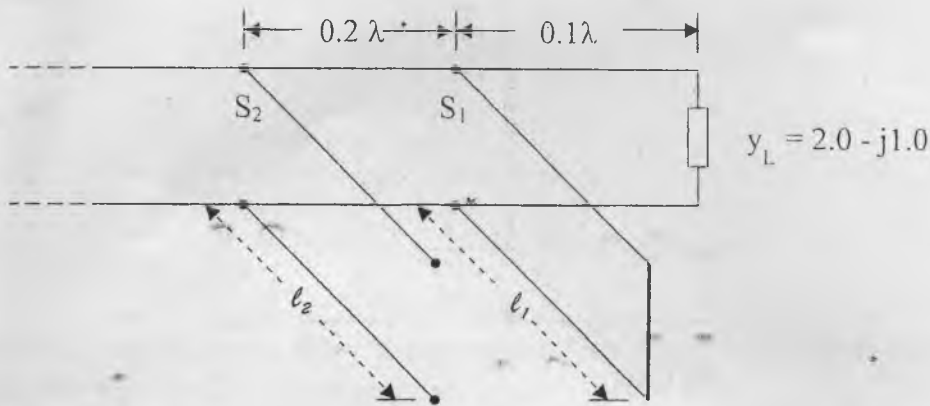


Figure Q4

QUESTION SIX: (20 MARKS)

- (a) Starting from the general expression for  $Z_{\ell}$ , the transmission line impedance at a point a distance  $\ell$  from the load  $Z_L$ , show that  $Z_{sc}Z_{oc} = Z_0^2$  and  $Z_{sc}/Z_{oc} = \tanh^2 \gamma \ell$

[4 marks]

- (b) A 50m long transmission line operating at 1MHz has open-circuit and short-circuit impedance of  $-j39.4\Omega$  and  $j142.8\Omega$  respectively. Calculate
  - (i) the characteristic impedance of the line
  - (ii) the propagation coefficient of the line
  - (iii) the line input impedance when terminated with a load of  $18.75 - j112.5\Omega$

[7 marks]

- (c) Given a high frequency line with  $Z_0=150\Omega$ , terminated in  $Z_L=70+j0\Omega$ . The line is  $18.68\lambda$  long. Neglecting losses, use the Smith Chart on an admittance basis to determine
  - (i) the reactance in ohms which, if connected across the sending end of the line, will make the input impedance of the combination a pure resistance
  - (ii) the input impedance of the line under the conditions in (i).

[3 marks]

- (d) Two transmission lines are connected in parallel at their sending ends. One line is  $0.625\lambda$  long and has  $Z_0=400\Omega$  with a termination  $Z_L=800\Omega$ . The other is  $0.375\lambda$  long and has  $Z_0=400\Omega$  and is terminated in an impedance of  $400+j400\Omega$ . Using ONLY the Smith Chart on an admittance basis, determine the input impedance of the parallel combination of the two lines.

[6 marks]

For a network  
 $R_1 = R_0 \left( \frac{N^2 - 1}{2N} \right)$   
 $R_2 = \frac{R_0}{2} \left( \frac{N+1}{N-1} \right)$

For T network  
 $R_1 = 2 R_0 \left( \frac{N-1}{N+1} \right)$   
 $R_2 = 2 R_0 \left( \frac{2N}{N^2-1} \right)$

$R_A = R_0 \left( \frac{N-1}{N+1} \right)$   
 $R_B = R_0 \left( \frac{N+1}{N-1} \right)$

Page 4 of 6