

KENYA METHODIST UNIVERSITY

END OF FIRST TRIMESTER 2008 EXAMINATIONS


FACULTY : **SCIENCE AND SOCIAL STUDIES**
DEPARTMENT : **COMPUTER AND INFORMATION SCIENCE**
COURSE CODE : **PHYS 310**
COURSE TITLE : **ELECTRICAL CIRCUITS**
TIME : **2 HOURS**

Instructions:

- Answer question **ONE** (compulsory) and any other **TWO** questions.

Question 1

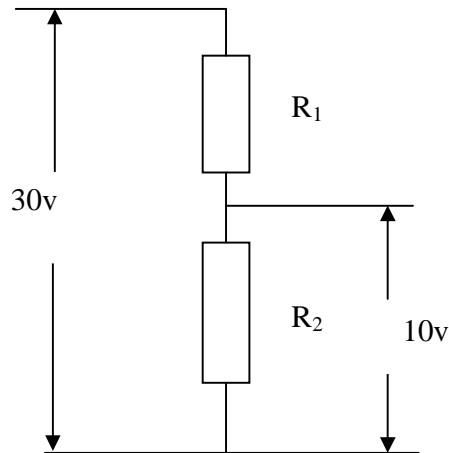
- a) Discuss the distinction between loads connected in series and loads connected in parallel. (4 mks)
- b) A voltage divider is to give an output voltage of 10v from an input voltage of 30v as shown.



- Calculate the resistance R₁, given $r_2 = 100\Omega$. (5 mks)
- c) An a.c generator consists of 8 turns of wire of area $A=0.09\text{m}^2$ and total resistance 12Ω . the loop operates in a magnetic field $B=0.5\text{T}$ at a constant frequency of 60Hz. Calculate the :-
- (i) Maximum induced e.m.f.
(ii) Maximum induced current. (7 mks)
- d) Draw phase diagrams showing relationship between the maximum voltage and current vectors for a resistor, inductor and capacitor. (6 mks)
- e) A resistance of 7Ω is connected in series with a pure inductance of 31.4mH and the circuit is connected to a 100v, 50Hz sinusoidal (ax) supply. Calculate the:-
- (i) Circuit current. (4 mks)
(ii) Phase angle. (4 mks)

Question 2

- a) State the superposition theorem. (4 mks)
- b) With reference to the circuit diagram shown below, use the superposition theorem to determine the value of the currents I_1 and I_2 respectively. (11 mks)

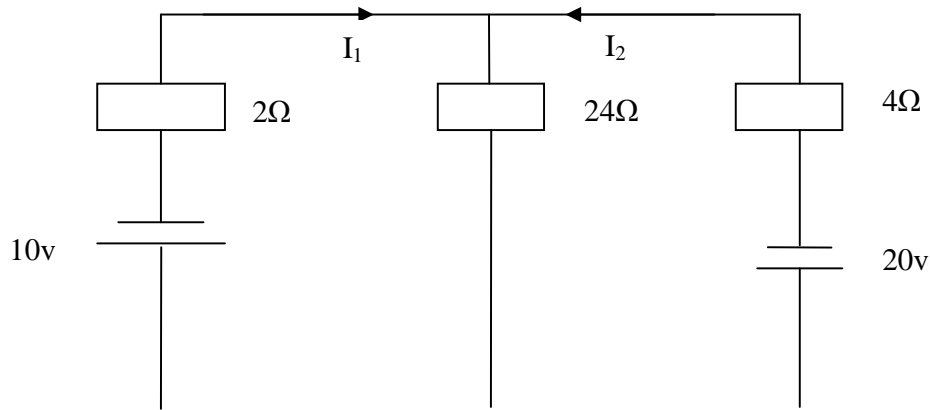

Question 3

- a) State Faraday's law of induction. (3 mks)
- b) Explain how a d.c generator operates. (5 mks)
- c) A coil is wrapped with 200 turns of wire on the perimeter of a square frame of sides 18cm. Each turn has the same area, equal to that of the frame, and the total resistance of the coil is 2Ω . A uniform magnetic field is turned on perpendicular to the plane of the coil. If the field changes linearly from 0 to 0.5Wb/m^2 in a time of 0.8 seconds, calculate the magnitude of:-
- (i) Induced e.m.f in the coil while the field is changing. (4 mks)
- (ii) Induced current in the coil while the field is changing. (3 mks)

Question 4

An alternating voltage supply contains in its circuit the following elements, inductor, $L = 230\text{mH}$, capacitor, $C = 15\text{mF}$ and resistor, $R=160\Omega$. All are connected in series.

- a) Using mathematical expressions differentiate between the terms reactance and impedance as used in a.c supply. (4 mks)
- b) Given that the elements given above operate on a 60Hz and 360v a.c supply, calculate
- (i) Impedance, z . (6 mks)
- (ii) Amplitude current, I_m . (2 mks)
- (iii) Phase angle θ . (3 mks)