



KENYA METHODIST UNIVERSITY

END OF 2ND TRIMESTER 2010 EXAMINATIONS

FACULTY : SCIENCE AND TECHNOLOGY
DEPARTMENT : COMPUTER SCIENCE & BUSINESS INFORMATION
UNIT CODE : PHYS 201
UNIT TITLE : ELECTRICAL CIRCUITS
TIME : 2 HOURS

Instructions:

- Question 1 is compulsory AND any other 2 questions.

Question 1

- a. Briefly discuss the following;
- Kirchoffs law (4mks)
 - Nortons theorem. (4mks)
- b. Define the following terms as used to AC circuits.
- Amplitude
 - Cycle (4mks)
- c. With the aid a well labeled diagram differentiate between first and second order circuits. (3mks)
- d. State three applications of a transformer. (3mks)
- e. Three phasors are given as $A=3+j3$, $B=4$ and $C=5+j$. Present operations AC in rectangular form; (2mks)

Question 2

- a. What's is a series A.C circuit [2marks]
- b. A coil has a resistance of $R=5\Omega$ and an inductance of $L=100\text{mH}$. At a particular instant in time after a battery is connected across the coil, the current is $i=2\text{A}$, and is increasing at a rate of $di/dt=20\text{As}^{-1}$. What is the voltage V of the battery? What is the time-constant of the circuit? What is the final value of the current? [7marks]
- c. With a relevant diagram, derive the differential equation of a series RL circuit [6marks]


Question 3

- a. Define the following forms in relation to DC circuits.
- Node [1marks]
 - Branch [1marks]
 - Loop [1marks]
- b. A current of $i(t)=12\sqrt{2}\cos(1000t+90^\circ)$ flows through a circuit composed of a resistor $R=18\Omega$ and a capacitor $C=83.3\times 10^{-6}\text{F}$ and a inductor $L=30\text{mH}$ connected in series. Find the resulting voltage across all three elements.

- i. Express $i(t)$ in phasor; $i=12 \angle 90^\circ$ [4marks]
- ii. Find the impedance for the ($\omega=1000$) [4marks]
- c. An alternating current is given by $i=120\sin 120\pi t$. find,
 - i. Maximum value [1marks]
 - ii. Time period [2marks]
 - iii. Instantaneous value when $t=1/360$ seconds [2marks]

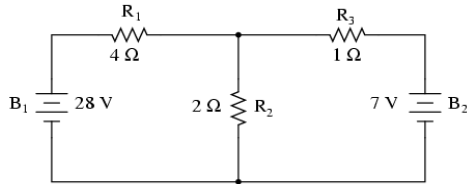Question 4

Find the currents and voltages across each resistor using the Superposition Theorem.



[20marks]

Question 5

- a. What is phase sequence in three-phase system [4marks]
- b. Differentiate between a step-down and step up transformer. [4marks]
- c. Draw a circuit showing the three windings of a three-phase alternator interconnected in a star connection. [5marks]
- d. In a RLC series circuit, show that $Z = \sqrt{R^2 + X_C^2 + X_L^2}$ [7marks]