

QUESTION ONE

- What is the effect of load p.f. on regulation of a transmission line? (2.5 mks)
- State the four key characteristic features that are required of all protection schemes (4 mks)
- A 3- $\phi$  overhead line has resistance and reactance per phase of  $5\Omega$  and  $20\Omega$  respectively. The load at the receiving end is 25 MW at 33kV and a p.f. of 0.8 lagging. Find the capacity of synchronous condenser required for this load condition if it is connected at the receiving end and the line voltages at both ends are maintained at 33 kV. (5.5 mks)
- What is the justification in neglecting line capacitance in short transmission lines? (2 mks)

Circle open  
resistor  
in circuit

QUESTION TWO

- What is Electric Power supply system? Draw a single line diagram of a typical a.c. power supply scheme. (5 mks)
- A 3- $\phi$  transmission line 200 km has the following constants:  
Resistance/phase/km =  $0.16\Omega$   
Reactance/phase/km =  $0.25\Omega$   
Shunt admittance/phase/km =  $1.5 \times 10^{-6} S$

Calculate by rigorous method the sending end voltage and current when the line is delivering a load of 20MW at 0.8 p.f. lagging. The receiving end voltage is kept constant at 110 KV. (9mks)

QUESTION THREE

- Discuss the requirements of a satisfactory electric supply system (6 mks)
- Deduce an expression for voltage regulation of a short transmission line, giving the vector diagram. (8 mks)

$$\frac{P}{I \cos \phi_r}$$

QUESTION FOUR

- Discuss conditions necessary for successful parallel operation of transformers (5 mks)
- Explain the construction and working of Brown-Boveri regulator with a neat sketch (9 mks)

QUESTION FIVE

- The present trend is towards a.c. for generation and distribution and d.c. for transmission. Discuss the reasons for it (4 mks)
- Tests on 31.5MVA, 132/33KV star/delta 3-phase transformer gave the following results (loss values given are for 100% load):

100% load  
100%  
100%

- open circuit test: 33KV, 5.5A, 21KW
- short circuit test: 13.2KV, 137.8A, 100KW. Calculate
  - Equivalent circuit parameters referred to LV side (3 mks)
  - Efficiency at full load and half of full load with unit p.f. (4 mks)
  - Regulation at full load with 0.8 p.f. lagging. (3 mks)

4V  
4W

QUESTION SIX

- Discuss the importance of voltage regulation in modern power systems (4 mks)
- A 3-phase, 50 Hz, 16 km long overhead line supplies 1000 KW at 11kV, 0.8 p.f. lagging. The line resistance is  $0.03\Omega$  per phase per km and line inductance is  $0.7 \text{ mH}$  per phase per km. Calculate the sending end voltage, voltage regulation and efficiency of transmission (7 mks)
- A long transmission line is open circuited at the receiving end. Will there be any current in the line at the sending? Explain your answer (3 mks)

Bulbs  
in  
meter

QUESTION SEVEN

- Discuss the terms voltage regulation and transmission efficiency as applied to transmission line (3 mks)
- A 3-phase, 50Hz transmission line 100km long delivers 20MW at 0.9 p.f. lagging and at 110 KV. The resistance and reactance of the line per phase are  $0.2\Omega$  and  $0.4\Omega$  respectively while capacitance admittance is  $2.5 \times 10^{-6}$  Siemens/km/phase. Calculate:
  - The current and voltage at the sending end
  - Efficiency of transmission. Use nominal T method (11 mks)



...the end.


Bonne chance

$$V_p = V_r + j I X$$

$$I_s = I_r + I_c$$

$$V_s = V_r + I R + j I X$$
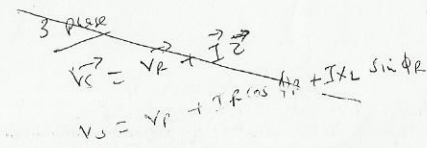
$$V_s = V_r + I R \cos \phi_r + j I X \sin \phi_r$$



$$X_c = \frac{1}{\omega C}$$

$$R_c = \frac{1}{\omega C}$$

QUESTION ONE

- a) What is the effect of load p.f. on regulation of a transmission line? (2.5 mks)
- b) State the four key characteristic features that are required of all protection schemes (4 mks)
- c) A 3- $\phi$  overhead line has resistance and reactance per phase of  $5\Omega$  and  $20\Omega$  respectively. The load at the receiving end is 25 MW at 33kV and a p.f. of 0.8 lagging. Find the capacity of synchronous condenser required for this load condition if it is connected at the receiving end and the line voltages at both ends are maintained at 33 kV. (5.5 mks)
- d) What is the justification in neglecting line capacitance in short transmission lines? (2 mks)

QUESTION TWO

- a) What is Electric Power supply system? Draw a single line diagram of a typical a.c. power supply scheme. (5 mks)
- b) A 3- $\phi$  transmission line 200 km has the following constants:
- Resistance/phase/km =  $0.16\Omega$
  - Reactance/phase/km =  $0.25\Omega$
  - Shunt admittance/phase/km =  $1.5 \times 10^{-6} S$

Calculate by rigorous method the sending end voltage and current when the line is delivering a load of 20MW at 0.8 p.f. lagging. The receiving end voltage is kept constant at 110 KV. (9mks)

QUESTION THREE

- a) Discuss the requirements of a satisfactory electric supply system (6 mks)
- b) Deduce an expression for voltage regulation of a short transmission line, giving the vector diagram. (8 mks)



QUESTION FOUR

- a) Discuss conditions necessary for successful parallel operation of transformers (5 mks)
- b) Explain the construction and working of Brown-Boveri regulator with a neat sketch (9 mks)

QUESTION FIVE

- a) The present trend is towards a.c. for generation and distribution and d.c. for transmission. Discuss the reasons for it (4 mks)
- b) Tests on 31.5MVA, 132/33KV star/delta 3-phase transformer gave the following results (loss values given are for 3 phases):

Regulation

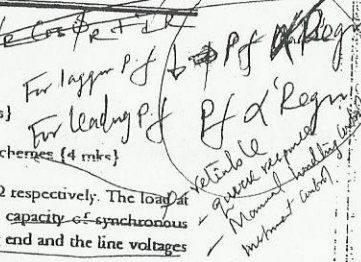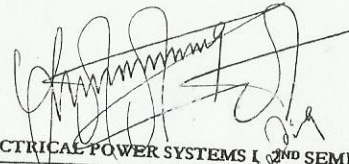

Handwritten notes:  $V_s = V_r + IR + jIX$ ,  $P_f \propto \cos \phi$ ,  $P_f \propto \cos \delta$

Handwritten notes:  $dc$  uses only 2 lines, less potential difference, hence need less insulation - Has Higher Voltage as it carries L.C. etc. - less corona loss

NO

- open circuit test: 33KV, 5.5A, 21KW
- short circuit test: 13.2KV, 137.8A, 100KW. Calculate
- Equivalent circuit parameters referred to LV side (3 mks)
  - Efficiency at full load and half of full load with unit p.f. (4 mks)
  - Regulation at full load with 0.8 p.f. lagging. (3 mks)

QUESTION SIX

- a) Discuss the importance of voltage regulation in modern power systems (4 mks)
- b) A 3-phase, 50 Hz, 16 km long overhead line supplies 1000 KW at 11kV, 0.8 p.f. lagging. The line resistance is  $0.03\Omega$  per phase per km and line inductance is 0.7 mH per phase per km. calculate the sending end voltage, voltage regulation and efficiency of transmission (7 mks)
- c) A long transmission line is open circuited at the receiving end. Will there be any current in the line at the sending? Explain your answer. (3 mks)

QUESTION SEVEN

- a) Discuss the terms voltage regulation and transmission efficiency as applied to transmission line (3 mks)
- b) A 3-phase, 50Hz transmission line 100km long delivers 20MW at 0.9 p.f. lagging and at 110 KV. The resistance and reactance of the line per phase are  $0.2\Omega$  and  $0.4\Omega$  respectively while capacitance admittance is  $2.5 \times 10^{-6}$  Siemens/km/phase. Calculate:
- The current and voltage at the sending end
  - Efficiency of transmission. Use nominal T method (11 mks)

...the end  
Bonne chance

$$V_{sc} = \sqrt{I^2 Z^2} = \sqrt{18.2^2 + 137.8^2}$$

$$Z_{01} = \left( \frac{137.8^2}{I^2} \right) = \dots$$

$$P_{01} = \left( \frac{W}{I^2} \right) = \dots$$

$$W = V I \cos \phi$$

$$\cos \phi = \frac{W}{V I}$$

$$\sin \phi = \frac{\sqrt{V^2 I^2 - W^2}}{V I}$$

$$\sin \phi = \frac{\sqrt{33^2 \times 10^2 - (33 \times 10)^2}}{33 \times 10} = 0.1157$$

$$\cos \phi = 0.9923$$

$$I_0 = \frac{W}{V \cos \phi} = \frac{33 \times 10^3}{33 \times 10 \times 0.9923} = 1000 A$$

$$X_0 = \frac{V}{I_0} = \frac{33 \times 10^3}{1000} = 33 \Omega$$

$$R_0 = \frac{W}{I_0^2} = \frac{33 \times 10^3}{1000^2} = 0.033 \Omega$$

$$Z_0 = \sqrt{R_0^2 + X_0^2} = \sqrt{0.033^2 + 33^2} = 33 \Omega$$

$$V_s = V_r + I_0 R_0 + j I_0 X_0 = 33 \times 10 + 1000 \times 0.033 + j 1000 \times 33 = 33330 + j 33000$$

$$|V_s| = \sqrt{33330^2 + 33000^2} = 46815 V$$

$$\text{Regulation} = \frac{|V_s| - V_r}{V_r} = \frac{46815 - 33000}{33000} = 0.4186$$

$$\text{Efficiency} = \frac{W}{V_s I_0 \cos \phi} = \frac{33 \times 10^3}{46815 \times 1000 \times 0.9923} = 0.71$$

QUESTION ONE

- $I_m$
- What is the effect of load p.f. on regulation of a transmission line? {1 mk}
  - State the four key characteristic features that are required of all protection schemes {4 mks}
  - A 3- $\phi$  overhead line has resistance and reactance per phase of  $5\Omega$  and  $20\Omega$  respectively. The load at the receiving end is 25 MW at 33kV and a p.f. of 0.8 lagging. Find the capacity of synchronous condenser required for this load condition if it is connected at the receiving end and the line voltages at both ends are maintained at 33 kV. {5 mks}
  - Describe *any four* equipment found/required in a transformer sub-station {4 mks}

QUESTION TWO

- State four desirable characteristics of insulating materials used in cables {4 mks}
- State any *three* advantages of reactors in control of short circuit currents {3 mks}
- A 3- $\phi$  transmission line 200 km has the following constants:

Resistance/phase/km =  $0.16\Omega$

Reactance/phase/km =  $0.25\Omega$

Shunt admittance/phase/km =  $1.5 \times 10^{-6} S$

Calculate by rigorous method the sending end voltage and current when the line is delivering a load of 20MW at 0.8 p.f. lagging. The receiving end voltage is kept constant at 110 KV. {7mks}

QUESTION THREE

- State *three advantages* and *three disadvantages* of oil circuit breakers {6 mks}
- Deduce an expression for voltage regulation of a short transmission line, giving the vector diagram. {8 mks}

QUESTION FOUR

- Explain the *arc phenomenon* in a circuit breaker. {4 mks}
- Explain the construction and working of Brown-Boveri regulator with a neat sketch {8mks}
- Define the term *Bushing* {2 mks}

QUESTION FIVE

- The present trend is towards *ac* for generation and distribution and *dc* for transmission. Discuss *four* reasons for it {4 mks}

- Tests on 31.5MVA, 132/33KV star/delta 3-phase transformer gave the following results (loss values given are for 3 phases):

-open circuit test: 33KV, 5.5A, 21KW

-short circuit test: 13.2KV, 137.8A, 100KW. Calculate

- Equivalent circuit parameters referred to LV side {3 mks}
- Efficiency at full load and half of full load with unit p.f. {4 mks}
- Regulation at full load with 0.8 p.f lagging. {3 mks}

QUESTION SIX

- Discuss the importance of voltage regulation in modern power systems {4 mks}
- A load of 1000kW at 0.8 p.f lagging is received at the end of a 3-phase line 20 km long. The resistance and reactance of each conductor are  $0.25\Omega$  and  $0.28\Omega$  per km. if the receiving end line voltage is maintained at 11KV, calculate:
  - Sending end voltage {2 mks}
  - Percentage regulation {2.5 mks}
  - Transmission efficiency {2.5 mks}
- A long transmission line is open circuited at the receiving end. Will there be any current in the line at the sending? Explain your answer. {3 mks}

QUESTION SEVEN

- State two advantages and two disadvantages of *fuses* as protection devices {4 mks}
- A 3-phase, 50Hz transmission line 100km long delivers 20MW at 0.9 p.f. lagging and at 110 KV. The resistance and reactance of the line per phase are  $0.2\Omega$  and  $0.4\Omega$  respectively while capacitance admittance is  $2.5 \times 10^{-6}$  Siemens/km/phase. Calculate:
  - The current and voltage at the sending end
  - Efficiency of transmission Use nominal  $T$  method {11 mks}

...the end

Bonne chance

5

6

*Handwritten notes and scribbles at the bottom of the page, including some numbers like 5230, 5738, and 28.*

Repetition

QUESTION ONE

- a) What is the effect of load p.f. on regulation of a transmission line? (2.5 mks)
- b) State the four key characteristic features that are required of all protection schemes (4 mks)
- c) A 3-φ overhead line has resistance and reactance per phase of 5Ω and 20Ω respectively. The load at the receiving end is 25 MW at 33kV and a p.f. of 0.8 lagging. Find the capacity of synchronous condenser required for this load condition if it is connected at the receiving end and the line voltages at both ends are maintained at 33 kV. (5.5 mks)

for lag p.f. =  $\frac{V_{s} - V_{r}}{V_r}$

$\frac{V_s - V_r}{V_r} = \frac{I R \cos \phi + I X \sin \phi}{V_r}$

- d) What is the justification in neglecting line capacitance in short transmission lines? (2 mks)

QUESTION TWO

- a) What is Electric Power supply system? Draw a single line diagram of a typical a.c. power supply scheme. (5 mks)


- b) A 3-φ transmission line 200 km has the following constants:

Resistance/phase/km=0.16Ω

Reactance/phase/km=0.25Ω

Shunt admittance/phase/km=1.5×10<sup>-6</sup>S

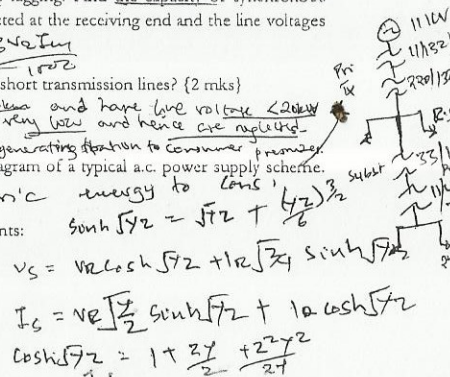Calculate by rigorous method the sending end voltage and current when the line is delivering a load of 20MW at 0.8 p.f. lagging. The receiving end voltage is kept constant at 110 KV. (9mks)



$V_s = V_r \cosh \sqrt{YZ} + I_r \sqrt{Z} \sinh \sqrt{YZ}$

$I_s = V_r \sqrt{Y} \sinh \sqrt{YZ} + I_r \cosh \sqrt{YZ}$

$\cosh \sqrt{YZ} = 1 + \frac{YZ}{2} + \frac{(YZ)^2}{24}$

QUESTION THREE

- a) Discuss the requirements of a satisfactory electric supply system (6 mks)
- b) Deduce an expression for voltage regulation of a short transmission line, giving the vector diagram. (8 mks)

Frequency Efficiency Voltage regulation

→ B.S. Balanced voltages

→ E = efficiency

→ D = dependability

→ F = frequency

→ Voltage Regulation

QUESTION FOUR

- a) Discuss conditions necessary for successful parallel operation of transformers (5 mks)
- b) Explain the construction and working of Brown-Boveri regulator with a neat sketch (9 mks)

→ same K

→ proper connection of polarity

→ if KV different, the imped. should be in the ratio of KV's

→ same % impedances or X/R ratio

→ pri. wind. should be suitable for the supply sys. with

QUESTION FIVE

- a) The present trend is towards a.c. for generation and distribution and d.c. for transmission. Discuss the reasons for it (4 mks)
- b) Tests on 31.5MVA, 132/33kV star/delta 3-phase transformer gave the following results (loss values given are for 3 phases):

no induction rd

$\cosh \sqrt{YZ} = 1 + \frac{YZ}{2} + \frac{(YZ)^2}{24}$

$\sinh \sqrt{YZ} = \sqrt{YZ} + \frac{(YZ)^2}{6}$


-open circuit test: 33KV, 5.5A, 21KW

-short circuit test: 13.2KV, 137.8A, 100KW. Calculate

- Equivalent circuit parameters referred to LV side (3 mks)
- Efficiency at full load and half of full load with unit p.f. (4 mks)
- Regulation at full load with 0.8 p.f. lagging. (3 mks)


QUESTION SIX

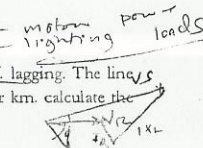- a) Discuss the importance of voltage regulation in modern power systems (4 mks)
- b) A 3-phase, 50 Hz, 16 km long overhead line supplies 1000 KW at 11kV, 0.8 p.f. lagging. The line's resistance is 0.03Ω per phase per km and line inductance is 0.7 mH per phase per km. calculate the sending end voltage, voltage regulation and efficiency of transmission (7 mks)
- c) A long transmission line is open circuited at the receiving end. Will there be any current in the line at the sending? Explain your answer. (3 mks)




QUESTION SEVEN

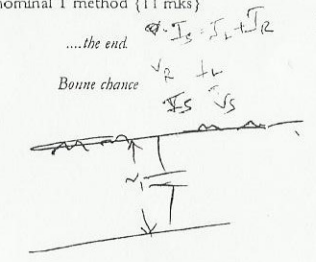- a) Discuss the terms voltage regulation and transmission efficiency as applied to transmission line (3 mks)
- b) A 3-phase, 50Hz transmission line 100km long delivers 20MW at 0.9 p.f. lagging and at 110 KV. The resistance and reactance of the line per phase are 0.2Ω and 0.4Ω respectively while capacitance admittance is 2.5 10<sup>-6</sup> Siemens/km/phase. Calculate:
- The current and voltage at the sending end
  - Efficiency of transmission. Use nominal T method (11 mks)



$I_0 = \frac{5.5}{\sqrt{3}} = 3.17$

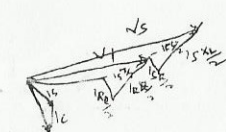

QUESTION ONE

- a) Figure Q1 shows interconnected power systems A and B. In quadrant 1 of figure Q1a (ii) the direction of flow of active and reactive power is shown. Determine the direction of flow of active and reactive power in quadrants 2, 3 and 4.

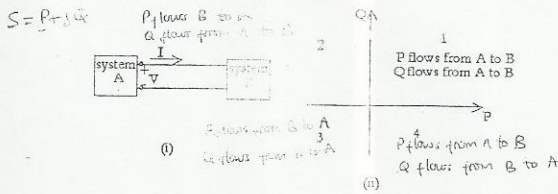


Figure 1a

(6 marks)

- b) A three phase, 50 Hz, 415 V motor develops 10kW, the power factor being 0.75 lagging and efficiency 95%. A bank of capacitors is connected in delta across the supply terminals and power factor raised to 0.92 lagging. Each of the capacitance units is built of 5 similar 83 V capacitors. Determine the capacitance of each capacitor (8 marks)

QUESTION TWO

- (a) Consider the circuit in Figure Q2. Given the following values:

$\bar{V}_m = 100 \angle 0^\circ \text{ A}$   
 $\bar{V}_n = 50 \angle 180^\circ \text{ A}$   
 $\bar{V}_o = 50 \angle 180^\circ \text{ A}$   
 $\bar{Z}_1 = 8 + j10 \Omega$   
 $\bar{Z}_{ab} = \bar{Z}_{bc} = \bar{Z}_{ca} = \bar{Z}_n = j4 \Omega$

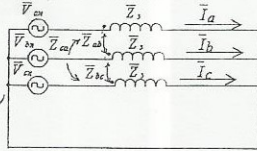


Figure Q2

- (b) Calculate  $\bar{I}_a$ ,  $\bar{I}_b$  and  $\bar{I}_c$  without using symmetrical components  
 (c) Calculate  $\bar{I}_a$ ,  $\bar{I}_b$  and  $\bar{I}_c$  using symmetrical components

Handwritten calculations for Question 2, including phasor diagrams and algebraic steps.  $I_a = 10 \times 0.55 = 5.5 \text{ A}$ ,  $5.5 \times 0.7 = 3.85 \text{ A}$ ,  $Q = 2375 \text{ VAr}$ ,  $\frac{260}{216} \text{ VAr}$ .

QUESTION THREE

- (a) Figure Q3 shows a single line diagram of a three-phase system. The percentage reactance of each generator is based on its own capacity. Find the short-circuit current that will flow a solid three-phase short-circuit at F.

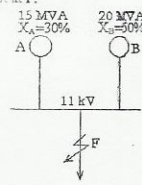


Figure Q3 Single line diagramme

(6 marks)

- (b) An ideal wattmeter has a zero-impedance current coil and an infinite-impedance potential coil and the meter reads  $P = VI \cos(\alpha - \beta)$ . Consider the following balanced 3-φ situation shown in Figure Q3b.

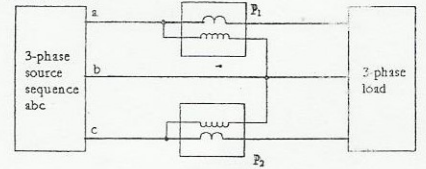


Figure Q3b

- (i) Prove that the top wattmeter reads  $P_1 = \sqrt{3} V_L I_L \cos(\psi + 30^\circ)$   
 (ii) Prove that the bottom wattmeter reads  $P_2 = \sqrt{3} V_L I_L \cos(\psi - 30^\circ)$   
 (iii) Show that  $P_1 + P_2 = \sqrt{3} V_L I_L \cos \psi$   
 (iv) Show that  $P_1 - P_2 = \sqrt{3} V_L I_L \sin \psi = \frac{Q_w}{\sqrt{3}}$

(8 marks)

QUESTION FOUR

- (a) Three-phase currents  $I_a$ ,  $I_b$  and  $I_c$  can be represented using symmetrical components  $I_1$  and  $I_2$ . Derive equations expressing:

- (i)  $I_a$ ,  $I_b$  and  $I_c$  in terms of  $I_1$ ,  $I_2$  and  $I_0$   
 (ii)  $I_1$ ,  $I_2$  and  $I_0$  in terms of  $I_a$ ,  $I_b$  and  $I_c$

QUESTION 1

- A star connected load consists of three equal resistors of  $1 \Omega$  resistance. The load is assumed to be connected to unsymmetrical 3-phase supply line voltages are  $V_{AB} = 240 \text{ V}$ ,  $V_{BC} = 240 \text{ V}$  and  $V_{CA} = 415 \text{ V}$ . Find:

- (i) the magnitudes of currents in phase A, B and C;  
 (ii) symmetrical components  $I_{a1}$ ,  $I_{a2}$ ,  $I_{a0}$ ;  $I_{b1}$ ,  $I_{b2}$ ,  $I_{b0}$ ;  $I_{c1}$ ,  $I_{c2}$  and  $I_{c0}$

Draw and explain an equivalent diagram of a long transmission line and explain all elements.

QUESTION 2

- (a) A 3-phase, 5 MVA, 11 kV generator with a solidly earthed neutral point supplies a feeder. The relevant impedances of the generator and feeder in Ohms are as under:


	Generator	Feeder
Positive sequence impedance	$11.2 + j1.0$	$11.0$
Negative sequence impedance	$10.9 + j1.0$	$11.0$
Zero sequence impedance	$10.4 + j1.0$	$11.0$

- If a fault from one phase to earth occurs on the far end of the feeder (phase A), calculate:  
 (i) the magnitude of fault current;  
 (ii) line to neutral voltage at the generator.

- (b) list the functions of circuit breakers in power systems

QUESTION 3

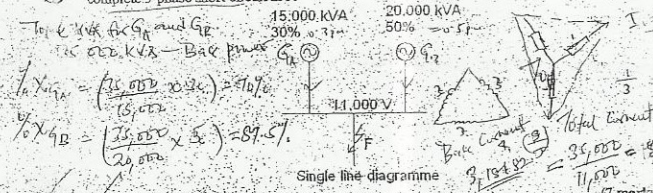- (a) Figure Q3 shows the single line diagramme of a 3-phase system. The percentage reactance of each generator is based on its own capacity. Find the short-circuit current that will flow into a complete 3-phase short circuit at F.



- (b) The currents in three phase unbalanced system are  $\bar{I}_a = (12 + j8) \text{ A}$ ;  $\bar{I}_b = (10 + j10) \text{ A}$ ;  $\bar{I}_c = (25 + j10) \text{ A}$ . The phase sequence is ABC. Calculate the zero, positive and negative sequence components of the currents.

Handwritten calculations for Question 3, including phasor diagrams and algebraic steps.  $X_d = 30\%$ ,  $X_d = 50\%$ ,  $I = 11362 \text{ A}$ .

QUESTION 4

- (a) Give two reasons why reactors are used in a power system


- (b) Prove that  $\frac{1-a^2}{1-a} = -a$

An overhead 3-phase transmission line delivers 10,000 kW at 11 kV at 0.8 power factor lagging. The resistance and reactance of each conductor is  $4 \Omega$  and  $6 \Omega$  respectively. Determine:

- (i) Sending end voltage;  $V_s = V_r + IZ$   
 (ii) Percentage regulation;  
 (iii) Transmission efficiency.

QUESTION 5

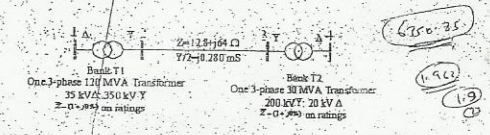
- (a) Consider the 3-phase system in fig 10. at bus 2,  $S_{3\text{phase}} = 100 \text{ MVA}$  and  $V_{Lbase} = 220 \text{ kV}$ .



- (i) Tabulate all four base values ( $S_{base}$ ,  $V_{base}$ ,  $I_{base}$ ,  $Z_{base}$ ) at all four buses (16 values total)  
 (ii) Draw the positive-sequence equivalent circuit for the given system locating all the four buses.  
 (iii) Convert all impedance data provided into per unit, and enter those values in the circuit in (ii)  
 (iv) Draw the zero sequence equivalent circuit for the system locating all the four buses.

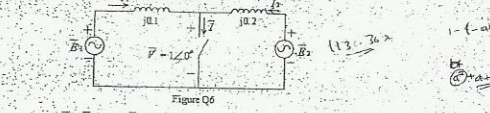QUESTION 6

- For the circuit in figure Q6 the prefault (before switch is closed) currents are  $\bar{I}_1 = -j2 = 120^\circ$ .



- (a) Calculate the fault currents  $\bar{I}_1$ ,  $\bar{I}_2$  and  $\bar{I}_3$  (switch closed) by calculating correct values for  $E_1$  and  $E_2$  first.

Handwritten calculations for Question 6, including phasor diagrams and algebraic steps.  $I = 11362 \text{ A}$ .

- (b) A balanced star connected load takes 60 A from a balanced 3-phase, 4-wire supply. If the fuses in the Y and B phases are removed, find the symmetrical components of the line currents:
- before the fuses are removed
  - after the fuses are removed

(6 marks)

QUESTION FIVE

- (a) A star connected load consists of three equal resistors of 1 Ω resistance. The load is assumed to be connected to an unsymmetrical 3-phase supply, whose magnitudes of line voltages are  $V_{ab}=208\text{ V}$ ,  $V_{bc}=360\text{ V}$  and  $V_{ca}=416\text{ V}$ . Find the magnitude of the current in phase 'a' using symmetrical component method. (Note:  $\vec{V}_{ab} + \vec{V}_{bc} + \vec{V}_{ca} = 0$ )
- (b) (i) Explain the causes of unsymmetrical and unbalanced supply in power systems  
(ii) Explain the measures taken in transmission lines to ensure that the supply is symmetrical and balanced.

(4 marks)

QUESTION SIX

- (a) Derive an expression for fault current for double line-to-ground fault by symmetrical components method.
- (b) (i) What is the justification in neglecting line capacitance in short transmission lines  
(ii) A long transmission line is open circuited at the receiving end. Explain whether there will be any current in the line

(4 marks)

QUESTION SEVEN

- (i) (i) Explain the functions of a circuit breaker (1 marks)  
(ii) Name four types of circuit breakers (2 marks)  
(iii) Give advantages and disadvantages of the circuit breakers given in (ii).
- (b) Explain the following terms as used in power systems
- Bushing
  - Instrument transformers
  - Bus-bars
  - Isolators

(5 marks)

Answer any five of the given seven questions. All questions carry equal marks

QUESTION ONE

- (a) For given three impedances in a network, connected in star, derive the delta connected impedances that would replace the star but maintain the currents and voltages to the points of connection.
- (b) Assume a balanced 3-phase voltage source with  $\vec{V}_{an} = E\angle 0^\circ$ , and phase sequence abc.
- Compute and locate on phasor-diagram  $\vec{V}_{ab}$ ,  $\vec{V}_{bc}$ ,  $\vec{V}_{ca}$ ,  $\vec{V}_{an}$ ,  $\vec{V}_{bn}$  and  $\vec{V}_{cn}$ .
  - Connect the three-phase source terminals (abc) to a balanced delta load such that  $\vec{Z}_\Delta = Z_\Delta \angle \psi$ .
  - For the diagram in (ii) compute the load currents  $\vec{I}_a$ ,  $\vec{I}_b$  and  $\vec{I}_c$  and add them to your diagram.
  - Determine the wye impedance,  $\vec{Z}_Y$ , (in terms of  $\vec{Z}_\Delta = Z_\Delta \angle \psi$ ) that could be used to replace the delta so that the line currents would remain unchanged, in both magnitude and phase.

(6 marks)

(8 marks)

QUESTION TWO

- (a) Explain why electrical power transmitted over a long distance is done at high voltage.
- (b) What is the percentage saving in copper conductor if the line voltage in a 2-wire d.c. system is raised from 220V to 500V for the same power transmitted over the same distance and having the same power loss?
- (c) Consider the circuit in Figure Q2. Suppose  $\vec{V}_{an} = 100\angle 0^\circ$ ,  $\vec{V}_{bn} = 50\angle 180^\circ$ ,  $\vec{V}_{cn} = 50\angle 180^\circ$ ,  $\vec{Z}_c = 8 + j10$ , and  $\vec{Z}_{bc} = \vec{Z}_{ca} = \vec{Z}_m = j4$

(4 marks)

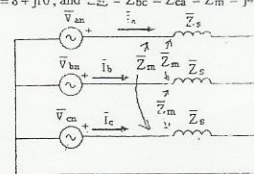


Figure Q2

- (i) Calculate  $\vec{I}_a$ ,  $\vec{I}_b$  and  $\vec{I}_c$  without using symmetrical components,  
(ii) Calculate  $\vec{I}_a$ ,  $\vec{I}_b$  and  $\vec{I}_c$  using symmetrical components.

(8 marks)

$$k_a = V_0 + V_1 + V_2$$

Answer any five of the given seven questions. All questions carry equal marks

QUESTION THREE

- (a) Explain the following terms:
- Geometric mean radius (GMR) of a wire
  - Equivalent geometrical spacing of conductors
- (b) Determine the equivalent geometric spacing of conductors A, B and C spaced as follows: distance between A and B is  $d_1$ ; B and C is  $d_2$ ; and A and C is  $d_3$ .
- (c) A single phase a.c. system supplies a load of 200 kW and if this system is converted to 3-phase, 3-wire a.c. system by running a third similar conductor, calculate the 3-phase load that can now be supplied if the voltage between the conductors is the same. Assume the power factor and transmission efficiency to be the same in the two cases.

(4 marks)

(2 marks)

(8 marks)

QUESTION FOUR

- (a) A long transmission line is open circuited at the receiving end. Explain whether there will be any current in the line at the sending end.
- (b) A single-phase transmission line has two parallel conductors 3 m apart, the radius of each conductor being 1 cm. Calculate the loop inductance per km length of the line if the material of the conductor is:
- copper
  - steel with relative permeability of 100
- (c) A 3-phase, 50 Hz, 66 kV overhead line conductor are placed in a horizontal plane. The conductor diameter is 1.25 cm. If the line length is 100 km, assuming complete transposition of the line, calculate:
- capacitance per phase,
  - charging current per phase.

(5 marks)

(6 marks)

QUESTION FIVE

- (a) What is the importance of short circuit calculations?
- (b) Explain why reactors are used in the power systems
- (c) A 4-winding ideal transformer has windings with the following numbers of turns:  $N_1=1000$  turns,  $N_2=500$  turns,  $N_3=2000$  turns,  $N_4=3000$  turns. The windings are terminated as follows:
- Source  $V_1=1000\angle 0^\circ\text{ V}$ .
  - impedance  $\vec{Z}_2 = 10\ \Omega$
  - impedance  $\vec{Z}_3 = 40 - j30\ \Omega$
  - impedance  $\vec{Z}_4 = j100\ \Omega$
- Draw a circuit diagram, defining all circuit currents and voltages
  - Solve for all winding currents and voltages
  - Calculate the complex power into winding 1
  - Calculate the winding power out of winding 2, 3 and 4.
  - Suppose  $V_{1base}=1000\text{ V}$  and  $I_{1base}=100\text{ A}$ . Calculate  $V_{2base}$ ,  $V_{3base}$ ,  $V_{4base}$ ,  $I_{2base}$ ,  $I_{3base}$ ,  $I_{4base}$ ,  $S_{1base}$ ,  $S_{2base}$ ,  $S_{3base}$  and  $S_{4base}$

(3 marks)

(2 marks)

(11 marks)

Answer any five of the given seven questions. All questions carry equal marks

QUESTION SIX

- (a) Prove that  $\frac{1-a}{1+a^2} = 1-a^2$ .
- (b) Consider the power system terminated as shown in Figure Q6. Derive the appropriate interconnections between sequence networks.

(2 marks)

(12 marks)

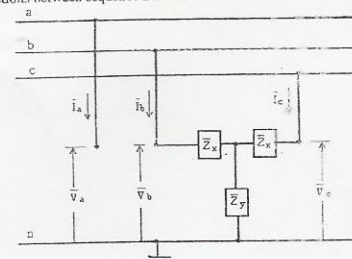


Figure Q6

QUESTION SEVEN

- (a) Do the sequence components physically exist in a 3-phase system? Explain.
- (b) Consider the system in figure Q7. Derive Thevenin equivalent sequence networks looking in at bus 1.

(3 marks)

(11 marks)

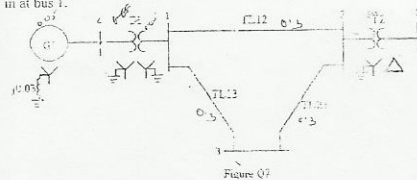


Figure Q7

**QUESTION ONE**

A three-bus system is given in the figure below. The ratings of the various components are as listed hereunder:

Generator 1: 50 MVA, 13.8 kV,  $x = 0.15$  p.u.

Generator 2: 40 MVA, 13.2 kV,  $x = 0.2$  p.u.


Generator 3: 30 MVA, 11 kV,  $x = 0.25$  p.u.

Transformer 1: 45 MVA, 11/110 ( $\Delta/Y$ ) kV,  $x = 0.1$  p.u.

Transformer 2: 25 MVA, 12.5/115 ( $\Delta/Y$ ) kV,  $x = 0.15$  p.u.

Transformer 3: 40 MVA, 12.5/115 ( $\Delta/Y$ ) kV,  $x = 0.1$  p.u.

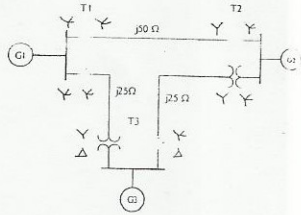The line impedances are indicated on the diagram. Determine impedance diagram based on 50 MVA and 13.8 kV as base quantities in Generator #1.



**QUESTION TWO**

Determine the sending-end voltage, current and power factor of a single phase 50 Hz, 76.2 kV transmission line delivering 12 MW at 0.8 p.f. lagging. The line constants are  $R = 25$  ohm, inductance = 200 mH and capacitance between lines = 2.5  $\mu$ F. Also determine the voltage regulation and efficiency of the line.

**QUESTION THREE**

Determine the efficiency and voltage regulation of a three-phase, 50 Hz, 150 km long transmission line having three conductors spaced 3.5 m delta formation when the receiving end delivers 25 MVA at 120 kV and 0.9 p.f. lagging. The resistance of the conductor is 0.25  $\Omega$ /km and the effective diameter is 0.75 cm. Neglect leakage and use:

(i) Nominal-T equivalent line model

(ii) Nominal- $\pi$  equivalent line model

**QUESTION FOUR**

Shown below is a 35 kV network supplying three step-down substations A, B and C from a generating station S. The whole network is made of aluminum conductor having a cross-sectional area of 120 mm<sup>2</sup> ( $r_c = 0.27 \Omega$ /km,  $x_c = 0.405 \Omega$ /km). The lengths of the network sections (in km) and the substation loads are indicated on the diagram. Determine power flow along the line sections and the maximum voltage drop under normal operating conditions.

