



EGERTON

UNIVERSITY

UNIVERSITY EXAMINATIONS

FIRST SEMESTER 2009/2010
SECOND YEAR EXAMINATION FOR THE DEGREE OF BACHELOR OF SCIENCE
IN INSTRUMENTATION AND CONTROL ENGINEERING

ICEN 221 - ELECTRONICS DEVICES

STREAM:

TIME: 2 HRS

DAY: TUESDAY, 8.30 – 11.30 A.M.

DATE: 08/12/2009

Instructions

- i. Answer any five questions
- ii. All questions carry equal marks
- iii. Exam takes 2 hours 30 minutes
- iv. Do not write on the question paper
- v. All the rough work should be done the answer booklet

Constants:

Charge of an electron:	$1.6 \times 10^{-19} \text{ C}$
Mass of an electron:	$9.1 \times 10^{-31} \text{ Kg}$
Planck's constant:	$6.625 \times 10^{-34} \text{ JHz}^{-1}$
Permittivity of free space:	$8.854 \times 10^{-12} \text{ C}^2\text{J}^{-1}\text{m}^{-1}$
Boltzmann's constant:	$1.38 \times 10^{-23} \text{ J/k}$

Question 1

- a) A germanium atom has an atomic number 32, and energy gap of 0.72 eV,
- i. Draw the electrons distribution diagram [2 marks]
 - ii. If an electron recombines with a hole, compute the wavelength of the resulting radiation [2 marks]
 - iii. Compute the energy of an electron revolving in the conduction band [4 marks]
 - iv. What is the radius of the valence orbit? [2 marks]

Handwritten notes:
 $\frac{mv^2}{r} = \frac{Ze^2}{4\pi\epsilon_0 r^2}$
 $v^2 = \frac{Ze^2}{4\pi\epsilon_0 m r}$
 $\frac{nh}{2\pi r} = v$
 $\frac{nh^2}{4\pi^2 m r^2} = \frac{Ze^2}{4\pi\epsilon_0 r}$
 $r = \frac{nh^2}{4\pi^2 m Ze^2}$
 $1\text{eV} = 10^{-10} \text{ J}$


$\frac{32}{8} = 4$

2, 4, 8, 7, 5, 3

ICEN 221

b) From the circuit given below,

- i. Calculate the value of V_o for $V_{in}=6V$ and for $V_{in}=20V$ [2 marks]
- ii. Explain the results obtained in part (i) [2 marks]

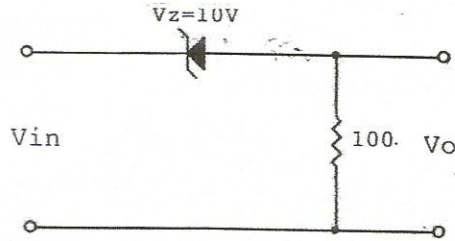

Question 2


a) Explain What courses the following phenomenon in a P-N junction [8 marks]

- i. Formation of depletion layer ✓
- ii. Existence of barrier potential ✓
- iii. Existence of junction capacitance
- iv. High resistance in reverse bias ✓

b) State two reasons why, Gallium arsenide (GaAs) is one of the compound semiconductor grapping the area of microwave semiconductor devices. [2 marks]

c) The data sheet of E-MOSFET in the circuit below gives $I_{D(on)} = 4mA$ at $V_{GS} = 10V$ and $V_{GS(th)} = 5V$. Calculate the V_{GS} and V_{DS} for the circuit. [4 marks]

Supply $V = 25V$

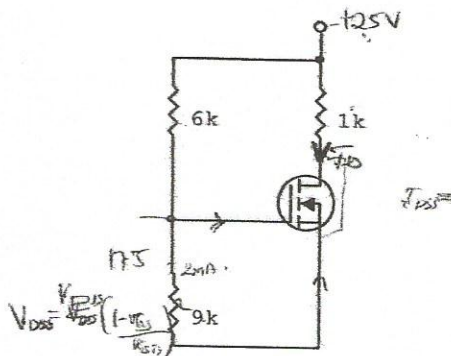

Handwritten calculations:
 $V_{GS} = 5 + 4 \times 9 = 41V$
 $V_{DS} = 25 - 4 \times 1 = 21V$

Question 3

a) A half-wave rectifier using silicon diode has a secondary e.m.f of 14.14V (rms) with internal resistance of 0.2Ω . The diode has a forward resistance of 0.05Ω and a threshold voltage of $0.7V$. If the load resistance is 10Ω , determine [6 marks]

- i. DC load current
- ii. DC load voltage
- iii. Efficiency

$V_{rms} =$

b) With the aid of a circuit diagram explain the working of a BJT as switch [4 marks]

c) State the difference that exist in conductivity of the following

- i. Metals and semiconductors
- ii. P-type and N-type semiconductors

[4 marks]

5 ← → 10

Question 4


- a) A given UJT has an inter-base resistance of 10K. It has $R_{B1}=6K$ with $I_E=0$. Find
- i. UJT current if $V_{BB}=20V$ and V_E is less than V_P [2 marks]
 - ii. Intrinsic standoff ratio η and V_A [2 marks]
 - iii. Peak point voltage V_P [2 marks]
- b) With reference to MOSFETs explain the formation of virtual Channel [6 marks]
- c) Define the following terms with reference to IC technology. [2 marks]
- i. Circuit probing
 - ii. Metallization

$\frac{1}{m^2} \times V \times \frac{m^2}{Vs} \frac{1}{m^2} = \dots$

$V_A = \eta V_{BB}$


$V_P = \eta V_{BB} = 0.7$

$0.2 \times 6 = \dots$

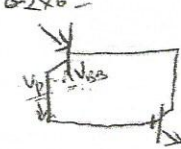

Question 5

- a) Manufacturers data sheets shows that an LED has maximum forward voltage of 1.8V, reverse breakdown voltage of 10V, if the LED maximum forward current is 15mA,
- i. Design a power on indicator circuit that feeds on AC. [3 marks]
 - ii. State two other applications that LEDs are used. [2 marks]
- b) The reverse saturation current of a NPN transistor in common – base circuit is 12.5 μ A. For an emitter current of 2mA, collector current is 1.97mA. Determine the current gain and the base current [3 marks]
- c) Using the two transistor analogy, explain the operation of SCR [6 marks]

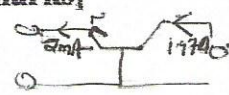

Question 6



- a) Discuss the working of JFET with the help of its drain characteristics [8 marks]
- b) Silicon is doped with acceptor atoms to a density of $10^{22} m^{-3}$. If it is assumed that all the acceptor centres are ionized, calculate the conductivity of the extrinsic silicon, given that the intrinsic density is $1.41 \times 10^{16} m^{-3}$, mobility of electron = $0.145 m^2/V-s$ and mobility of holes = $0.05 m^2/V-s$. [4 marks]
- c) Explain the zener breakdown mechanism [2 marks]

acceptor - $|atom = 4e|$
 donor - $|atom = 1|$

Question 7

- a) The input signal in the figure below is applied to the clamper circuit adjacent,
- i. Draw the output waveform V_o
 - ii. State the necessary condition for the circuit to operate as a clamper circuit
 - iii. Draw the waveform when R is changed to 100 Ω
 - iv. Comment on the shape obtained in part (iii).

$f=1000Hz$

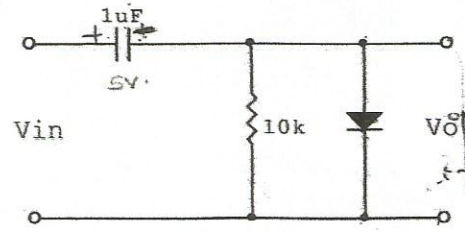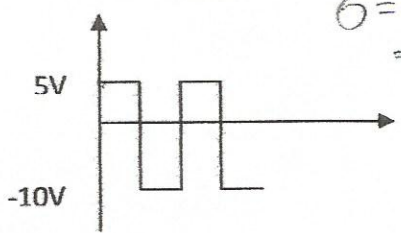

[8 marks]

V_{DS}
 $V_{GS} = 0$
 JFET

$6 = \eta e \mu e$


10
 5
 10

$\alpha = \frac{\beta}{\beta + 1}$

- b) From the basic transistor current equations derive the relationship between α and β . [4 marks]
- c) Explain how thermal runaway condition is attained in a transistor [2 marks]

Question 8

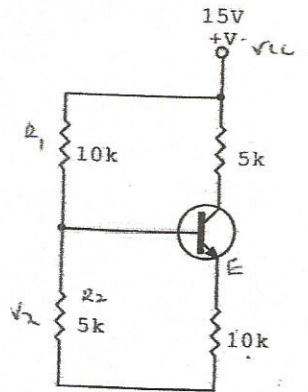a) Find the VCE and VE for the circuit given below



$I_C \approx I_E$ [4 marks]

$V_{CE} = V_{CC} - I_C(R_C + R_E)$
 $= 15 - 0.5 \times 10^{-3} (5 + 10) \times 10^3$
 $= 15 - 0.0075 \times 15$
 $= 14.9925$

$V_B = V_{CC} \times \frac{R_2}{R_1 + R_2} = \frac{15 \times 5}{15} = 5V$

$I_E = \frac{V_B - V_{BE}}{R_E} = \frac{5 - 0.7}{10 \times 10^3} = 0.43$

$V_E = 0.43 \times 10^{-3} \times 10 = 4.3$

- b) Explain why the output signal of CE circuit is 180° out of phase [2 marks]
- c) Compare abrupt-junction and hyperabrupt-junction varactor diodes [4 marks]
- d) State three roles of a bleeder resistor in a power supply [3 marks]
- e) State the precaution that would take when handling MOSFETs out of circuit [1 mark]

