

TECHNICAL UNIVERSITY OF MOMBASA
A Centre of Excellence

Department of Electrical & Electronic Engineering

TEST1 3rd November 2011

Time: 2 hours

1. (a) A lossless transmission line of characteristic impedance 75Ω is terminated in a load of $75 + j150 \Omega$. If the line is 1m long and the signal frequency is 1 GHz, find the:
- (i) Reflection coefficient at the load
 - (ii) Normalized load admittance
 - (iii) VSWR
 - (iv) Input impedance
- (20 Marks)
2. (a) Consider the transmission line in figure (Qu.1a). Given : $V_g = 15V_{RMS}$; $Z_0 = 75 \Omega$; $Z_g = 75 \Omega$; $Z_L = 50 - j100 \Omega$ and the length $l = \lambda$. Determine:
- (v) Reflection coefficient at the load
 - (vi) Reflection coefficient along the line
 - (vii) Voltage along the line
 - (viii) Maximum line voltage
 - (ix) Minimum line voltage
 - (x) SWR
- (20 Marks)

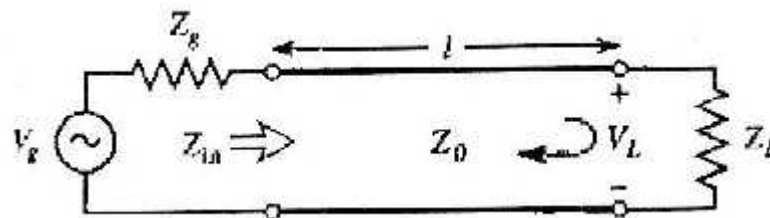


Figure (Qu.1a)

3. Prove mathematically that the input impedance of a short-circuited length of transmission line $\lambda/8$ long is equal to $+jZ_0$, while the input impedance of an open-circuited length of transmission line $\lambda/8$ long is equal to $-jZ_0$. Check your answers with a Smith chart.
- (10 marks)