



THE MOMBASA POLYTECHNIC UNIVERSITY COLLEGE
DEPARTMENT OF ELECTRICAL & ELECTRONIC ENGINEERING



Faculty of Engineering and Technology

FOURTH YEAR /SUPPLEMENTARY SEMESTER EXAMINATIONS
FOR THE DEGREE OF SCIENCE IN ELECTRICAL & ELECTRONIC ENGINEERING

EEE 2405 ANALOGUE FILTERS

MAY 2011 SERIES

TIME: 2 HOURS

INSTRUCTION TO CANDIDATES

Answer question ONE and any other TWO questions from the FIVE presented

- Qu. 1(a) (i) Relate the concept of a transfer function to the operation of a filter
(ii) Describe any TWO major functions of filters in RF systems (4 marks)
- (b) Figure Q1(b) shows the circuit of a simple notch filter.

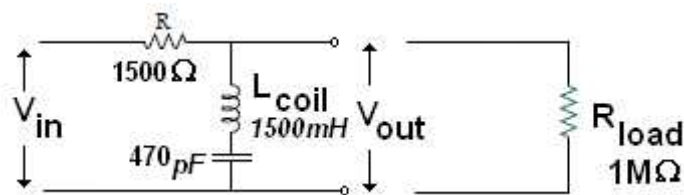


Fig. Qu.(1b)

Determine the following:

- I. The transfer function $H(\omega)$ for the loaded and unloaded output
- II. The resonant frequency
- III. The circuit magnification (Q)
- IV. The circuit bandwidth
- V. Upper and lower cut-off frequency (16 marks)

Qu. 2(a) With the aid of well labeled sketches illustrate the pass and stop bands for the following filter responses

- (i) Low pass
- (ii) High pass
- (iii) Band pass
- (iv) Notch (8 marks)

- (b) Describe how filters are used in the following applications:
- (i) Power supplies
 - (ii) Receivers
 - (iii) Transmitters
 - (v) Audio electronics (4 marks)
- (c) (i) Distinguish between passive and active filters indicating their ranges of operation in frequency.
- (ii) List any TWO challenges posed by cascading filter sections (6 marks)
- (d) Given a transfer function $H(s)$, explain the important information that can be extracted from the following:
- (i) No. of poles
 - (ii) Coefficient of $H(s)$ (2 marks)

- Qu.3 (a) With the aid of a sketch compare the essential characteristics of the following filters types:
- i. Butterworth
 - ii. Chebyshev
 - iii. Bessel (6 marks)

- (b) Consider an RLC low pass filter shown in figure Q3(b).

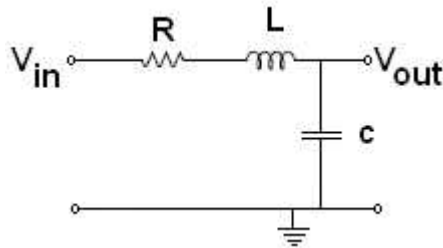


Fig. Qu.(3b)

- (i) Determine the transfer functions $H(s)$
- (ii) Express the transfer function in (b)(i) in terms of ζ_0 and Q .
- (iii) Solving for the denominator of the transfer function $H(s)$ in b(ii) analyze the circuits behaviour when:
 - a) $Q = 0.5$
 - b) $Q > 0.5$ (14 marks)

Qu.4. Design a passive wide band filter according to the data indicated in figure Q4(i) and table Q(4).

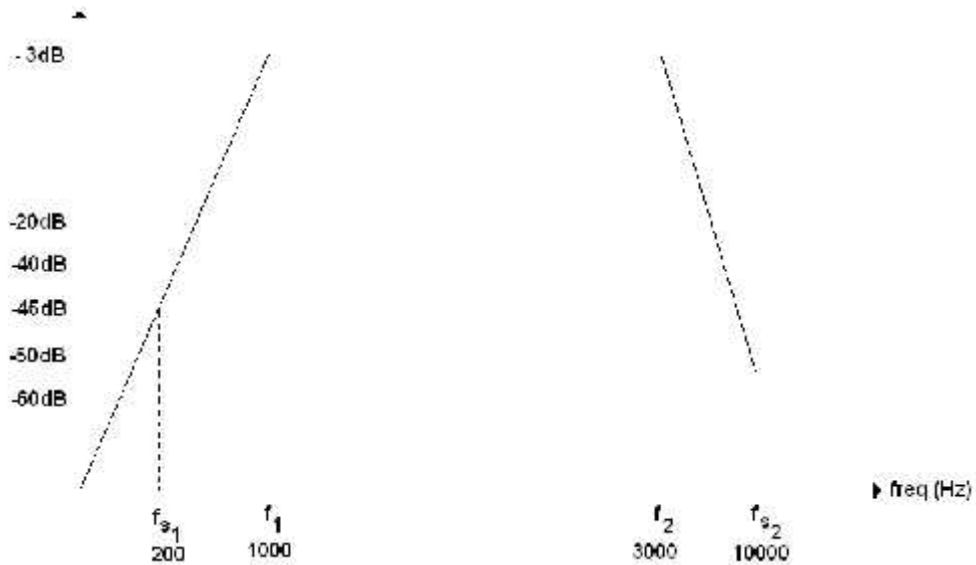


Fig. Qu.4(i)

Assume that the source and load impedances are both 50 Ω and a Butterworth design is desired.

- Qu.5 (a) (i) Describe any THREE desirable characteristics of active filters. (4 marks)
- (ii) Highlight ONE major drawback of active filters (4 marks)
- (b) Using the data in figure Q4(ii) and table Q(5) design a Butterworth low-pass active filter with the following specifications: (14 marks)
- 3 dB point at 100 Hz
 - 60 dB attenuation at 400 Hz
 - Z value of 10,000
- (c) Explain the effect of circuit Q on the transient response of the filter output. (7 marks)