## BPY 1101 BASIC ELECTRICITY AND OPTICS

## CAT 1 [30 MARKS]

TIME: 1<sup>1</sup>/<sub>2</sub> HOURS

#### Instruction: Attempt ALL questions in CAT I & II

- The charge in a certain body is determined to be  $+0.6\mu$ C. Determine the number of a) electrons needed to neutralize the body. [3 marks] Solution:  $+1C = 10^{6} \mu C$  of charge consists of  $6.25 \times 10^{18}$  protons. Let the number of protons be  $N_p$ Therefore, for  $+0.6\mu$ C of charge  $N_p = \frac{0.6}{10^6} \times 6.25 \times 10^{18} = 3.75 \times 10^{12} \ protons$ [2 marks] Number of electrons  $(N_e)$  needed must be equal to the number of excess protons. Hence,  $N_{e} = 3.75 \times 10^{12}$  electrons. [1 mark] b) State the four factors that affect the resistance of a conductor. [4 marks] Solution: *The resistance* R *offered by a conductor depends on the following factors: (i) The length of the conductor* [1 mark] (ii) the cross-sectional area A of the conductor [1 mark] (iii) the nature of the material [1 mark] *(iv) the temperature of the conductor* [1 mark]
- c) Silicon atom has Z = 29. Give its electronic distribution indicating which orbits are full and which are not. [2 marks]

Solution:

*Since atomic number represents protons, then the number of electrons is also 29. Thus the distribution is:-*

K-orbit	2 electrons	full
L-orbit	8 electrons	full
M-shell	18 electrons	full
N-shell	1 electron	incomplete
Total	29 electrons	

- d) For the arrangement shown in the diagram, find
  - (i) The equivalent capacitance of the circuit
  - (ii) The voltage across QR
  - (iii)The charge on each capacitor

[12 marks]



## Solution:

*(i) The equivalent capacitance of the circuit* 

$$\frac{1}{C_{eq}} = \frac{1}{2+3} + \frac{1}{15} = \frac{1}{5} + \frac{1}{15} = \frac{3+1}{15} = \frac{4}{15} \text{ or}$$

$$C_{eq} = \frac{15}{4} \mu F = 3.75 \,\mu F$$
[2 marks]

(ii) The voltage across QR The charge flowing in the circuit is given by  $Q = C_{eq}V = (3.75 \times 10^{-6})(240) = 9 \times 10^{-4} C$ 

Voltage across QR is given by

$$V_{QR} = \frac{Q}{15 \times 10^{-6}} = \frac{9 \times 10^{-4}}{15 \times 10^{-6}} = 60 \,\mathrm{V}$$
 [2 marks]

(iii) The charge on each capacitor  
Voltage across the capacitor connected in parallel is  

$$V_p = V - V_{QR} = 240 - 60 = 180 V$$
 [2 marks]  
Charge on 2  $\mu$ F capacitor is

$$Q_{2\mu F} = (2 \,\mu F) (V_p) = (2 \times 10^{-6}) (180) = 3.6 \times 10^{-4} \,C \qquad [2 \text{ marks}]$$
  
Charge on 3 µF capacitor is

$$Q_{2\mu F} = (2 \,\mu F) (V_p) = (3 \times 10^{-6}) (180) = 5.4 \times 10^{-4} C \qquad [2 marks]$$
  
The charge on 15  $\mu F$  capacitor is

$$Q = C_{eq}V = (3.75 \times 10^{-6})(240) = 9 \times 10^{-4} C$$
 [2 marks]

e) A coil is would from a 10m length of copper wire having a cross-sectional area of  $1mm^2$ . Calculate the resistance of the coil. Take the specific resistance of copper as  $1.73 \times 10^{-8} \ \Omega - m$ . [3 marks] Solution:

$$R = \rho \frac{l}{A} = (1.73 \times 10^{-8}) \frac{10}{1 \times 10^{-6}} = 0.173 \,\Omega$$
 [3 marks]

f) A small sphere is given a charge of  $+20 \,\mu\text{C}$  and a second sphere of equal diameter is given a charge of  $-5\mu\text{C}$ . The two spheres are allowed to touch each

other and are then spaced 10 cm apart. What force exists between them? What electric field is being radiated by the  $+20 \ \mu$ C sphere?. Assume air as the medium.

[6 marks]

## Solution:

When the two spheres touch each other, the resultant charge is: =  $20+(-5)=15\mu$ C [1 mark]

When the spheres are separated, charge on each sphere is:

$$Q_1 = Q_2 = \frac{15}{2} \mu C = 7.5 \mu C$$
 [1 mark]

Hence, force between is

$$F = \frac{Q_1 Q_2}{4\pi\varepsilon_0 \varepsilon_r r^2} = \frac{(9 \times 10^9)(7.5 \times 10^{-6})(7.5 \times 10^{-6})}{1 \times (0.1)^2} = 50.56 \, N \, repulsive \qquad [2 \, marks]$$

Electric Field 
$$E = \frac{F}{Q} = \frac{50.56}{7.5 \times 10^{-6}} = 6.74 \times 10^6 N/C$$
 [2 marks]

# CAT 2 [25 MARKS]

- a) For the circuit shown in Fig. Q a), find
  - (i) the total circuit resistance
  - (ii) the supply current
  - (iii)the current through each resistor
  - (iv) the voltage across each resistor

[9 marks]



# Solution:

Let the voltages be in the circuit as shown below. Hence,



*(i) the total circuit resistance* 

$$R_{T} = R_{1} + \frac{R_{2}R_{3}}{R_{2} + R_{3}} + R_{4}$$

$$= 2.5 + \frac{6 \times 2}{6 + 2} + 4$$

$$= 2.5 + 1.5 + 4$$

$$= 8 \Omega$$
[1 mark]

(ii) the supply current

$$I = \frac{V}{R_{T}} = \frac{200}{8} = 25 \,\mathrm{A}$$
 [1 mark]

(iii) the current through each resistor

$$I_1 = \left(\frac{R_3}{R_2 + R_3}\right) I = \left(\frac{2}{6+2}\right) 25 A = 6.25 A$$
 [1 mark]

$$I_{2} = \left(\frac{R_{2}}{R_{2} + R_{3}}\right)I = \left(\frac{6}{6+2}\right)25A = 18.75A$$
[1 mark]
Current through  $R_{1}$  is  $I = 25$ A
[1/2 mark]

Current through  $R_1$  is I = 25 A Current through  $R_4$  is I = 25 A

*(iv) the voltage across each resistor* 

$$V_{1} = R_{1}I = (25)2.5 = 62.5V$$

$$[1 mark]$$

$$V_{2} = (R_{2})I_{1} = (6.25)6 = 37.5V$$

$$[1 mark]$$

$$V_{3} = (R_{4})I = (25)4 = 100V$$

$$[1 mark]$$

- b) A coil of  $12\Omega$  resistance is in parallel with a coil of  $20\Omega$  resistance. This combination is connected in series with a third coil of  $8\Omega$  resistance. If the whole circuit is connected across a battery having a e.m.f. of 30V, calculate
  - i) the terminal voltage of the battery and
  - ii) the power in the  $12\Omega$  coil.
  - iii) currrent flowing in each resistor

#### [7 marks]

[½ mark]

Solution:



- *i)* The terminal voltage of battery is 30V since it does not have internal resistance [1 mark]
- ii) Total circuit resistance is  $R_T = R_1 + \frac{R_2 R_3}{R_2 + R_3}$  [1 mark] =  $8 + \frac{12 \times 20}{12 + 20} = 15.5 \Omega$  [1 mark]

Circuit current is  $I = \frac{V}{R_T} = \frac{30}{15.5} = 1.94 A$ 

[1 mark]

Current through the 12 
$$\Omega$$
,  $I_1 = \left(\frac{20}{12+20}\right)I = \left(\frac{20}{12+20}\right) \times 1.71 = 1.2125 \text{ A}$   
[1 mark]

Current through the 20 
$$\Omega$$
,  $I_2 = \left(\frac{12}{12+20}\right)I = \left(\frac{12}{12+20}\right) \times 1.94 = 0.7275 \text{ A}$   
[1 mark]

iii) Power in the 12 
$$\Omega$$
,  $P_{R_2} = R_2 I_1^2 = 12 (1.2125)^2 = 17.64 \text{ W}$  [1 mark]

- c) State the Kirchhoff's laws.
  - (i) Kirchhoff's Current Law (KCL): It states that in any network of conductors, the algebraic sum of currents meeting at a point (or a junction) is zero i.e. the total current leaving a junction is equal to the total current entering that junction. [1<sup>1</sup>/<sub>2</sub> marks]
  - (ii) Kirchhoff's Voltage Law: It states that the algebraic sum of all IR drops and emfs in any closed loop (or mesh) of a network is zero i.e. [1<sup>1</sup>/2 marks]

[3 marks]

d) Use Kirchhoff's laws to obtain the values of  $I_1$  and  $I_2$  in Fig Q d).





# Solution:

Applying KVL to the first loop of Fig. 2, we get

 $-2700I_{1} - 3300(I_{1} - I_{2}) - 4700I_{1} + 20 = 0$ 10700I\_{1} - 3300I\_{2} = 100 -------[i] [2 marks] Applying KVL to the second loop of Fig.2, we get  $-5600I_{2} - 2700I_{2} + 3300(I_{1} - I_{2}) = 0$ 3300I\_{1} - 11600I\_{2} = 0 -------[ii] [2 marks] Solving equation [i] and [ii] for the currents, have  $I_{2} = 2.91 \times 10^{-3} A$ [1 mark]  $I_{1} = 0.0102 A$ [1 mark]