



MASENO UNIVERSITY
UNIVERSITY EXAMINATIONS 2016/2017

**THIRD YEAR FIRST SEMESTER EXAMINATIONS FOR THE
DEGREE OF BACHELOR OF SCIENCE AND BACHELOR OF
EDUCATION SCIENCE WITH INFORMATION TECHNOLOGY**

MAIN CAMPUS

SPH 307: INTRODUCTION TO ELECTRONICS

Date: 28th November, 2016

Time: 3.30 - 6.30 pm

INSTRUCTIONS:

- Answer ALL questions in SECTION A and any TWO questions in SECTION B.



SECTION A. This section is **COMPULSORY**.

It carries a total of **30 marks**.

1. a) (i) What is the most important characteristic that differentiates semiconductors from metals and insulators? Explain. **(3 marks)**
- (ii) Electrons do not recombine with holes in the p-type base region as they diffuse to the collector. Why? **(2 marks)**
- (iii) Using a diagram, derive the relation between *drift velocity* (v_d) and *current density* (J). **(5 marks)**
- b) (i) State three important parameters of semiconductor diodes. **(3 marks)**
- (ii) Describe the phenomenon of *avalanche* and *Zener* breakdown effects. **(5 marks)**
- (iii) Figure 1 shows the characteristics of a Zener diode.

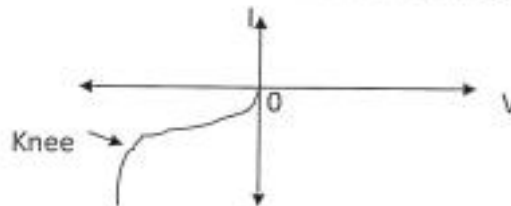


Fig.1

Explain the significance of the *knee*? **(3 marks)**

- c) (i) Explain why NPN transistor is more popular than PNP transistor. **(2 marks)**
- (ii) In practice, why are transistors most often used in *common-emitter* configuration. **(2 marks)**
- (iii) State two important features of a transistor. **(2 marks)**
- d) (i) What is an *oscillator*? **[1 mark]**
- (ii) Draw an oscillator equivalent circuit. **[2 marks]**

SECTION B. Answer **ONLY TWO** questions from this section.

Each question carries twenty (20) marks.

2. a) The diagram in figure 2 shows a simplified transistor circuit with a few discrete components.

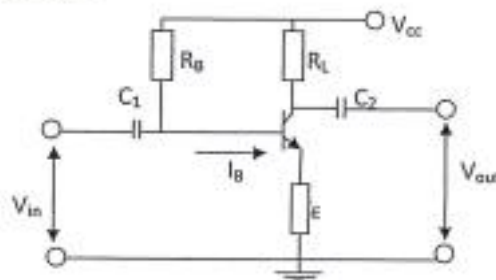


Fig. 2

You are given that $R_B = 1.8 \text{ M}\Omega$, $R_L = 4.7 \text{ k}\Omega$, $R_E = 1 \text{ k}\Omega$, $C_1 = C_2 = 10 \mu\text{F}$ and $V_{CC} = 15\text{V}$.

- (i) Explain how V_{out} and I_B are developed. [2 marks]
- (ii) What is the purpose of C_1 and C_2 in the circuit? [2 marks]

- b) Sketch an improved method of the biasing mode in figure 2 and explain how it works. [10 marks]

- c) (i) Write the *load line equation* for the circuit in figure 2. [2 marks]
(ii) If $V_{CE} = 7.5\text{V}$ and $\alpha_E = 50$, calculate I_C and I_B . [4 marks]

3. a) (i) Indium antimonide has a narrower forbidden gap than silicon. But why is silicon more desirable for semiconductor devices than it? [2 marks]
(ii) Name four areas of application for semiconductor devices. [2 marks]
(iii) Semiconductor devices have many important advantages over other types of electronic devices. Name any four advantages. [2 marks]

- b) (i) Explain why electrons in the valence band of a semiconductor can conduct current at room temperature. [2 marks]
(ii) What is a *compensated crystal*? [2 marks]
(iii) Explain *doping* as used in semiconductors. [2 marks]

- c) (i) What is a semiconductor? (2 marks)
 (ii) What happens to the silicon crystal lattice if its temperature is raised above absolute temperature? (2 marks)
 (iii) What happens to the conductivity of silicon:
 I) when you dope the material with equal numbers of donors and acceptors? (2 marks)
 II) when you dope silicon with unequal numbers of both kinds of dopants? (2 marks)

4. a) (i) Give any four characteristics of an ideal operational amplifier. [3 marks]
 (ii) Describe what bandwidth means and give an example of an amplifier application where bandwidth is important. [3 marks]

b) (i) Give a schematic diagram of an operational amplifier. [2 marks]

- (ii) Draw a circuit of an op-amp wired as an *integrator*. Show the currents in the circuit. [4 marks]

- c) Prove that the output voltage V_o and the input voltage V_i of the integrator are related as:

$$V_o = -(1/RC) \int V_i dt \quad [8 \text{ marks}]$$

5. a) (i) By indicating the flow of carriers in a diagram and explaining each step, derive the expression of conductivity (σ) of an intrinsic semiconductor in terms of mobility (μ). (10 marks)
 (ii) As in (a) above, derive the expression of conductivity of N and P types of semiconductors. (6 marks)

- b) What is the resistivity of an intrinsic germanium semiconductor at 300°K given that $q = 1.6 \times 10^{-19} \text{C}$, $n_i = 2.5 \times 10^{13}$, $\mu_n = 3600$ and $\mu_p = 1700$. (4 marks)

END