



MASENO UNIVERSITY
UNIVERSITY EXAMINATIONS 2013/2014

FIRST YEAR FIRST SEMESTER EXAMINATIONS FOR THE
DEGREE OF BACHELOR OF SCIENCE IN COMPUTER SCIENCE
& TECHNOLOGY, BACHELOR OF SCIENCE IN COMPUTER
SCIENCE AND BACHELOR OF SCIENCE IN INFORMATIO
TECHNOLOGY
(MAIN CAMPUS)

SCS 108/CCS 103: ELECRICAL PRINCIPLES

Date: 26th November, 2013

Time: 2.30 - 4.30 p.m.

INSTRUCTIONS:

- **SECTION A: Question ONE is COMPULSORY.**
- **SECTION B: Questions 2-5: Answer ANY TWO questions.**

SECTION A**{30 MARKS}**

- Q1. (a) State the primary energy source used in each of the following electrical devices:
- (i) Battery
 - (ii) Generator
 - (iii) Thermocouple [3 marks]
- (b) Give the definitions of the following terms:
- (i) Watt [2 marks]
 - (ii) Joule [2 marks]
- (c) (i) State the resistance value and percentage tolerance for the four-band colour-coded resistor shown in figure 1.1.

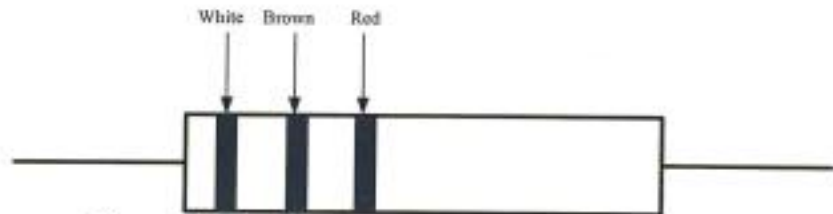


Figure 1.1.

[2 marks]

- (ii) A separate fifth orange stripe is present on a colour-coded carbon-composition resistor. If 100 000 of such resistors were made, determine the number of these resistors likely to fail in the first 1000-hour period. [2 marks]
- (d) Two resistors having resistances of $6\ \Omega$ and $9\ \Omega$ respectively are connected across a battery having an e.m.f. of $9\ \text{V}$ and an internal resistance of $1.8\ \Omega$. Calculate:
- (i) the terminal voltage [4 marks]
 - (ii) the energy dissipated by the $9\ \Omega$ resistor if the current remains constant for 6 minutes. [2 marks]
- (e) The field coil of a motor has a resistance of $220\ \Omega$ at 18°C . Determine the increase in resistance if the motor attains an average temperature of 50°C when running. Assume $\alpha = 0.00426 / ^\circ\text{C}$. [5 marks]

- (f) A circuit consists of a resistor R in parallel with a capacitor C and connected across an ac source as shown in figure 1.2.

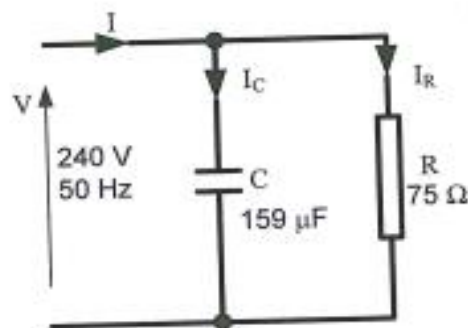


Figure 1.2.

Calculate the currents flowing in the circuit.

[8 marks]

SECTION B

{20 MARKS EACH}

- Q2. (a) With the aid of diagrams, briefly explain the meaning of **temperature coefficient of resistance of a material** [6 marks]
- (b) A load supplied by copper and aluminium cables connected in parallel draws a current of 250 A. Each cable has a conductor of total length of 150 m and cross-sectional area of 45 mm^2 . Taking resistivity of copper and aluminium to be $0.018 \mu\Omega \text{ m}$ and $0.028 \mu\Omega \text{ m}$ respectively, determine the current carried by each cable. [8 marks]
- (c) The field winding of a d.c. motor is connected directly across a 480 V supply. A current of 2.5 A flows when the winding is at a room temperature of 18°C . The current drops to 1.7 A and the voltage remains unaltered after some hours of machine operation. Assuming the temperature coefficient of resistance of copper to be $0.00426 / ^\circ \text{C}$ at 0°C , calculate the average temperature throughout the winding. [6 marks]

Q3.

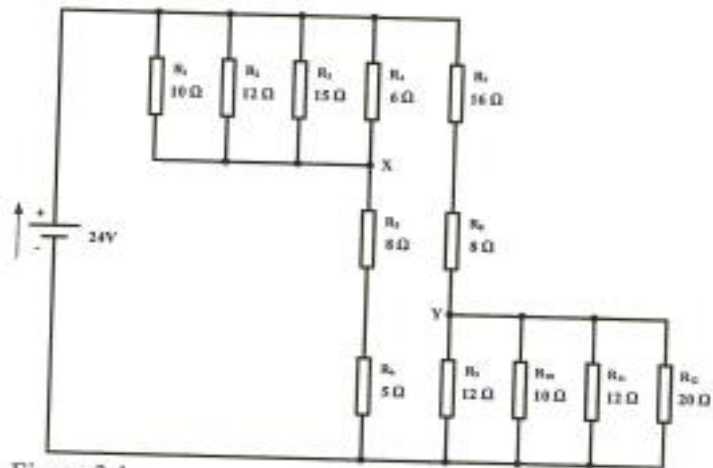


Figure 3.1.

Using the network shown in figure 3.1., determine:

- (a) Currents through points X and Y [12 marks]
- (b) Potential of point X with reference to point Y. [8 marks]

Q4.

- (a) With the aid of sketches show the dependence of reactance and current on frequency for a circuit that is purely:
 - (i) Capacitive [4 marks]
 - (ii) Inductive [4 marks]

(b)

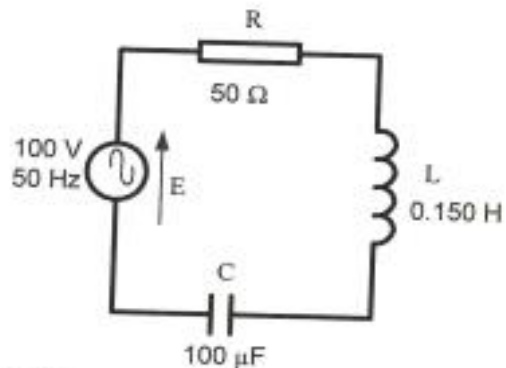


Figure 4.1.

From the circuit given in figure 4.1., calculate:

- (i) the circuit impedance [4 marks]
- (ii) the voltages across R, L and C [6 marks]
- (iii) the phase difference between the supply current and the supply voltage [2 marks]

Q5. (a) State:

- (i) Kirchoff's first law [2 marks]
- (ii) Kirchoff's second law [2 marks]

(b) A certain circuit is arranged as shown in figure 5.1.

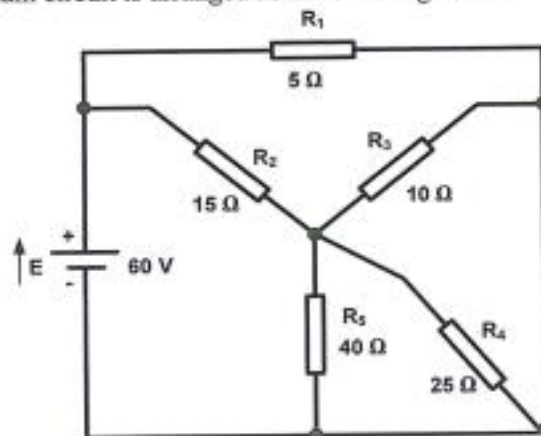


Figure 5.1.

Applying Maxwell's circulating current technique, calculate current in each of the network. [16 marks]