



MERU UNIVERSITY OF SCIENCE AND TECHNOLOGY

P.O. Box 972-60200 – Meru-Kenya.

Tel: 020-2069349, 061-2309217. 064-30320 Cell phone: +254 712524293, +254 789151411

Fax: 064-30321

Website: www.must.ac.ke Email: info@must.ac.ke

University Examinations 2013/2014

SECOND YEAR, FIRST SEMESTER EXAMINATION FOR DIPLOMA IN ELECTRICAL
ENGINEERING

EEE 0224: DIGITAL ELECTRONICS I

DATE: APRIL 2014

TIME: 1 ½ HOURS

INSTRUCTIONS: Answer question *one* and any other *two* questions

QUESTION ONE – (30 MARKS)

- (a) In the circuit of figure 1.1 below, the switches may be ON (1) or OFF (0) and will cause the bulb to be ON (1) or OFF(0).

Prepare a truth table for the circuit diagram above indicating all the possible conditions of the switches S1 and S2 and the corresponding responses for the bulb. (5 Marks)

- (b) For the logic expression

$$Y = A\bar{B} + \bar{A}B$$

- (i) Obtain the truth table (2 Marks)
 - (ii) Realize the operation using AND, OR and NOT gates (3 Marks)
 - (iii) Realize the operation using only NAND gates (3 Marks)
 - (iv) Name the operation performed (2 Marks)
- (c) Convert the following decimal to octal
- (i) 24 (2 Marks)
 - (ii) 110.2 (3 Marks)
- (d) Draw the schematic diagram of a 2-input RTL NOR gate and explain its logic operation. (5 Marks)
- (e) Define the following terms;
- (i) Bit (1 Mark)
 - (ii) MSB (2 Marks)
 - (iii) Fan-out (2 Marks)

QUESTION TWO – (15 MARKS)

- (a) Use the figure below to answer the following questions

- (i) Obtain the Boolean expression for C, D, E and F. (4 Marks)
 - (ii) Obtain the truth table of the circuit. (5 Marks)
- (b) Perform the following arithmetic operations
- (i) $1B_{(16)} + 2E_{(16)} =$ (2 Marks)
 - (ii) $21_{(8)} + 14_{(8)} =$ (2 Marks)
 - (iii) $1101_{(2)} - 1100_{(2)} =$ (2 Marks)

QUESTION THREE – (15 MARKS)

- (a) Represent the decimal number 27 in binary form using;
- (i) Binary code (straight binary) (3 Marks)
 - (ii) BCD code (2 Marks)
 - (iii) Excess-3 code (2 Marks)
 - (iv) Gray code (2 Marks)
 - (v) Octal code (2 Marks)
 - (vi) Hexadecimal code (2 Marks)
- (b) State two commonly used alphanumeric codes. (2 Marks)

QUESTION FOUR – (15 MARKS)

Draw the schematic diagram of a 3-input TTL NAND gate and explain its operation showing the components used to fabricate it. (15 Marks)