

MERU UNIVERSITY OF SCIENCE AND TECHNOLOGY

P.O. Box 972-60200 – Meru-Kenva.

Tel: 020-2069349, 061-2309217. 064-30320 Cell phone: +254 712524293, +254 789151411

Fax: 064-30321

Website: www.must.ac.ke Email: info@must.ac.ke

University Examinations 2013/2014

FIRST YEAR, SECOND SEMESTER EXAMINATION FOR DIPLOMA IN ELECTRICAL ENGINEERING

EEE 0203: ELECTRICAL ENGINEERING PRINCIPLES II

DATE: APRIL 2014

TIME: 1 ¹/₂ HOURS

INSTRUCTIONS: Answer question one and any other two questions

QUESTION ONE – (30 MARKS)

- (a) Define the following terms as used in A.C circuits
 - (i) Instantaneous value
 - (ii) Form factor
 - (iii) Amplitude (3 Marks)
- (b) Describe the generation of A.C voltage with the aid of a diagram. (4 Marks)
- (c) State two advantages of A.C transmission over D.C transmission. (4 Marks)
- (d) The following three impedances are connected in series across a 40V, 200KHZ supply
 - (i) A resistance of 8Ω
 - (ii) A coil of inductance $130\mu H$ and 5Ω resistor
 - (iii) A 10 Ω resistor in series with 0.25 μ H capacitor

Determine

- (i) The circuit current
- (ii) The phase angle
- (iii) The voltage drop across each element. (10 Marks)
- (e) State Faradays law of electromagnetic induction.
- (f) With the aid of diagrams differentiate between self inductance and mutual inductance.

(4 Marks)

(2 Marks)

(g) Describe a resonance RLC series circuit and derive the formula for resonance for the circuit. (3 Marks)

QUESTION TWO - (15 MARKS)

- (a) A resistor of 25Ω is connected in series with a capacitor of $45\mu F$. Determine
 - (i) The impedance of the circuit.
 - (ii) The current taken from the supply of 240V, 50HZ
 - (iii)The phase angle between current and voltage (10 Marks)
- (b) With aid of a circuit diagram and a phasor diagram derive the equation for determining impedance in a series RL circuit. (5 Marks)

QUESTION THREE – (15 MARKS)

- (a) Show that the total inductance in a parallel connection of three inductances is given by the reciprocal of the sum of the three inductances. (2 Marks)
- (b) State two applications of inductors. (2 Marks)
- (c) A coil of inductance 318.3mH and negligible resistance is connected in series with 200Ω resistor to a 240V, 50HZ supply. Determine
 - (i) The inductance of the coil
 - (ii) The impedance of the circuit
 - (iii)The p.d across each component
 - (iv)The circuit phase angle. (10 Marks)

QUESTION FOUR – (15 MARKS)

- (a) With the aid of a circuit diagram differentiate between an RLC series circuit and an RLC parallel circuit. (4 Marks)
- (b) Define the term impedance as used in A.C circuits. (1 Mark)
- (c) A coil of negligible resistance and inductance 100mH is connected in series with a capacitance of $2\mu F$ and a resistance of 10Ω across a 50V, variable frequency supply. Determine:
 - (i) The resonant frequency
 - (ii) The current at resonance
 - (iii)The voltages across the coil and the capacitor at resonance. (10 Marks)