



SOUTH EASTERN KENYA UNIVERSITY
UNIVERSITY EXAMINATIONS 2016/2017

FIRST SEMESTER EXAMINATION FOR THE DEGREE OF BACHELOR
SCIENCE

SCE 203: ELEMENTS PHYSICS II

9TH DECEMBER, 2016

TIME: 4.00-6.00 P.M

INSTRUCTIONS TO CANDIDATES

- This paper consists of FIVE questions.
- Answer question **ONE** and any other **TWO** questions.
- Question **ONE** carries 30 mark while the other **TWO** questions carry 20 marks each
- Use the following constants where necessary

$$\text{Coulomb's Constant } k_e = 8.99 \times 10^9 \text{ N.m}^2 / \text{C}^2$$

$$\text{Permittivity of free space } \epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2 / \text{N.m}^2$$

$$\text{Permeability of free space } \mu_0 = 4\pi \times 10^{-7} \text{ H / m}$$

$$\text{Proton mass } m_p = 1.67 \times 10^{-27} \text{ kg}$$

$$\text{Electron mass } m_e = 1.67 \times 10^{-31} \text{ kg}$$

$$g = 9.81 \text{ m/s}^2$$

QUESTION ONE (COMPULSORY) (30 MARKS)

- a) State coulombs law and give its mathematical form [2 marks]
- b) Calculate the value of two equal charges if they repel one another with a force of 0.2N. when situated 30cm apart in a vacuum [3 marks]
- c) Give the expression for electric field strength at a distance d from an isolated point charge Q [1 mark]

- d) Define the term electric potential at any point in the field [2 marks]
- e) Sketch a graph showing how the potential varies with distance from the charge [2 marks]
- f) Along straight conductor X- carrying a current of 2A is placed parallel to short conductors Y of length 0.05m carrying a current 3A. The two conductors are 0.1m apart. Calculate
- The flux density due to X and Y [2 marks]
 - The force on Y [3 marks]
- g) State the faradays law of electromagnetic induction [2 marks]
- h) A capacitor in an RC circuit is charged to 67% of its maximum value in 0.9s. What is the time constant for the circuit [5 marks]
- i) State and explain two ways through which electrical energy is lost in a transformer (4 marks)
- j) Sketch an I-V curve characteristics for a diode both in forward and reverse bias (4 marks)

QUESTION TWO (20 MARKS)


- a) Show that the equivalent capacitance C_{eq} of three capacitors C_1, C_2, C_3 connected in series is given by

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

And in parallel

$$C_{eq} = C_1 + C_2 + C_3 \quad [8 \text{ marks}]$$

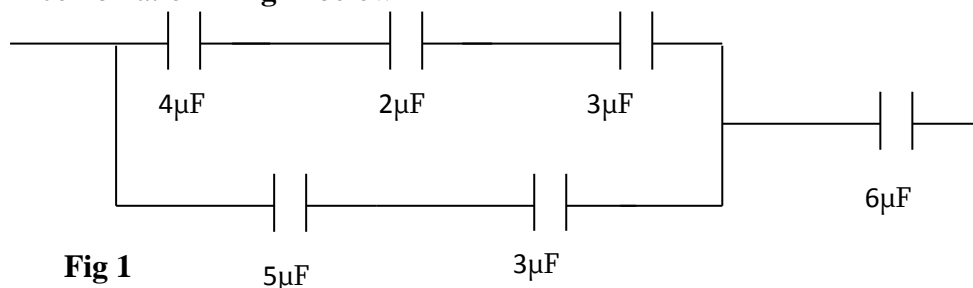- b) Six capacitors are connected as shown below. Find the equivalent capacitance of the combination in **fig 1** below [5marks]



- c) A capacitor is made of parallel plates of cross-section area 20cm^2 separated by 2cm. If the space between the two plates is a vacuum. Calculate its capacitance [3 marks]
- d) If the capacitor in © above is charged to a p.d of 200V. calculate the energy stored by the capacitor [4 marks]

QUESTION THREE (20 MARKS)

- a) State kirchoffs laws [2 marks]
 b) Calculate the size of Current through the 5 ohms, 10 ohms and 2 ohms resistors respectively in **fig 2** below [9 marks]

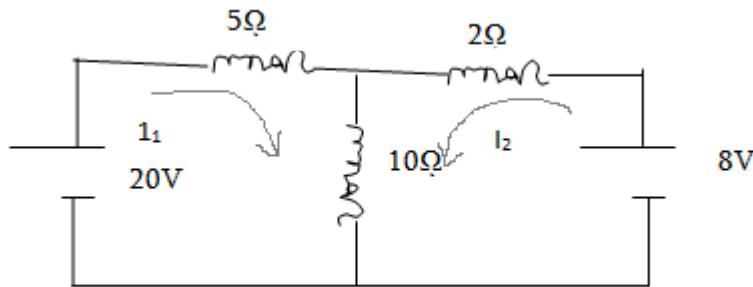


Fig 2

- c) Calculate the magnitude of electric field E in which an electron placed in the field would experience a force equivalent to its own weight. [4 marks]
 d) A step up transformer is designed to operate from a 20V supply and delivers energy at 250V. if the transformer is 90 percent efficient, determine the current in its primary winding when the output terminals are connected to a 250V, 100W lamp [5 marks]

QUESTION FOUR (20 MARKS)

- a. A vertical rectangular coil of sides 5cm by 2cm has 10 turns and carries a current of 2A. Calculate the torque on the coil when it is placed in a uniform horizontal field of 0.1T with its plane at 30° to the field. [4 marks]
 b. A solenoid is 4 cm long and 10 turns per cm. each of the solenoid has an area of 50cm^2 . Calculate the value of self inductance in the solenoid [4 marks]
 c. Derive an expression for the inductance of a toroid of rectangular cross-section shown in **fig 3** below. Evaluate the inductance. For $N=10^3$, $a = 5.0\text{cm}$, $b= 10\text{ cm}$ and $h=10\text{ cm}$. [8 marks]

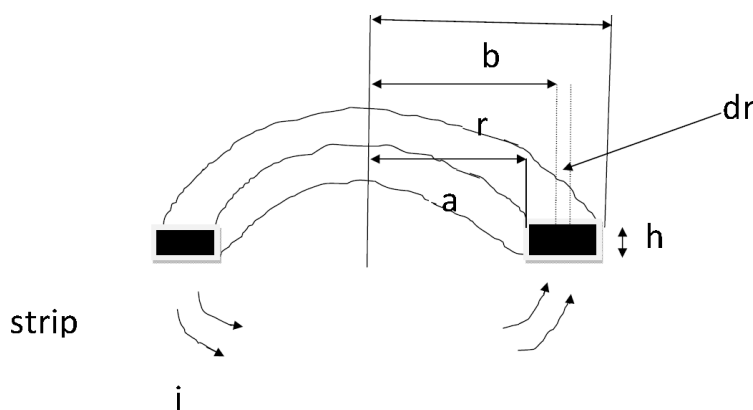


fig 3

- e) The fig 4 below is a circuit use it to answer the questions that follows assuming that $V_{BE} = 0.75\text{V}$ and that $h_{FE} = 80$.

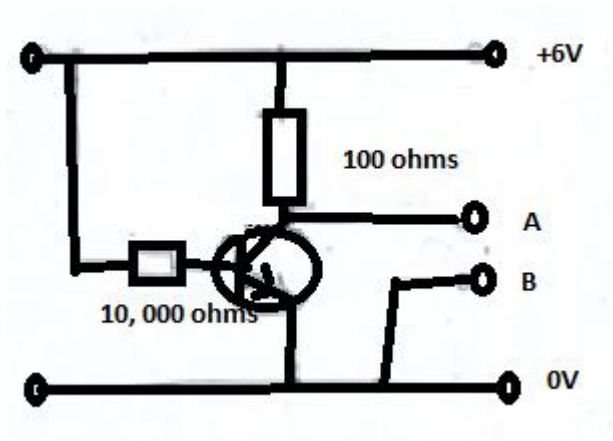


Fig 4

Calculate

- i. the base current [2 marks]
- ii. the collector current [2 marks]

QUESTION FIVE (20 MARKS)

- a. The **fig 5** below shows a bridge rectifier.

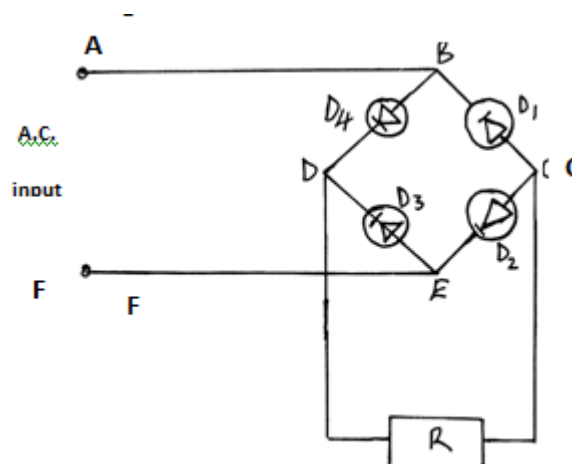


Fig 5

- i. Define the term rectification. (1 mark)
 - ii. Describe how the illustrated rectifier works. (5 marks)
 - iii. State the modification that can be made on the arrangement to improve the quality of the output. (1 mark)
 - iv. Sketch on the areas below how the improved output is displayed on a C.R.O screen. (1 mark)
- b. Explain how an n-type and p-type semiconductors are formed [6 marks]
- c. Using band gap theory explain the difference in insulators, metals and non-metals [6marks]