



# **SOUTH EASTERN KENYA UNIVERSITY**

## **UNIVERSITY EXAMINATIONS 2016/2017**

### **FIRST SEMESTER EXAMINATION FOR THE DEGREE OF BACHELOR SCIENCE IN ELECTRONICS**

#### **ELC 404: INTEGRATED CIRCUIT DESIGN**

**7<sup>TH</sup> DECEMBER, 2016**

**TIME:10.30-12.30 P.M**

#### **INSTRUCTIONS TO CANDIDATES**

- **This paper consists of FIVE questions.**
- **Answer question ONE and any other TWO questions.**
- **Question ONE carries 30 mark while the other TWO questions carry 20 marks each**

#### **QUESTION 1, 30 MARKS [COMPULSORY]**

- a) What is an Integrated circuit [2 marks]
- b) Differentiate between direct and indirect band gap [4 marks]
- c) State two reasons why GaAS is used in many applications such as microwaves and ICs [2 marks]
- d) What is a charged coupled device (CCD) [2 mark]
- e) A particular layer of MOS circuit has resistivity of 10 Ohms-cm. the section is 55  $\mu\text{m}$  long, 5  $\mu\text{m}$  wide and 1  $\mu\text{m}$  thick. Calculate
- Sheet resistance [ 3 marks]
  - Resistance of the layer [ 2 marks]
- f) State tree advantages of using static CMOS [3 marks]
- g) Compare IC based on MOS and bipolar transistor technologies [3 marks]
- h) Draw the circuitry representation of  $I^2L$  inverter [2 marks]

- i) Describe three general functions of computer register [ 3 marks]
- j) Draw a CMOS schematic diagram implementation of D-latch [4 marks]

**QUESTION 2 [20 MARKS]**

- a) Explain the functions of the following registers
- i. Memory address register [2 marks]
  - ii. Program counter [2 marks]
  - iii. Accumulator register [2 marks]
  - iv. Memory data register [2 marks]
- b) Describe the two types of charged coupled devices [8 marks]
- c) Draw the logic operations- NAND gate and its truth table [4 marks]

**QUESTION 3, [20 MARKS]**

- a) State two main factors considered during design of any basic circuit [ 2 marks]
- b) State two models used by IC designers to shrink the size of a circuit [2 marks]
- c) Define the following terminologies used in ICs designs
- i. Epitaxy [1 mark]
  - ii. Wafer [1 mark]
  - iii. Metallization [1 mark]
  - iv. Bonding [ 1 mark]
- d) Using a physical structure of p-Si substrate with a thin film layer of SiO<sub>2</sub> describe the process of photolithography [12 marks]


**QUESTION 4, [20 MARKS]**

- a) State three advantages of using dynamic CMOS [3 marks]
- b) Draw a CMOS inverter circuit and its transfer characteristics [5 marks]
- c) State and explain three circuit elements used in CMOS and radio frequency design [6 marks]
- d) Draw the physical structure of BiMOS npn transistor [6 marks]

### QUESTION 5, [20 MARKS]

- a) The figure 1 below shows a DTL circuit model with high inputs. Use it to attempt questions that follow. Given that  $\beta = 40$ , in the diagram  $5K=5k\Omega$  and  $2.2K=2.2k\Omega$ ,  $+5=+5V$ ,  $0.7=0.7V$ ,  $0.2=0.2V$  and  $0.8=0.8V$

**Figure 1**

 

Given that all the outputs are high and all the system is saturated. Find

- i. The voltage at point P [2 marks]
- ii. The current  $I_1$  [1 marks]
- iii. The current  $I_2$  [1 marks]
- iv. The current  $I_B$  [2 marks]
- v. Calculate the maximum collector current when the transistor is saturated [2 marks]
- vi. The current  $I_3$  [2 marks]
- vii. The maximum load current,  $V_{in}$  and  $I_{in}$  [3 marks]

- b) Using inverters, and gates and OR gates implement a  $5 \times 8 \times 4$  (V\*P\*Z) programmable logic array with following outcomes [7 marks]

$$z_1 = \bar{a}\bar{b}\bar{d}e + \bar{a}\bar{b}\bar{c}\bar{d}\bar{e} + bc + de$$

$$z_2 = \bar{a}\bar{c}e$$

$$z_3 = bc + de + \bar{c}\bar{d}\bar{e} + bd$$

$$z_4 = \bar{a}\bar{c}e + ce$$