

2506/202
2507/202
ELECTRONICS AND
CONTROL SYSTEMS
Oct./Nov. 2016
Time: 3 hours



THE KENYA NATIONAL EXAMINATIONS COUNCIL
DIPLOMA IN AERONAUTICAL ENGINEERING
(AIRFRAMES AND ENGINES OPTION)
(AVIONICS OPTION)
MODULE II

ELECTRONICS AND CONTROL SYSTEMS

3 hours

INSTRUCTIONS TO CANDIDATES

You should have the following for this examination:

*Scientific calculator (Non-Programmable); and
Answer booklet.*

This paper consists of EIGHT questions in TWO sections; A and B.

Answer any THREE questions from section A, and any TWO questions from section B in the answer booklet provided.

All questions carry equal marks.

Maximum marks for each part of a question are as shown.

Candidates should answer the questions in English.

This paper consists of 8 printed pages and 1 insert.

Candidates should check the question paper to ascertain that all the pages are printed as indicated and that no questions are missing.

SECTION A: ELECTRONICS

Answer any **THREE** questions from this section.

1. (a) (i) State Demorgan's theorems and show how they can be implemented using logic gates. (6 marks)
- (ii) Simplify the logical expression $f = \overline{A}B\overline{C} + A\overline{B}\overline{C}D + A\overline{C}$ using rules of Boolean algebra. (4 marks)
- (b) Convert the octal number $(1745.246)_8$ into its equivalent hexadecimal number. (4 marks)
- (c) State any **three** merits of Gray code. (3 marks)
- (d) Figure 1 shows the interconnection of NOR gates to form a flip-flop.


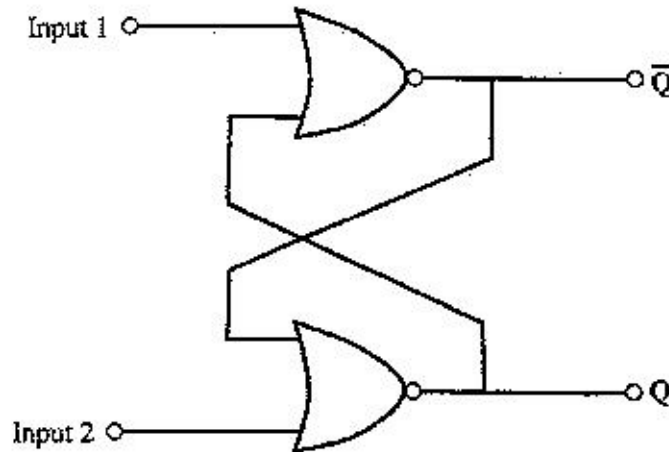


Fig. 1

- (i) Identify the type of flip-flop;
- (ii) Draw its truth table. (3 marks)
2. (a) With the aid of a circuit diagram, explain the operation of a dynamic RAM cell. (6 marks)

Name

Index No. /

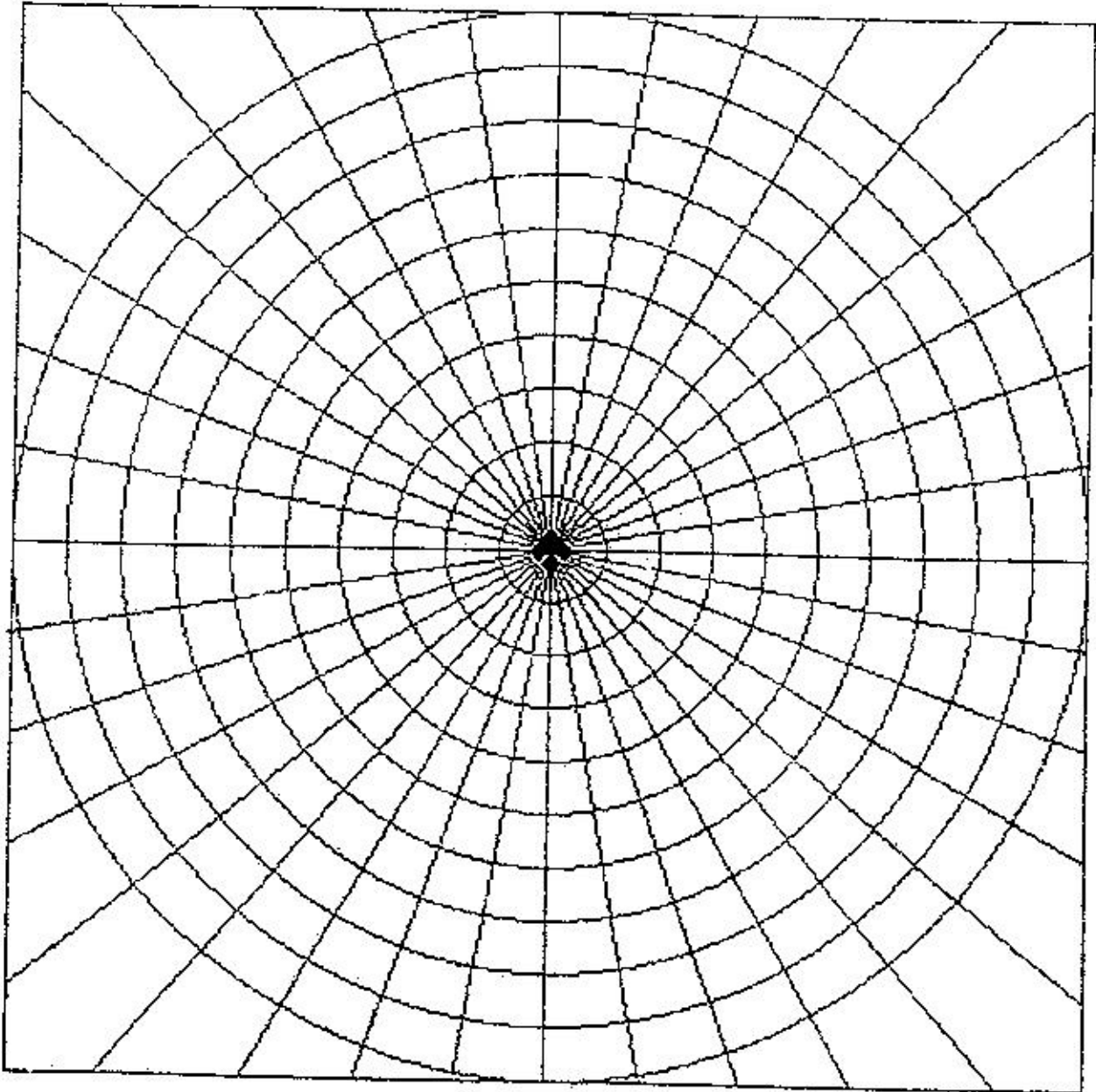

(b) Figure 2 shows a type of sequential logic circuit.

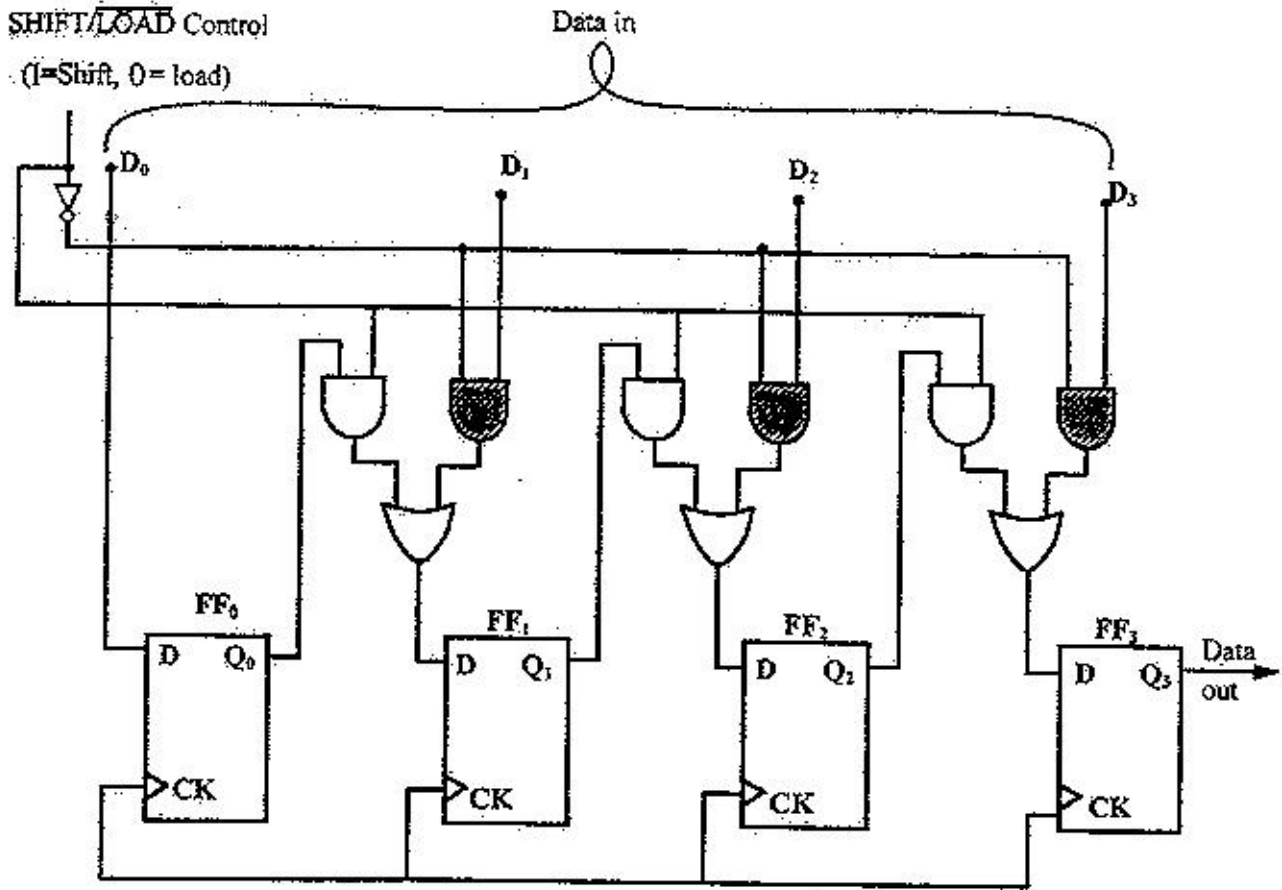


Fig. 2

- (i) identify the device;
- (ii) explain its operation.

(5 marks)

(c) A combinational circuit has 3 inputs A, B, C and output F. F is true for the following input combinations:

A is false, B is true;
 A is false, C is true;
 A, B, C are false;
 A, B, C are true.

- (i) Draw the truth table for F. Use the convention true = 1 and false = 0.
- (ii) Using a K-map, write the simplified expression for F.
- (iii) Draw the logic circuit diagram using NAND gates only.

(9 marks)

3. (a) State any two applications of a varactor diode in electronics. (2 marks)
- (b) (i) Explain each of the following in relation to operational amplifiers:
- (I) slew rate;
 - (II) input offset voltage.
- (ii) The input to an OP-amp differentiator circuit is a sinusoidal voltage of peak value $10 \mu\text{V}$ and frequency of 2 kHz . If the values of differentiating components are given as $R = 40 \text{ K}\Omega$ and $C = 3 \mu\text{F}$. Determine the output voltage. (7 marks)
- (c) Figure 3 shows a circuit diagram of a triangular-to-square wave shaping circuit. Describe its operation. (5 marks)

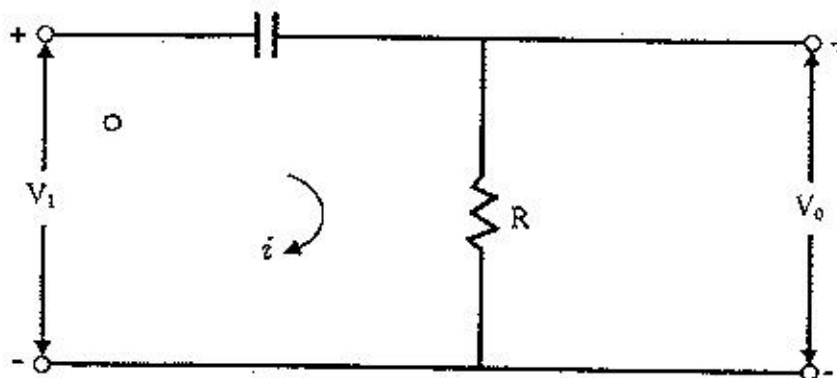


Fig. 3

- (d) With the aid of circuit diagram, explain the operation of a positive wave clipper. (6 marks)
4. (a) Define each of the following as applied in semi-conductor theory:
- (i) hole;
 - (ii) doping. (2 marks)
- (b) With the aid of a diagram, explain the formation of an N-type semi-conductor. (7 marks)

- (c) Figure 4 shows a BJT transistor biased circuit.

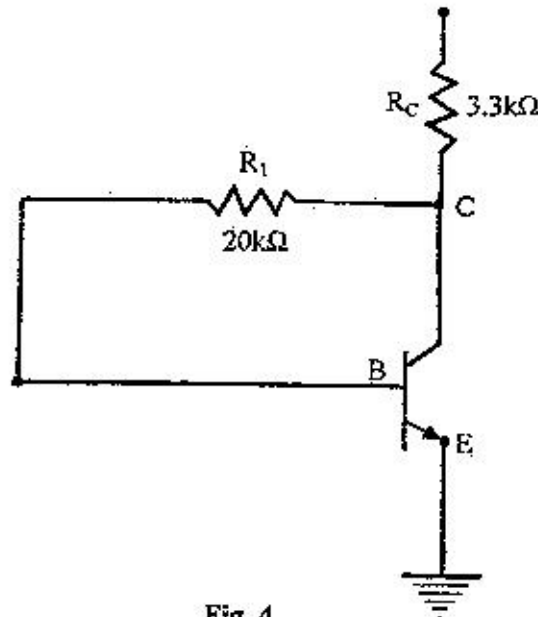


Fig. 4

If $I_E = 2\text{mA}$; $V_{BE} = 0.7$ and $\alpha = 0.98$. Calculate:

- (i) collector current, I_c ;
- (ii) current through R_1 .

(5 marks)

- (d) With the aid of a diagram, explain the construction of a Unijunction Transistor (UJT).

(6 marks)

5. (a) (i) Define each of the following terms as applied in Digital to Analog Conversion (DAC):

- (i) resolution;
- (ii) accuracy.

- (ii) With the aid of a circuit diagram, explain the operation of a 4-bit Binary-weighted resistor DAC.

(10 marks)

- (b) A tuned collector oscillator operates at 22 kHz when a variable capacitor is set to 2 nF. Determine the value of the tuned circuit inductance.

(3 marks)

- (c) With the aid of a construction diagram, explain the principle of operation of an LED display.

(7 marks)

SECTION B: CONTROL SYSTEMS

Answer any TWO questions from this section.

6. (a) Figure 5 shows a signal flow graph for a control system:

(i) Draw its equivalent block diagram;

(ii) Obtain the transfer function using block diagram reduction rules.

(10 marks)

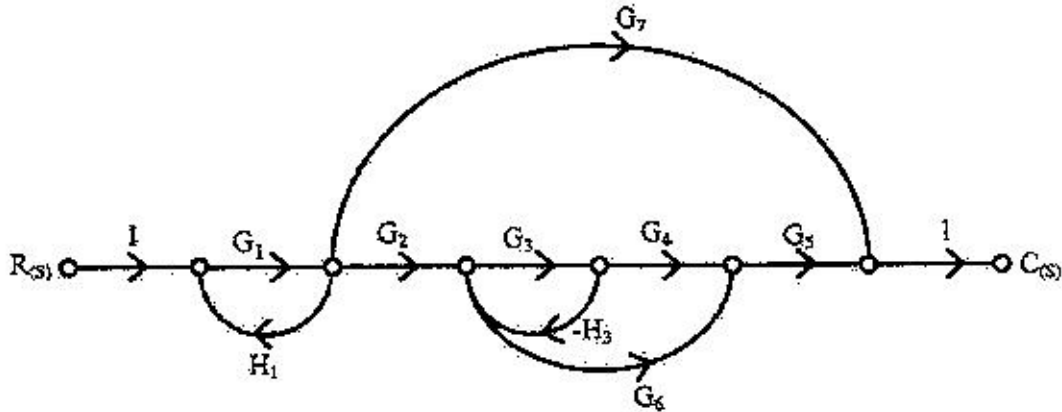


Fig. 5

(b) The open loop transfer function of a unity feedback second order control system is given by $G(s) = \frac{25}{S(S+5)}$

(i) Derive an expression for the characteristic equation;

(ii) Determine:

- (I) damping factor;
- (II) maximum overshoot;
- (III) peak time.

(10 marks)

7. (a) State three characteristics of an ideal op-amp.

(3 marks)

(b) Table 1 shows the open-loop harmonic frequency response of a control system.

- (i) Plot the bode diagram for the system;
- (ii) Determine the gain and phase margins;
- (iii) Describe the stability of the system.

(10 marks)

Table 1

Frequency in rad/s	0.1	0.4	1	4	10	40
Gain (dB)	43	31	23	11	0	-24
Phase lag (deg)	-94	-100	-108	-144	-180	-244

(c) A unity feedback control system has

$$G(s) = \frac{K}{s(s+10)(s^2+4s+5)}$$

Determine the range of K for the closed loop system to be stable.

(7 marks)

8. (a) (i) State **three** essential features of a servo-mechanism.

(ii) Define each of the following in relation to servo-systems:

- (I) time lag;
- (II) frequency response.

(5 marks)

(b) Figure 6 shows a circuit diagram of an electrical network. Derive its transfer function.

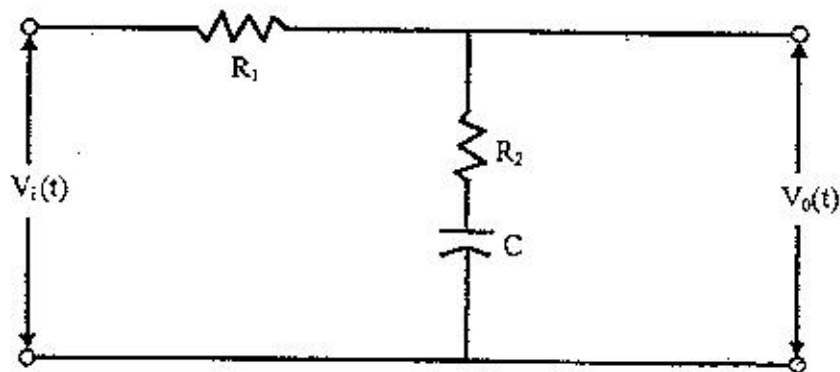


Fig. 6

(5 marks)

- (c) The open-loop transfer function of a control system is given by

$$G(s) = \frac{50}{(1 + 2.5s)(1 + 0.05s)}$$

Sketch its Nyquist diagram.

(10 marks)

THIS IS THE LAST PRINTED PAGE.