



MERU UNIVERSITY OF SCIENCE AND TECHNOLOGY

P.O. Box 972-60200 – Meru-Kenya.

Tel: 020-2069349, 061-2309217. 064-30320 Cell phone: +254 712524293, +254 789151411

Fax: 064-30321

Website: www.must.ac.ke Email: info@must.ac.ke

University Examinations 2013/2014

**STAGE 3, EXAMINATION FOR DIPLOMA/CERTIFICATE IN INFORMATION
TECHNOLOGY**

DIT 0304: ELECTRONIC CONSTRUCTION I

DATE: APRIL 2014

TIME: 1½ HOURS

INSTRUCTIONS: Answer questions *one* and any other *two* questions

QUESTION ONE - (30 MARKS)

- a) What is an electric circuit? (2 marks)
- b) State the role of the following components in an electric circuit:-
- i. Source (2 marks)
 - ii. Switch (1 mark)
 - iii. Load (2 marks)
 - iv. Conductor (1 mark)
- c) What is a resistor? (1 mark)
- d) Calculate the effective resistance of the following resistor network: (3 marks)

- e) Two capacitors of capacitance $10\mu\text{F}$ and $15\mu\text{F}$ are connected in series. Determine the effective capacitance. (3 marks)
- f) Identify any FOUR factors that determine the inductance of a coil of wire. (4 marks)
- g) What is a diode? (1 mark)
- h) Draw the correct circuit symbols for the following devices: (2 marks)
- i. NPN transistor
 - ii. Silicon Controlled Rectifier (SCR)
- i) What is a simpler way of expressing $0.000\ 005\ \text{A}$? (1 mark)
- j) A p.d of 6V causes a current of 0.6A to flow in a conductor. Calculate the resistance of the conductor. (3 marks)
- k) The trace displayed by a CRO shown below:

The signal amplitude control is set to 0.5V/cm and the time-based control to $100\mu\text{s/cm}$.

Determine the peak-to-peak voltage of the signal and its frequency. (4 marks)

QUESTION TWO –(15 MARKS)

- a) What do the following terms mean?
- i. Positive coefficient of resistance (2 marks)
 - ii. Negative coefficient of resistance (2 marks)
- b) State the four factors that determine the resistance of a wire. (2 marks)

- c) Three resistors of resistance value 2ohms and 4 ohms are connected in parallel to a 12 volt battery.
- i. Draw a circuit diagram of the arrangement. (3 marks)
 - ii. Determine the total circuit resistance. (3 marks)
 - iii. Determine the total circuit current. (3 marks)

QUESTION THREE– (15 MARKS)

- a) What is a capacitor? (2 marks)
- b) State the three factors that determine the capacitance of a capacitor. (3 marks)
- c) Determine the effective capacitance of the following capacitor network.

- The capacitance of each capacitor is $4\mu\text{F}$. (4 marks)
- d) What is inductance? (2 marks)
- e) State any FOUR practical applications of inductance. (2 marks)
- f) What is the effective inductance of the following inductor circuit? (2 marks)

QUESTION FOUR- (15 MARKS)

- a) What is a diode? (2 marks)
- b) Name any four types of diode. (2 marks)
- c) Shown below is one application of a diode:
- i. Sketch the output voltage the load resistor R_L experiences in the above circuit. (2 marks)
 - ii. What name is given to the above circuit? (1 mark)
- d) What is silicon controlled rectifier (SCR)? (2 marks)
- e) State any two applications of the SCR. (2 marks)
- f) What current will flow in the zener diode circuit shown below?

QUESTION FIVE – (15 MARKS)

- a) What is a Field effect Transistor (FET)? (2 marks)
- b) Name any two types of FET and indicate their respective circuit symbols. (4 marks)
- c) State any four uses of FETs (4 marks)
- d) State the two rules that guide on correct operational amplifier analysis. (2 marks)
- e) Shown below is an op-amp inverting amplifier. Determine its voltage gain.