



# MURANG'A UNIVERSITY OF TECHNOLOGY

## SCHOOL OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

UNIVERSITY ORDINARY EXAMINATION

2017/2018 ACADEMIC YEAR

**SECOND YEAR FIRST SEMESTER EXAMINATION FOR THE DIPLOMA IN  
ELECTRICAL AND ELECTRONIC ENGINEERING**

SEE 1202 – ANALOGUE ELECTRONICS II

DURATION: 2 HOURS

DATE:

TIME:

### **Instructions to Candidates:**

1. Answer **Question 1** and **Any Other Two** questions.
2. Mobile phones are not allowed in the examination room.
3. You are not allowed to write on this examination question paper.

## SECTION A – ANSWER ALL QUESTIONS IN THIS SECTION

### QUESTION ONE

- a) Explain the following classes of amplifiers:
- Class-A amplifier
  - Class-B amplifier
  - Class-C amplifier
  - Class-AB amplifier (4 marks)
- b) In a class B amplifier,  $V_{CE(\min)}=2V$  and  $V_{CC}=15V$ . Calculate its overall efficiency. (3 marks)
- c) State two advantages of RC coupling. (2 marks)
- d) State two advantages of negative feedback. (2 marks)
- e) Define the term distortion as used in amplifiers. (2 marks)
- f) An amplifier has an open-loop gain of 400 and a feedback of 0.1. If open-loop gain changes by 20% due to temperature, find the percentage change in closed-loop gain. (3 marks)
- g) A differential amplifier has an open-loop gain of 150 and a common input signal of 4.0V to both terminals. If an output signal of 15mV results, determine:
- Common-mode gain and
  - Common-Mode Rejection Ratio (CMRR) (4 marks)
- h) A filter section is required to pass all frequencies above 50kHz and to have a nominal impedance of  $300\Omega$ . Design a high-pass  $\pi$ -section filter to meet these requirements. (6 marks)
- i) Define the following terms as used in oscillators:
- Damped oscillations
  - Undamped oscillations (4 marks)

## SECTION B – ANSWER ANY TWO QUESTIONS IN THIS SECTION

### QUESTION TWO

- a) State four applications of Silicon-Controlled Rectifiers (SCRs) (4 marks)
- b) Using appropriate diagrams, show each of the following types of waveforms:
- Sine waveform
  - Saw-tooth waveform
  - Pulse waveform (6 marks)

- c) Design an OP-amp that will produce an output equal to  $-(4V_1+V_2+0.1V_3)$ . Write an expression for the output and sketch its output when  $V_1=2\sin \omega t$ ,  $V_2=+5V_{d.c.}$  and  $V_3=100V_{d.c.}$  (10 marks)

### QUESTION THREE

- a) Distinguish between linear and non-linear distortion. (4 marks)
- b) Define the following terms as used in filter networks:
- Attenuation
  - Cut-off frequency,  $f_c$
  - Nominal impedance,  $R_o$  (3 marks)
- c) The parameters of a crystal oscillator equivalent circuit are  $L_1=0.8H$ ;  $C_1=0.08pF$ ;  $f=5kHz$  and  $C_2=1.0pF$ . Determine the resonant frequency  $f_1$ . (3 marks)
- d) For the single stage Common-Emitter (CE) amplifier shown in figure 1,  $R_B=1M\Omega$ ,  $R_C=10k\Omega$ ,  $V_{cc}=20V$ ,  $R_L=10k\Omega$ , and  $\beta = 50$ .

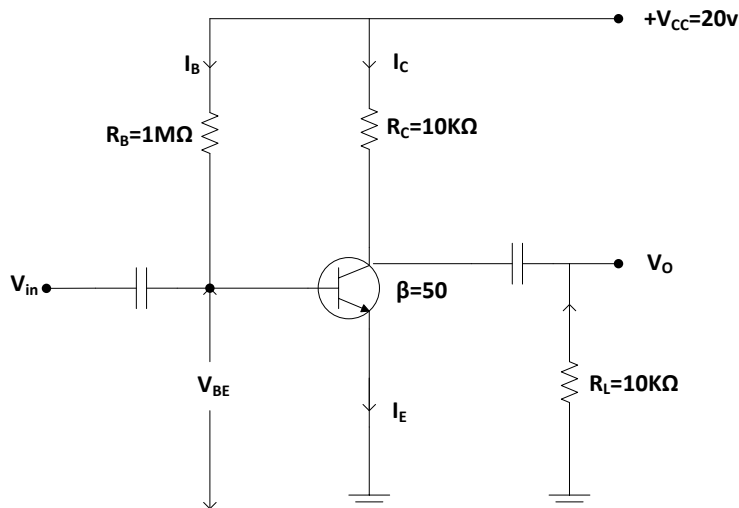


fig 1

Calculate:

- $V_{in}$
- $r_o$
- $A_i$
- $A_v$
- Gp in dB

## QUESTION FOUR

- a) In a negative feedback feedback amplifier,  $A=50$ ,  $\beta = 0.05$  and  $V_i = 100\text{mV}$ . Find:
- Gain with feedback,  $A$
  - Output voltage,  $V_o$
  - Feedback factor
  - Feedback voltage
- (8 marks)
- b) Define the following OP-amp parameters:
- Input bias current
  - Slew rate
- (4 marks)
- c) For the differential amplifier shown in figure 2, determine the output voltage,  $V_o$  if:
- $V_1=4\text{mV}$  and  $V_2=0$
  - $V_1=40\text{mV}$  and  $V_2=30\text{mV}$
- (8 marks)

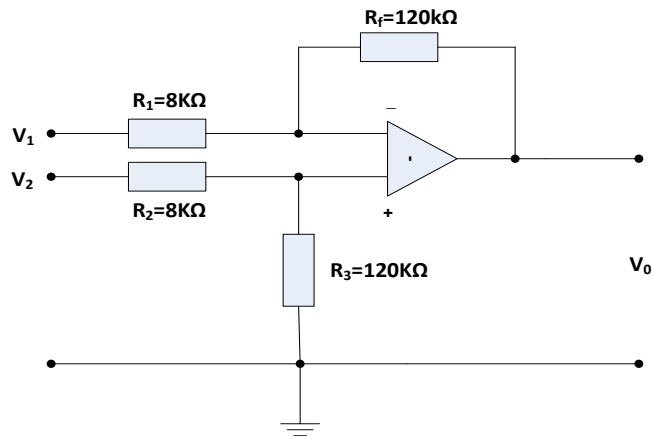


Fig 2