

CHUKA



UNIVERSITY

UNIVERSITY EXAMINATIONS

EXAMINATION FOR THE AWARD OF DEGREE OF BACHELOR OF
SCIENCE (PHYSICS) AND BACHELOR OF EDUCATION (SCIENCE)

PHYS 423: ANALOGUE ELECTRONICS

STREAMS: Y4S2 BSC (GEN)BED (SC)

TIME: 2 HOURS

DAY/DATE: TUESDAY 10/04/2018

2.30 P.M – 4.30 P.M

INSTRUCTION:

- Answer question one and any other two questions

Question one (30 marks)

- Explain why the base of a BJT transistor is lightly doped while the emitter is heavily doped. (2marks)
- What do you understand by the term “biasing” in transistors (1mark)
- Differentiate between voltage follower and differential amplifier (2marks)
- With the help of circuit diagrams, discuss the three basic configurations of the operational Amplifiers (OPAMPS) (3marks)
- The transistor from a p and n type semiconductor doesn't conduct at 0 V but slight above this value (0.7 V for silicon). Explain this observation (3marks)
- How is the resistance of a semiconductor material as compared to that of a metal (2marks)
- Discuss the output transfer characteristics ($I_C - V_{CE}$) of a BJT transistor for various V_{BE} (4marks)
- Explain the terms modulation and demodulation as used in electronics (2marks)
- A transistor amplifier has a gain that varies with frequency. Explain this observation with a curve (Bode plot) (3marks)
- Class B power amplifiers have zero current when the input signal is zero. With a circuit symbol, explain how it is designed and show its output (5marks)
- Differentiate between JFET and BJT transistors from their design point of view (3marks)

Question two (20 marks)

- (a) Figure 2.1 shows an operational amplifier circuit that was used in the input stage of a loudspeaker. The source voltage (V_{in}) is sinusoidal and there are no distortion of the output voltage (V_{out}).

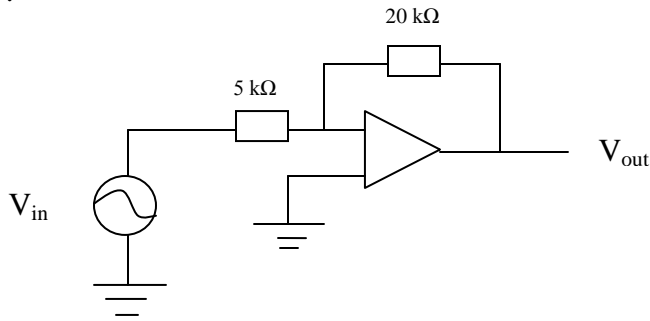


Figure 2.1. Operational amplifier circuit

- (i) Sketch the waveform for the output voltage in relation to that of the input voltage.
Explain your answer. (3marks)
- (ii) Calculate the voltage gain of this amplifier configuration (3marks)
- (b) Class B push pull amplifiers are known to have cross over distortion problems. With the help of a waveform, discuss the effect of this problem in sound producing devices ie loudspeaker (6marks)
- (c) With a well labeled circuit diagram, show the circuit symbol of n-channel and p-channel MOSFET (4marks)
- (d) For high amplification, a multistage transistor amplifier is preferred. Describe how this is designed (4marks)

Question three (20 marks)

- (a) With circuit diagrams, describe how an operational amplifier is configured as an integrator and a differentiator (6marks)
- (b) Figure 3.1 shows a two stage current amplifier used in a sensor circuit with BJT transistors Tr_1 and Tr_2 .

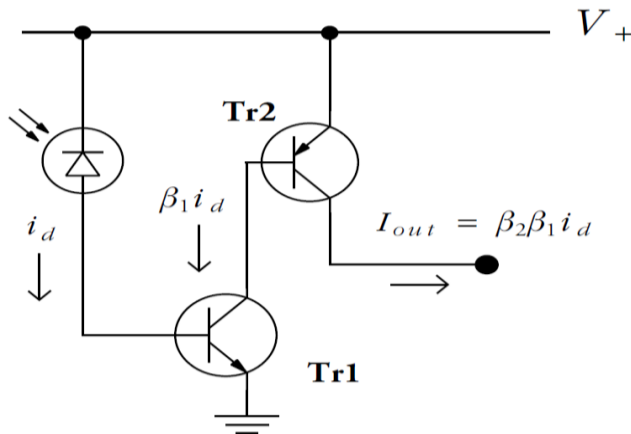


Figure 3.1. A two stage current amplifier based on BJT transistors.

- (i) Briefly explain how the current i_d is generated in the circuit when light falls on the given diode as shown. (3marks)
- (ii) What is the purpose of V_+ voltage connected to the transistor Tr_2 and the diode. (2marks).
- (iii) Given $\beta_1 = 200$ and $\beta_2 = 100$, calculate the gain of the two stage current amplifier (4marks)
- (iv) Describe one practical application of the above circuit in security surveillance with slight addition of electronics components if any (3marks)
- (c) An OPAMP can be applied as a summing amplifier. Describe how this is designed. (2marks)

Question four (20 marks)

(a) An n-p-n transistor circuit is given in figure 4.1 with $\beta = 100$ and the transistor is made of silicon ie $V_{BE} = 0.7 \text{ V}$.

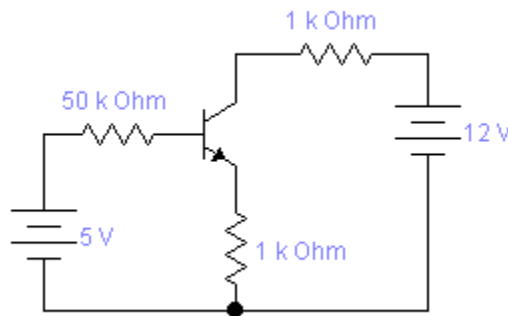


Figure 4.1. n-p-n transistor circuit.

Compute the following parameters for the given transistor

- (i) I_B (4mks)
- (ii) I_C (2mks)
- (iii) I_E (2mks)

- (iv) V_{CE} (3mks)
- (b) With a well labeled diagram, describe how the following diodes operate: Shotky diode, Zener diode and tunnel diode (6marks)
- (c) Explain why intrinsic semiconductor doesn't conduct electricity at room temperature . (3marks)

Question five (20 marks)

- (a) Figure 5.1 shows a bipolar junction transistor amplifier circuit that was used in the input stage of a sensor. If the source voltage (V_{in}) is equal to V_B , show that, the voltage gain of this amplifier is given by $-R_C/R_E$. (8marks)

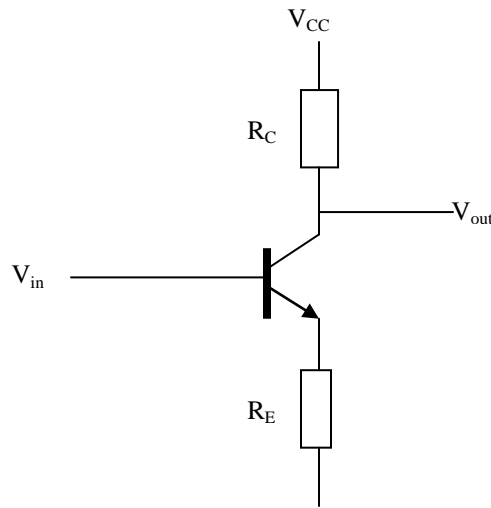


Figure 5.1. BJT amplifier circuit

- (b) With a well labeled diagram, describe how a junction field effect transistor with n-channel is constructed (6marks)
- (c) Discuss the input characteristics ($I_B - V_{BE}$) of a BJT transistor for various V_{CE} (4marks)
- (d) An OPAMP can be applied as a integrator amplifier. Describe how this is designed (2marks)
-